

CS & IT

Digital Logic

DPP: 1

Boolean Theorems & Logical Gates

- Q1** $(A + B)(A + C)(A + \overline{C})$ is equivalent to
 (A) $A + BC$ (B) $A + B\overline{C}$
 (C) 0 (D) A


- Q2** A logical function is given as:
 $f(A, B, C) = B\overline{C}[A + A\overline{C}D + \overline{B}CD + \overline{A}B\overline{C} + \overline{A}B\overline{C}]$
 is equivalent to
 (A) $\overline{A}\overline{B}CD$
 (B) $\overline{B}\overline{C}$
 (C) $\overline{A}\overline{B} + \overline{B}\overline{C} + CD$
 (D) $AB\overline{C}D$

- Q3** If we have 4-variables in a logical function, then number of non-dual logical functions possible_____.

- Q4** A logical function $f(A, B, C) = (A + B)(\overline{B} + C)(A + C)$, then $\overline{f}$ will be equal to
 (A) $AB + \overline{B}C$
 (B) $\overline{A}\overline{B} + \overline{B}\overline{C}$
 (C) $\overline{A}\overline{B} + \overline{A}\overline{C}$
 (D) $AB + AC$

- Q5** Which of the following statement is true?
 (A) Dual function f^D is always equals to f .
 (B) NAND is self dual in nature.
 (C) NOT is self dual in nature.
 (D) Number of self dual function with 3-variables is 8.

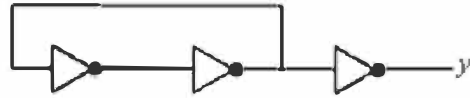
- Q6** A digital circuit is designed as shown:



This circuit works as

- (A) Astable multivibrator as odd number of Not gates are used.
 (B) Bistable multivibrator
 (C) Monostable multivibrator
 (D) None of these

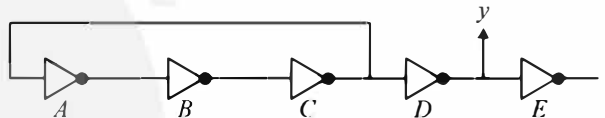- Q7** An astable multivibrator circuit is designed as shown:



NOT gates A, B & C are of logic family TTL with delay $t_d = 20/3$ nsec of each gate and gates D & E are of logic family ECL with delay $t'_d = 10/3$ nsec of each gate, then frequency of the waveform at output y is _____ MHz.


- Q8** Logical function $f(A, B, C, D) = AB + \overline{A}CD + \overline{B}CD$ is equivalent to
 (A) $AB + \overline{B}C$
 (B) $AB + CD$
 (C) $\overline{A}C + \overline{B}C$
 (D) $AB + \overline{B}C$

- Q9** A logical function is given as:
 $f(A, B, C) = \overline{A}\overline{B} + \overline{A}BC + \overline{A}B\overline{C}$
 then which of the following statement is true?
 (A) $f(A, B, C) = \overline{A}\overline{B} + \overline{B}\overline{C}$
 (B) $f(A, B, C) = \overline{A} + \overline{C}$
 (C) $f(A, B, C)$ is a self dual function.



(D) None of the above

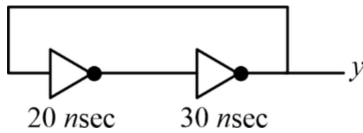Q10 A logical circuit is designed as shown:



Output y is

- (A) A bistable multivibrator's output
- (B) A square waveform with $f = 10$ MHz
- (C) A square waveform with $f = 25$ MHz
- (D) None of the above.

Q11 Which of the following is true?

- (A) $\overline{A}B + A\overline{B} = (\overline{A} + \overline{B})(A + B)$
- (B) $\overline{A}B\overline{C}D = \overline{A} + \overline{B} + \overline{C} + \overline{D}$
- (C) $\overline{A}\overline{B} \cdot C = (A + \overline{C})(\overline{B} + \overline{C})$
- (D) None of these


Q12 Which of the following is true?

- (A) We can use '1' as enable input for OR gate
- (B) We can use '0' as enable input for AND gate
- (C) '0' as well as '1' can be used as enable input for XNOR gate
- (D) None of these

Q13 Which of the following relation is true?

- (A) $A \oplus \overline{B} = \overline{A} \odot B$
- (B) $\overline{A} \oplus \overline{B} = A \odot B$
- (C) $\overline{A} \odot \overline{B} = A \oplus B$
- (D) $\overline{A} \oplus \overline{B} = A \oplus B$

Q14 A logical circuit is as given below:

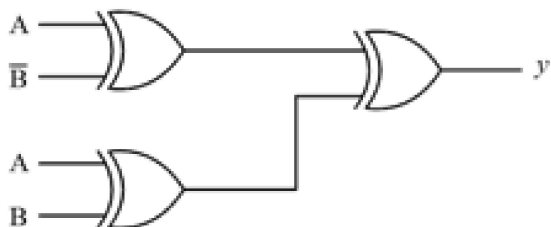

Output y will be


- (A) $\overline{A} + B$

(B) $\overline{A} + \overline{B}$

(C) $A\overline{B}$

(D) $A + B$

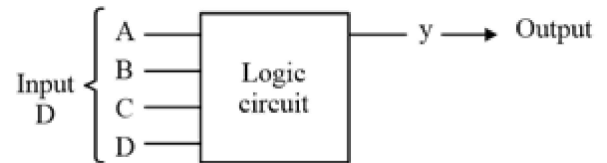
Q15 A logic circuit has 4-input & 1-output line as shown:



Output y is '1' wherever no. of zeroes on input side are odd, then output y can be expressed as:


- (A) $A \odot B \odot C \odot D$
- (B) $\overline{A} \odot B \odot C \odot D$
- (C) $\overline{A} \oplus B \oplus C \oplus D$
- (D) None of these

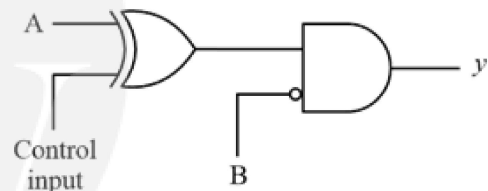Q16 A logic circuit is as given below:
Which of the following is true?



- (A) Output y is $\overline{A}B$ if control input = 0
- (B) Output y is $\overline{A} + \overline{B}$ if control input = 1
- (C) Output y is $\overline{A} \cdot \overline{B}$ if control input = 0
- (D) Output y is $\overline{A} \cdot B$ if control input = 1

Q17 A logic circuit is as given below:

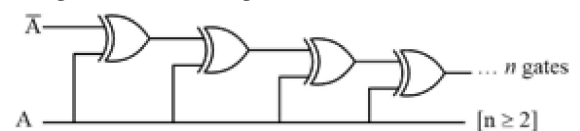


Which of the following is true?

- (A) Output is $\overline{A}$ if n is even
- (B) Output is A if n is even
- (C) Output is $\overline{A}$ if n is odd
- (D) Output is A if n is odd



Q18 A logical circuit is as given below:

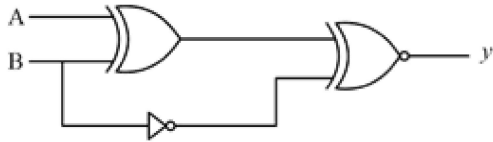

Output y is

- (A) A (B) $\overline{B}$
 (C) $\overline{A}$ (D) B

Q19 A logical expression is given as:

$$f(A, B, C, D) = \overline{A} + AB[ABC + \overline{B}C + AB\overline{C} + C\overline{D}]$$

then minimum number of 2-input NAND gate require to implement above logic function will be _____.

Q20 A logical expression is given as:

$$f(A, B, C) = (\overline{A} + B)(A + \overline{B}),$$

minimum number of 2-input NAND gate require to implement above logical function is .

Q21 A logical expression is given as:

$$f(A, B, C) = \overline{A} + ABC,$$

then minimum number of 2-input NAND gate require to implement above logical function is _____.

Q22 A logical function is given as:

$$f(A, B) = A \oplus A\overline{B},$$

If we implement this logical function using 2-input NAND gate then, minimum number of NAND gate require is



Answer Key

Q1 (D)
Q2 (B)
Q3 65280~65280
Q4 (B)
Q5 (C)
Q6 (B)
Q7 25~25
Q8 (B)
Q9 (C)
Q10 (A)
Q11 (C)

Q12 (C)
Q13 (C)
Q14 (B)
Q15 (B, C)
Q16 (B)
Q17 (A)
Q18 (A)
Q19 2~2
Q20 5~5
Q21 2~2
Q22 2~2



[Android App](#) | [iOS App](#) | [PW Website](#)