

CS & IT ENGINEERING



Digital Logic

Combinational Circuits

Lecture No. 02



By- Aditya sir

Recap of Previous Lecture



Topic



K-maps

Duality

Intro to Combinational ccts.

Topics to be Covered



Topic



Combinational ckts

→ Misc Concepts + Ques



About Aditya Jain sir



1. Appeared for GATE during BTech and secured AIR 60 in GATE in very first attempt - City topper
2. Represented college as the first Google DSC Ambassador.
3. The only student from the batch to secure an internship at Amazon. (9+ CGPA)
4. Had offer from IIT Bombay and IISc Bangalore to join the Masters program
5. Joined IIT Bombay for my 2 year Masters program, specialization in Data Science
6. Published multiple research papers in well known conferences along with the team
7. Received the prestigious excellence in Research award from IIT Bombay for my Masters thesis
8. Completed my Masters with an overall GPA of 9.36/10
9. Joined Dream11 as a Data Scientist
10. Have mentored 12,000+ students & working professions in field of Data Science and Analytics
11. Have been mentoring & teaching GATE aspirants to secure a great rank in limited time
12. Have got around 27.5K followers on LinkedIn where I share my insights and guide students and professionals.



Telegram



Telegram Link for Aditya Jain sir: [https://t.me/AdityaSir PW](https://t.me/AdityaSir_PW)

* Combinational Circuit :-

→ 1 > 1 bit magnitude Comparator :-

5 Step framework for ^{designing} Combinational ckt:

Step 1:- Find the no. of i/p's and o/p's.


Step 2:- Create the truth table.

Step 3:- Write down the logical expression.

Step 4:- Minimize the logical expression.

Step 5:- Design the circuit / Hardware impletn.

Summary of 1-bit Comparator:-

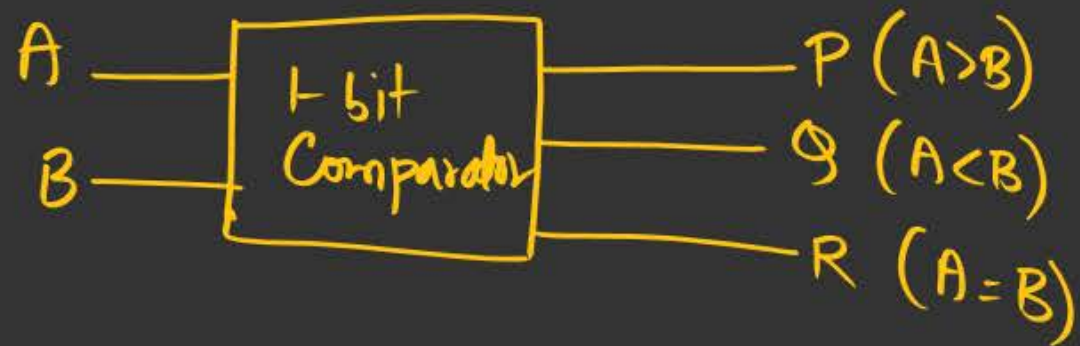


$$P (A > B) = A \cdot \overline{B}$$

$$Q (A < B) = \overline{A} \cdot B$$


$$\begin{aligned} R (A = B) &= \overline{A} \cdot \overline{B} + A \cdot B \\ &= A \odot B \end{aligned}$$

2) 2-bit Magnitude Comparator :-

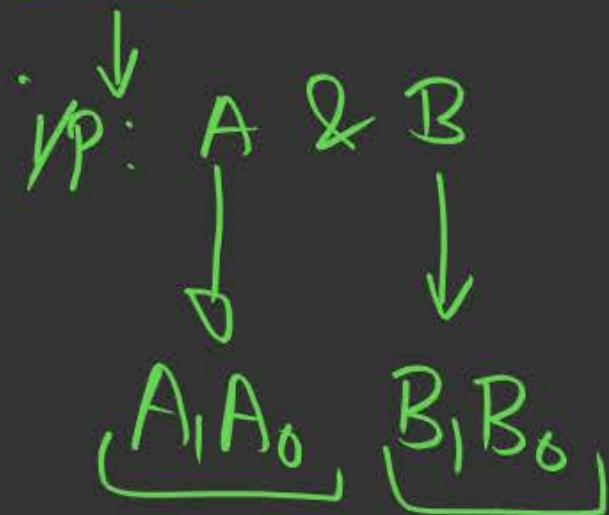

Step 1: I/p & o/p: ✓



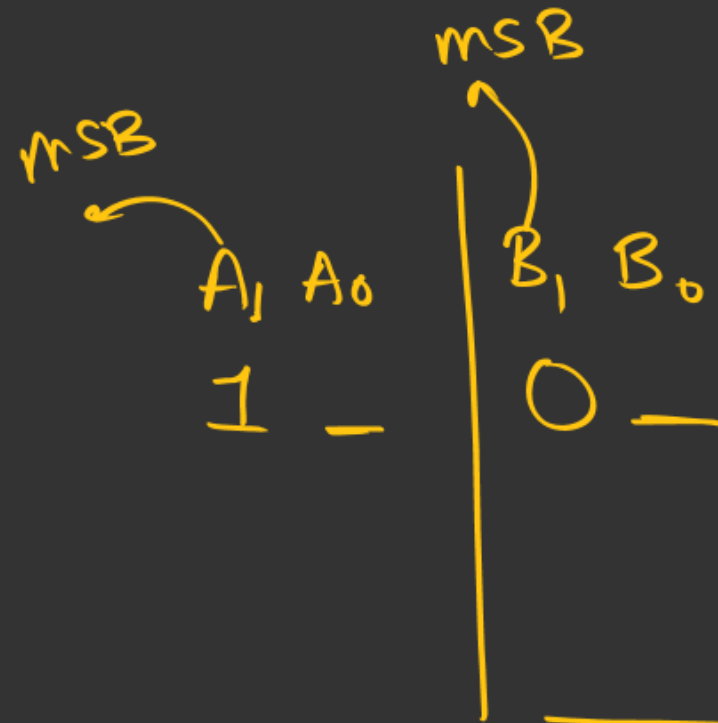

eg:-



eg:- 79 > 42

79 75

0	0	0	1	→ A < B
1	0	0	1	→ A > B
1	1	1	1	→ A = B

Step 2

Four-1
Fahn-0

Decimal	<u>A</u>		<u>B</u>		$(A > B)$ P	$(A < B)$ Q	$(A = B)$ R
	A ₁	A ₀	B ₁	B ₀			
0	0	0	0	0		0	1 ✓
1	0	0	0	1		1	0
2	0	0	1	0		1	0
3	0	0	1	1		1	0
4	0	0	1	1		1	0
5	0	1	0	0		0	0
6	0	1	0	1		0	1 ✓
7	0	1	1	1		0	0
8	1	0	0	0		0	0
9	1	0	0	1		0	0
10	1	0	1	0		0	1
11	1	0	1	1		0	0
12	1	1	0	0		0	0
13	1	1	0	1		0	0
14	1	1	1	0		0	0
15	1	1	1	1		0	0

Step 3:- Logical Expression:-

1) $P(A > B): \sum m(4, 8, 9, 12, 13, 14)$

2) $Q(A < B): \sum m(1, 2, 3, 6, 7, 11)$

3) $R(A = B): \sum m(0, 5, 10, 15)$

Step 4:- Minimization

For P $\Rightarrow \Sigma m(4, 8, 9, 12, 13, 14)$

A > B

Minimized SOP:

$A_1 A_0 \backslash B_1 B_0$	$\bar{B}_1 \bar{B}_0$	$\bar{B}_1 B_0$	$B_1 \bar{B}_0$	$B_1 B_0$
$\bar{A}_1 \bar{A}_0$	0	1	3	2
$\bar{A}_1 A_0$	4	5	7	6
$A_1 \bar{A}_0$	12	13	15	14
$A_1 A_0$	8	9	11	10

$A_0 \bar{B}_1 \bar{B}_0$ (points to cell 4)
 $A_1 \bar{A}_0$ (points to row 3)
 $A_1 A_0 \bar{B}_0$ (points to cell 14)
 $A_1 \bar{B}_1$ (points to cell 12)

$$\begin{aligned}
 F &= \underline{A_0} \bar{B}_1 \bar{B}_0 + A_1 \underline{A_0} \bar{B}_0 + A_1 \bar{B}_1 \\
 &= \underline{A_0 \bar{B}_0} (\bar{B}_1 + A_1) + \underline{A_1 \bar{B}_1}
 \end{aligned}$$

Step 4: Minimization

For $P \Rightarrow \Sigma m(4, 8, 9, 12, 13, 14)$

$$\underline{\underline{A > B}}$$

★ Semi-minimized

$A_1 A_0 \backslash B_1 B_0$	$\bar{B}_1 \bar{B}_0$	$\bar{B}_1 B_0$	$B_1 \bar{B}_0$	$B_1 B_0$
$\bar{A}_1 \bar{A}_0$	0	1	3	2
$\bar{A}_1 A_0$	4	5	7	6
$A_1 \bar{A}_0$	12	13	15	14
$A_1 A_0$	8	9	11	10

$\bar{A}_1 A_0 \bar{B}_1 \bar{B}_0$ (points to cell 4)
 $A_1 \bar{A}_0$ (points to row 3)
 $A_1 \bar{B}_1$ (points to column 1)
 $A_1 A_0 B_1 \bar{B}_0$ (points to cell 14)

$$\begin{aligned}
 f &= A_1 \bar{B}_1 + \bar{A}_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 B_1 \bar{B}_0 \\
 &= A_1 \bar{B}_1 + (\bar{A}_1 \bar{B}_1 + A_1 B_1) \cdot A_0 \bar{B}_0 \\
 &= A_1 \bar{B}_1 + (A_1 \oplus B_1) \cdot A_0 \bar{B}_0
 \end{aligned}$$

for Q:- $\Sigma m(1, 2, 3, 6, 7, 11)$

$A_1 A_0 \backslash B_1 B_0$	$\bar{B}_1 \bar{B}_0$	$\bar{B}_1 B_0$	$B_1 \bar{B}_0$	$B_1 B_0$
$\bar{A}_1 \bar{A}_0$	0	1	3	2
$\bar{A}_1 A_0$	4	5	7	6
$A_1 \bar{A}_0$	12	13	15	14
$A_1 A_0$	8	9	11	10

Annotations on the K-map:

- A circle around cells 1, 3, 5, 7 is labeled $\bar{A}_1 \bar{A}_0 B_0$.
- A circle around cells 3, 7, 11, 15 is labeled $\bar{A}_1 B_1$.
- A circle around cells 9, 11 is labeled $A_0 B_1 B_0$.

$B > A$

minimized SOP

$$F = \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$$

$$= \bar{A}_1 B_1 + (\bar{A}_1 + B_1) \cdot \bar{A}_0 B_0$$

for Q: $\Sigma m(1, 2, 3, 6, 7, 11)$

$B > A$

$A_1 A_0 \backslash B_1 B_0$		$B_1 B_0$			
		$\bar{B}_1 \bar{B}_0$	$\bar{B}_1 B_0$	$B_1 \bar{B}_0$	$B_1 B_0$
$\bar{A}_1 \bar{A}_0$	0	1	3	2	
$\bar{A}_1 A_0$	4	5	7	6	
$A_1 \bar{A}_0$	8	9	11	10	
$A_1 A_0$	12	13	15	14	

Annotations:
 - A group of four cells (1, 3, 7, 6) is circled in orange, labeled $\bar{A}_1 B_1$.
 - A group of two cells (1, 11) is circled in orange, labeled $A_1 \bar{A}_0 B_1 B_0$.
 - The expression $\bar{A}_1 \bar{A}_0 \bar{B}_1 B_0$ is written above the first row, second column.

Semi-minimized SOP

$$\begin{aligned}
 F &= \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 \bar{B}_1 B_0 + A_1 \bar{A}_0 B_1 B_0 \\
 &= \bar{A}_1 B_1 + (\bar{A}_1 \bar{B}_1 + A_1 B_1) \cdot \bar{A}_0 B_0 \\
 &= \bar{A}_1 B_1 + (A_1 \odot B_1) \cdot \bar{A}_0 B_0
 \end{aligned}$$

for R: $\sum m(0, 5, 10, 15)$


$A_1 A_0$	$B_1 B_0$	$\bar{B}_1 \bar{B}_0$	$\bar{B}_1 B_0$	$B_1 \bar{B}_0$	$B_1 B_0$
$\bar{A}_1 \bar{A}_0$	0	1	3	2	
$\bar{A}_1 A_0$	4	5	7	6	
$A_1 \bar{A}_0$	12	13	15	14	
$A_1 A_0$	8	9	11	10	

$\bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0$ (0)
 $\bar{A}_1 A_0 \bar{B}_1 B_0$ (5)
 $A_1 \bar{A}_0 B_1 \bar{B}_0$ (14)
 $A_1 A_0 B_1 B_0$ (15)

$$\begin{aligned}
 f &= \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 B_0 \\
 &\quad + A_1 \bar{A}_0 B_1 \bar{B}_0 + A_1 A_0 B_1 B_0 \\
 &= \bar{A}_1 \bar{B}_1 (\bar{A}_0 \bar{B}_0 + A_0 B_0) \\
 &\quad + A_1 B_1 (A_0 B_0 + \bar{A}_0 \bar{B}_0)
 \end{aligned}$$

1-bit
(A $\odot$ B)
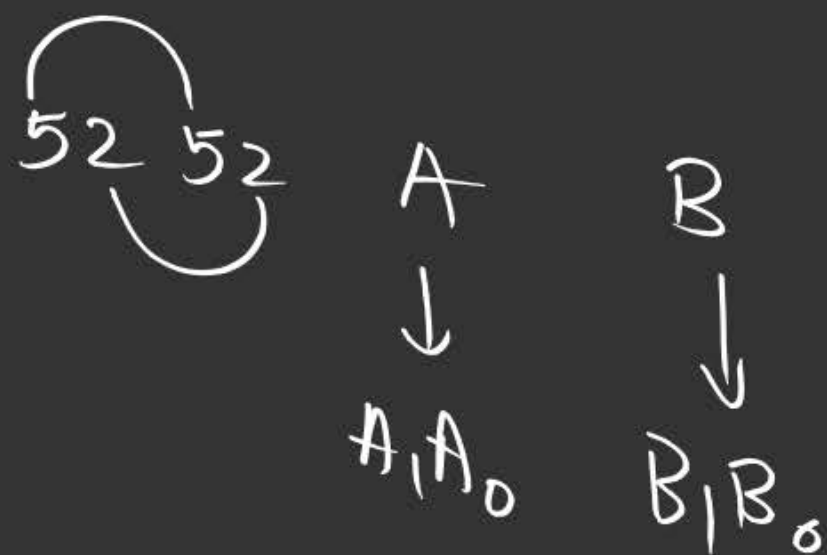
$$\begin{aligned}
 &= (A_0 B_0 + \bar{A}_0 \bar{B}_0) (A_1 B_1 + \bar{A}_1 \bar{B}_1) \\
 &= (A_0 \odot B_0) (A_1 \odot B_1) \\
 &= (A_1 \odot B_1) (A_0 \odot B_0)
 \end{aligned}$$




Summary: Semi-Minimised 80P (Imp Shortcut)

$$1) P(A > B) \Rightarrow A_1 \bar{B}_1 + (A_1 \odot B_1) \cdot A_0 \bar{B}_0$$

↓
2 bit

$$2) P(A > B) \Rightarrow A \bar{B}$$

for 1-bit

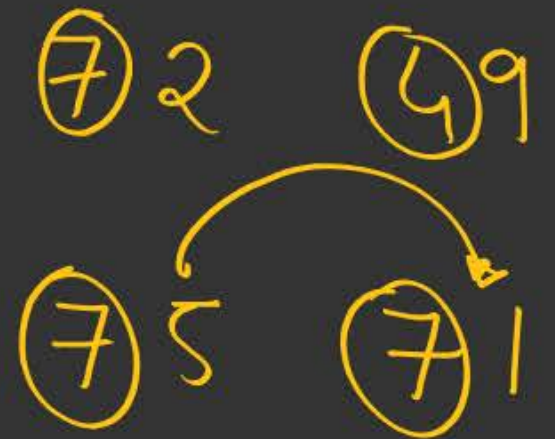

$$2) \Phi(B > A) \Rightarrow \bar{A}_1 B_1 + (A_1 \odot B_1) \cdot \bar{A}_0 \cdot B_0$$

2-bit Comp.

$$2) \Phi(B > A)$$

1-bit


$$\Rightarrow \bar{A} \cdot B$$

A
↓
A₁A₀

B
↓
B₁B₀

A	B
<u>4</u> 5	<u>6</u> 3
(4)5	(4)9

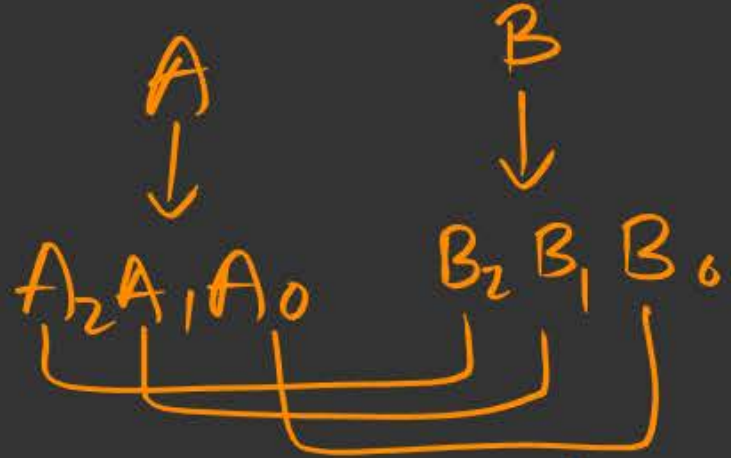eg:- Shortcut to directly write 3-bit Comparator




$$1) P(A > B) \Rightarrow A_2 \cdot \overline{B_2} + (A_2 \odot B_2) \cdot A_1 \overline{B_1} + (A_2 \odot B_2) \cdot (A_1 \odot B_1) \cdot A_0 \overline{B_0}$$

$$2) Q(B > A) \Rightarrow \overline{A_2} B_2 + (A_2 \odot B_2) \cdot \overline{A_1} B_1 + (A_2 \odot B_2) (A_1 \odot B_1) \cdot \overline{A_0} B_0$$


$$3) R(A = B) \Rightarrow (A_2 \odot B_2) (A_1 \odot B_1) (A_0 \odot B_0)$$

✓ Step 5: Hardware design:

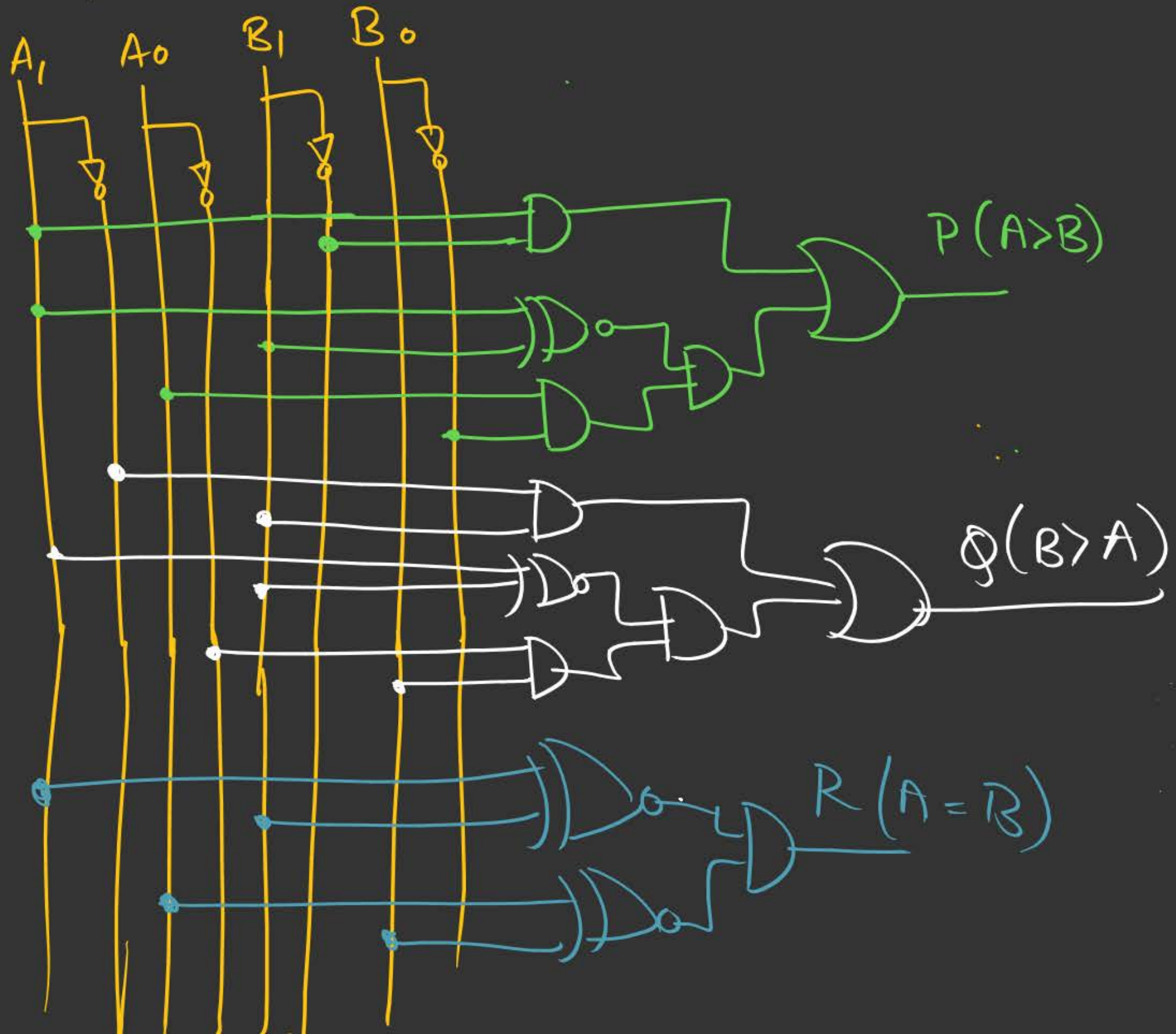

Properties/Observation (Comparators)

1) 1-bit Comparator :

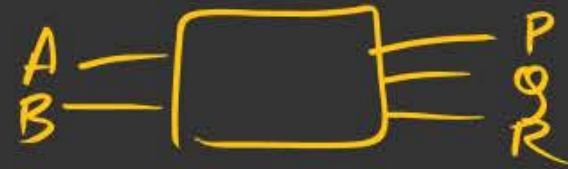


→ Total Combinations/Condition = 4

→ Equal Combinations = 2
(R=1)

→ Unequal Combinations = $(4-2)=2$
(R=0)

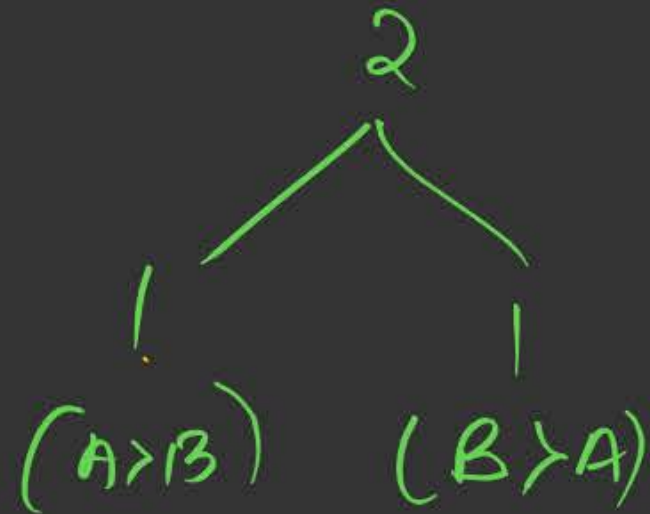→ # Greater Combith = # lesser Combith = 1



2) 2-bit Comparator :-




→ Total Combi = 16

→ Equal Combi = 4

→ Unequal " = $(16 - 4) = 12$

→ # greater = # lesser = 6

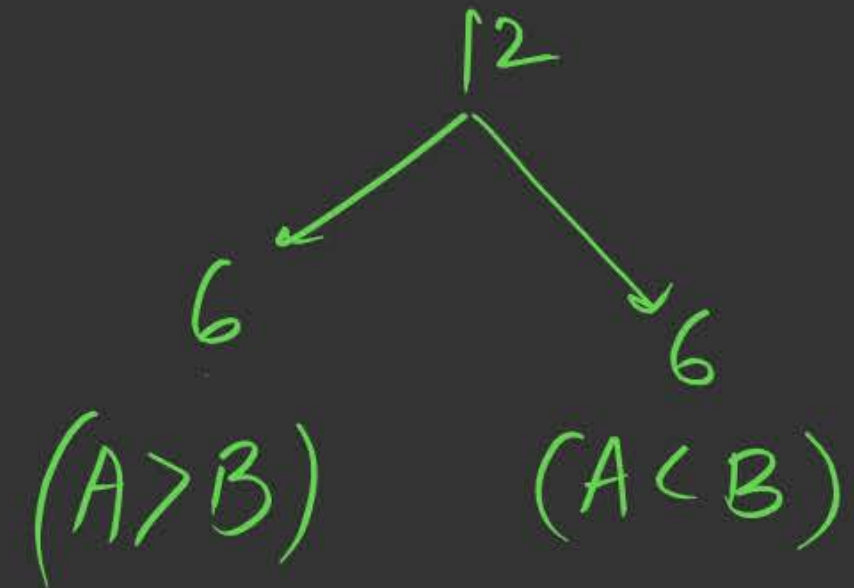

3) 3-bit Comparator

$$2^6 = \underline{64}$$






$$\rightarrow \text{Total Combi} = 64$$

$$\rightarrow \text{Equal Combi} = 8$$

$$\rightarrow \text{Unequal Combi} = (64 - 8) = 56$$
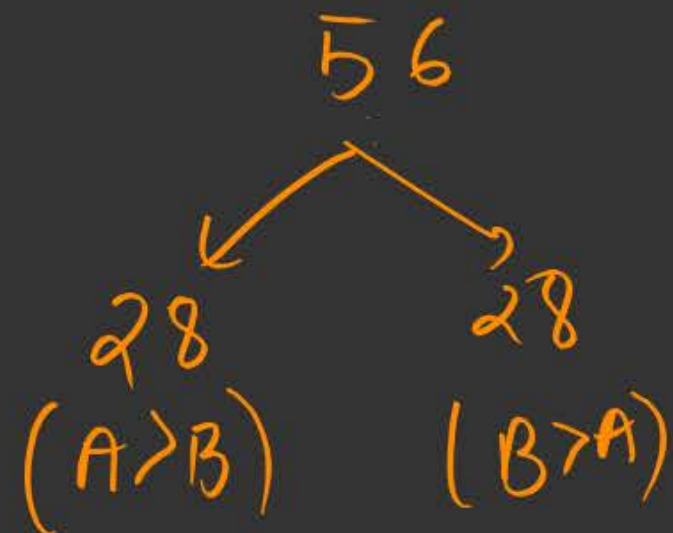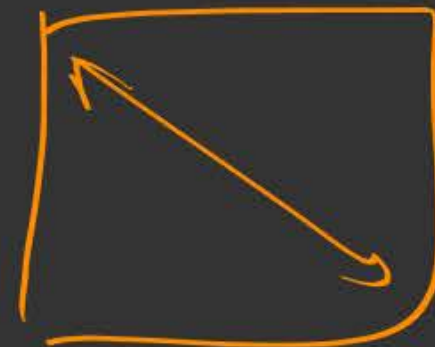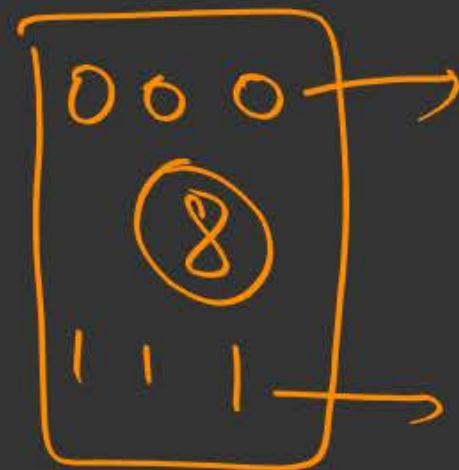
$$\rightarrow \# \text{ greater} = \# \text{ lesser} = \frac{56}{2} = 28$$



Generalised (V.V. Imp shortcut)

n-bit Comparator

4 16 64

- 1) Total conditions/Combinations = $2^{(2n)}$
- 2) Equal Combi = 2^n
- 3) Unequal Combi = $(2^{(2n)} - 2^n)$
- 4) $\# \text{ Greater} = \# \text{ lesser Combi} = \frac{(2^{2n} - 2^n)}{2}$

12, 13 → No digital logic class

→ DPP-2 → Solve

→ Produce entire K-map (2 times)

→ Solve PYQs on Ch-1 & Ch-2
content.



2 mins Summary



→ Comparator

(1-bit
2-bit
3-bit)

obs

→ Expression logic
(Shortcut)



THANK - YOU