

CS & IT ENGINEERING



Digital Logic

Combinational Circuits

Lecture No. 03



By- Aditya sir

Recap of Previous Lecture



Topic



n-bit Comparators

Generalised

Topics to be Covered



Topic




Multiplexors


(Mux)

Multiplexer (mux)


↳ Multi i/p $\xrightarrow{\text{to}}$ One o/p

Select lines

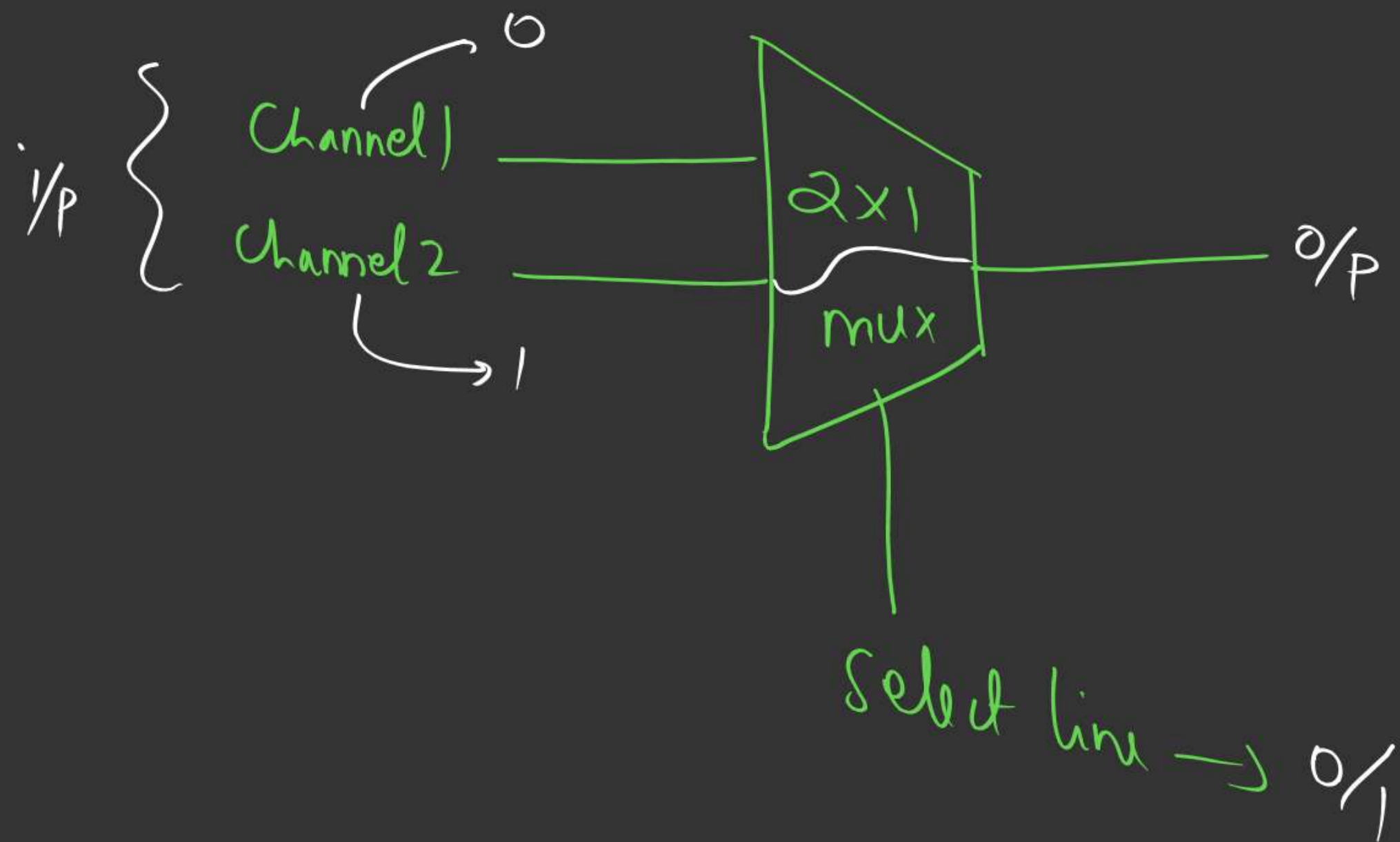

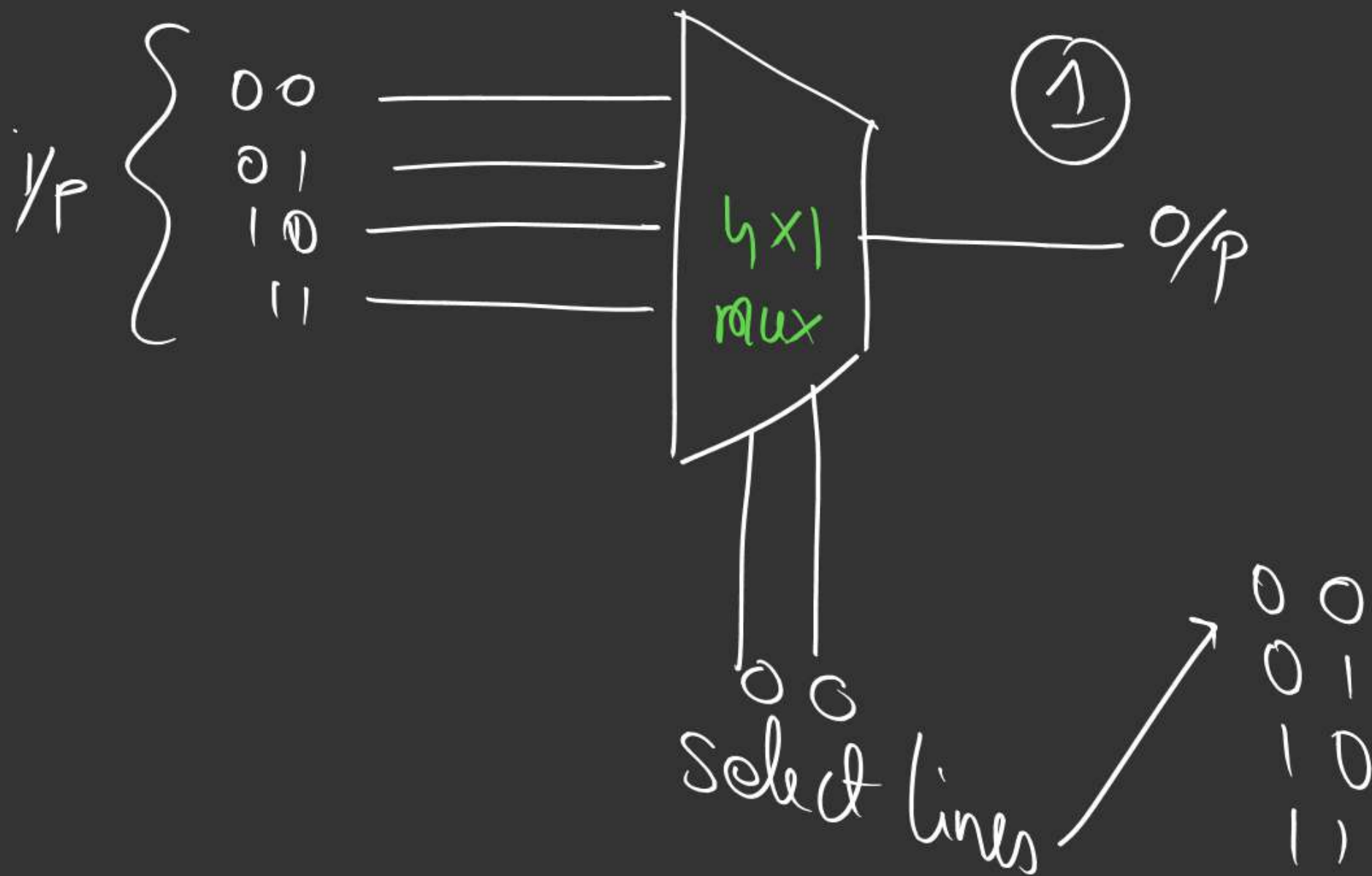

Mux (in general)

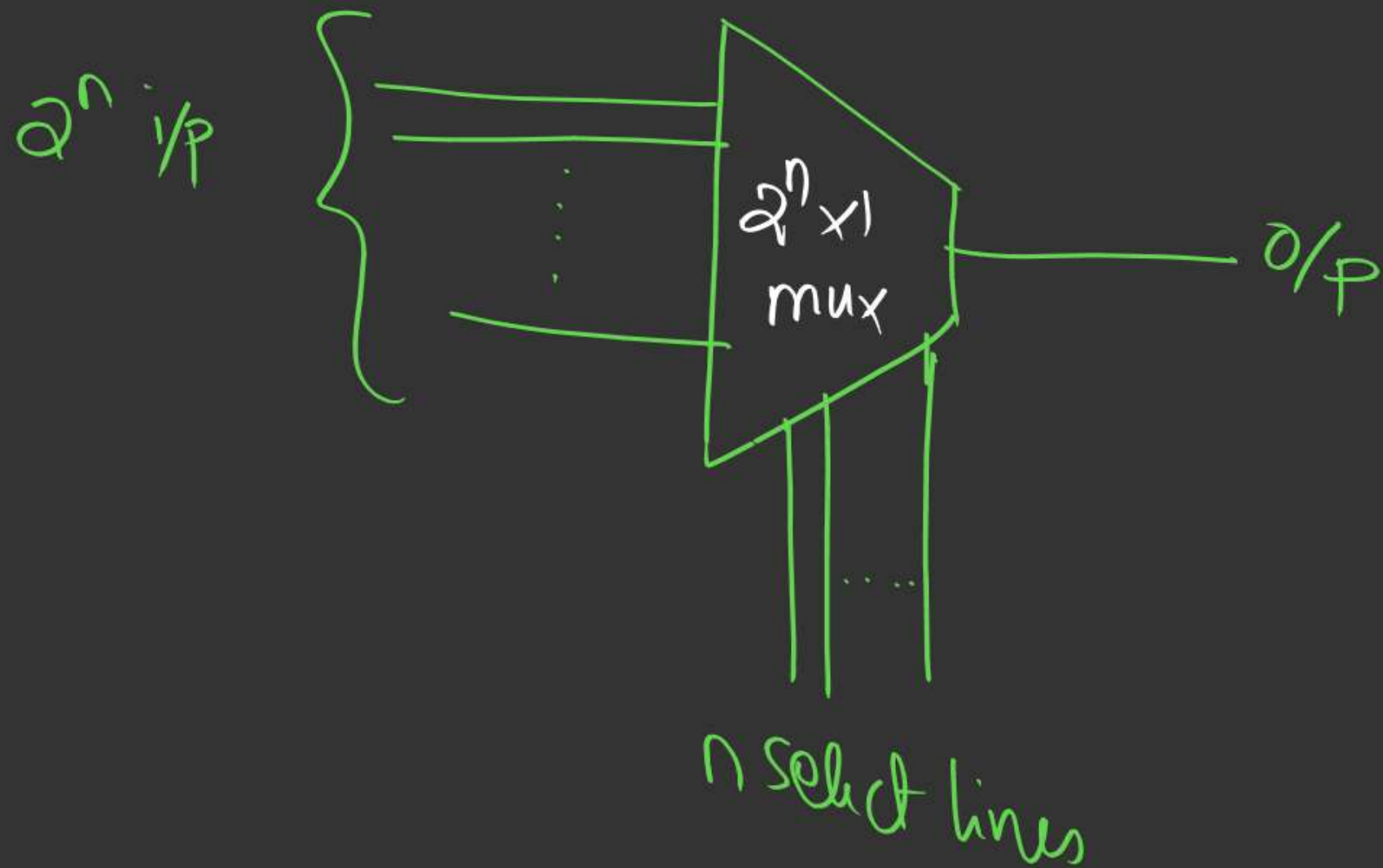


$2^n \times 1$ mux

→ 2^n to 1 Converter.

→ Universal Logic

→ AND-OR

⇒ 2x1 mux

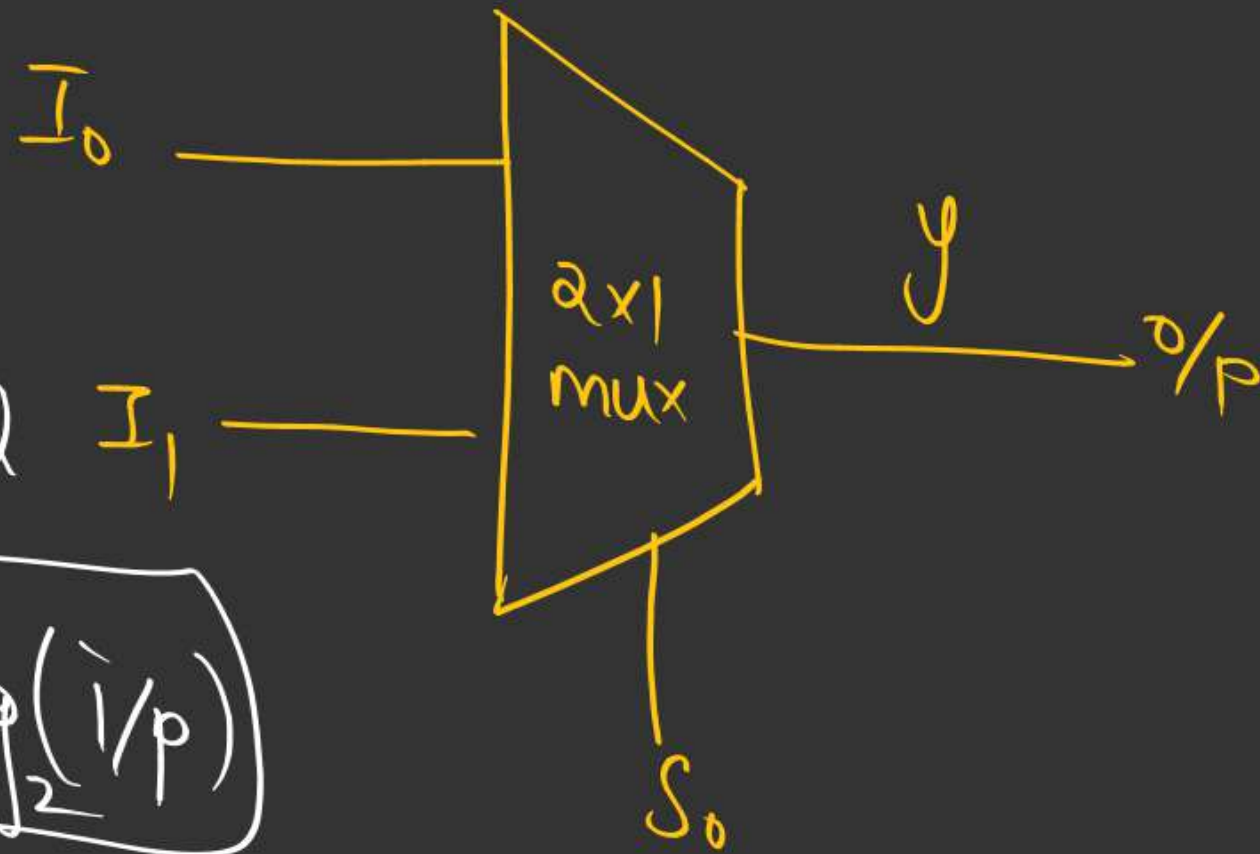

In general

$$S_L = \log_2(i/p)$$

Step 1: $\frac{2^{i/p}}{1^{o/p}}$
→ 1 select line

Step 2:- Truth Table:-

S_0	y
0	I_0
1	I_1

Step 3:- Logical Expression:

$$S_0 = 0 \rightarrow \text{or } I_0$$

$$S_0 = 1 \rightarrow I_1$$


$$y = \overline{S_0} \cdot I_0 + S_0 \cdot I_1$$

Step 4:- Minimize Expression



$$y = \bar{S}_0 I_0 + S_0 I_1$$

Step 5:- Draw logical Diagram/Hardware.

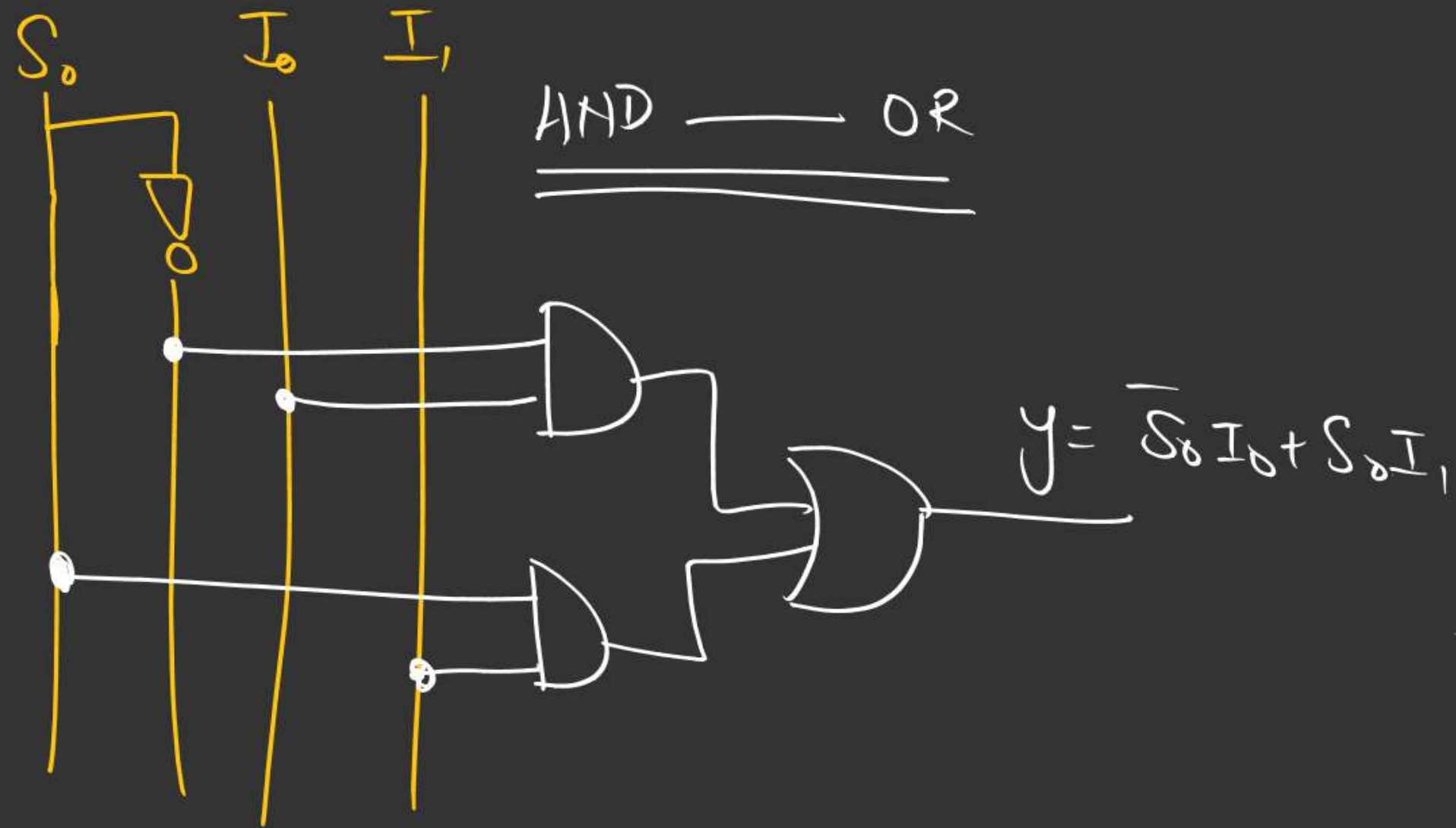

② 4x1 mux

Step 1 : 4 i/p (I_0, I_1, I_2, I_3), 1 o/p

Select lines = 2


Step 2:- Tenth table

$\overrightarrow{S_2, S_1, S_0}$

S_1	S_0	y
0	0	H_0
0	1	H_1
1	0	H_2
1	1	H_3

Step 3:- Logical Expression:-
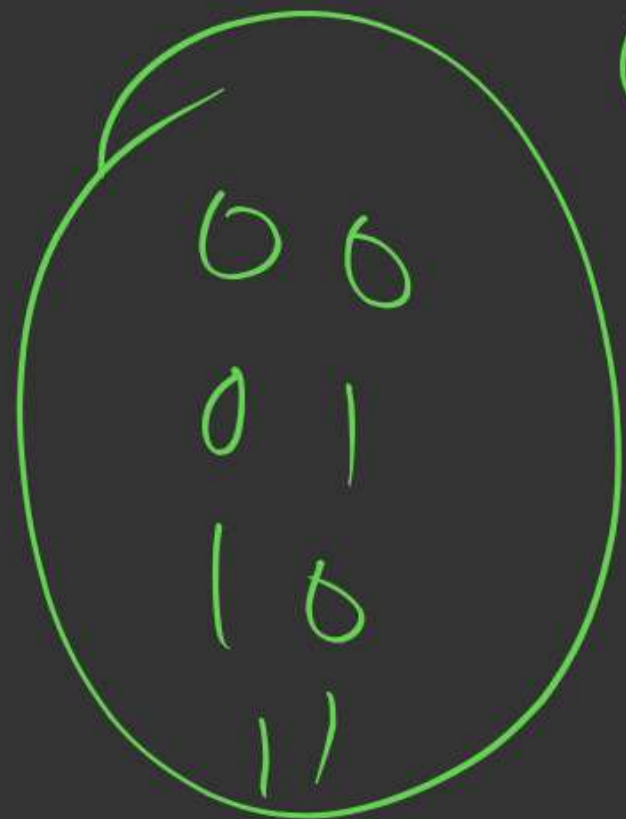
$$y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$





0	0
0	1
1	0
1	1

Step 4: minimized Expression

$$\left[y = \overline{S}_1 \overline{S}_0 I_0 + \overline{S}_1 S_0 I_1 + S_1 \overline{S}_0 I_2 + S_1 S_0 I_3 \right]$$

Step 5:- Hardware/Diagram

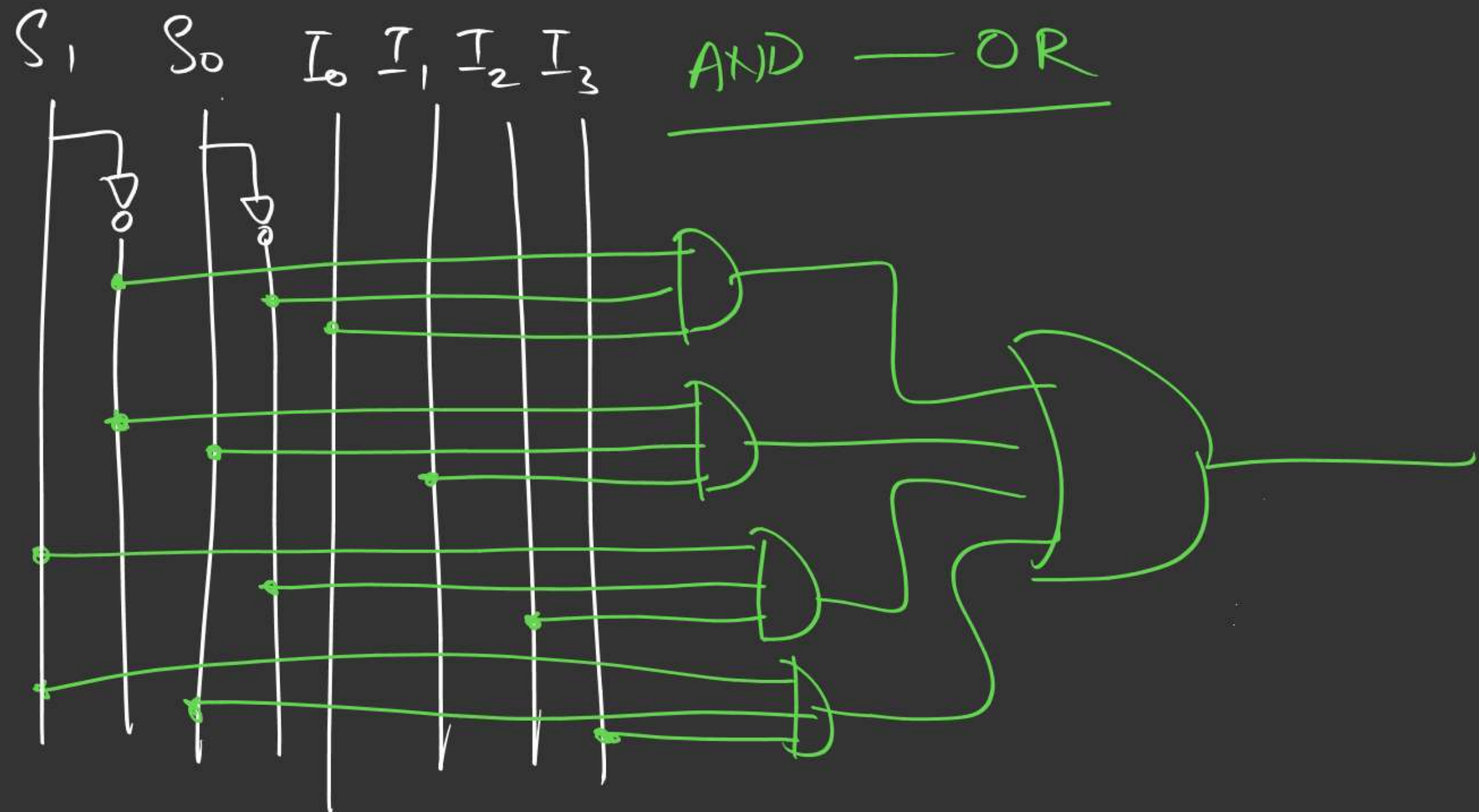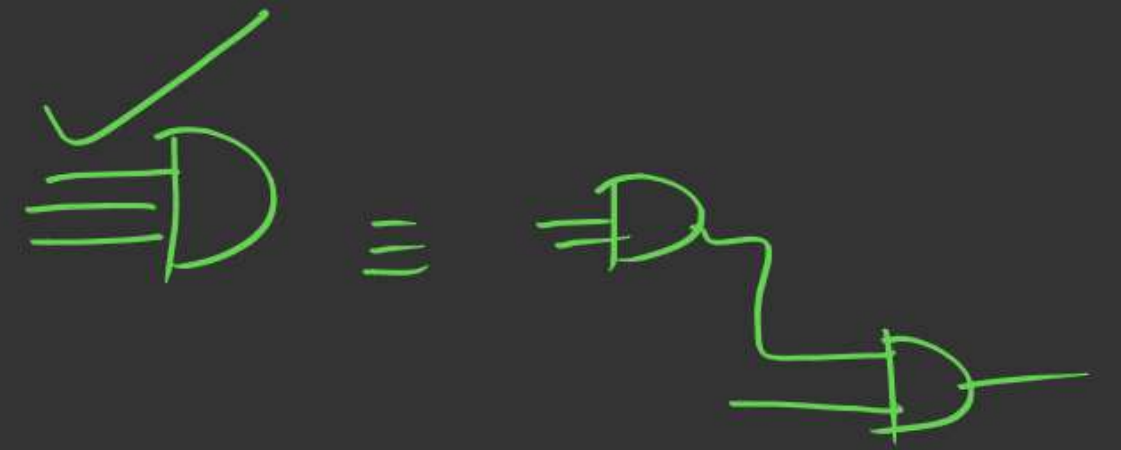

h.w

1> Design

8x1 mux

(5 steps)

2> "

16x1 mux

(5 steps)

Type 1

↳ Create/design a Higher order mux
by using smaller order mux



(Q1) How many 2x1 mux needed to design
a 4x1 mux?


(Q2) Design Structure?

eg:-

Design a 4x1 mux using 2x1 mux(s)


4 i/p

2 i/ps

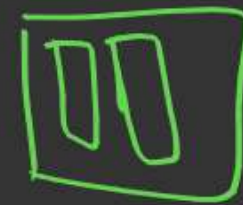

(Q) How many 2x1 mux $\rightarrow$ 4x1 mux.

explanation

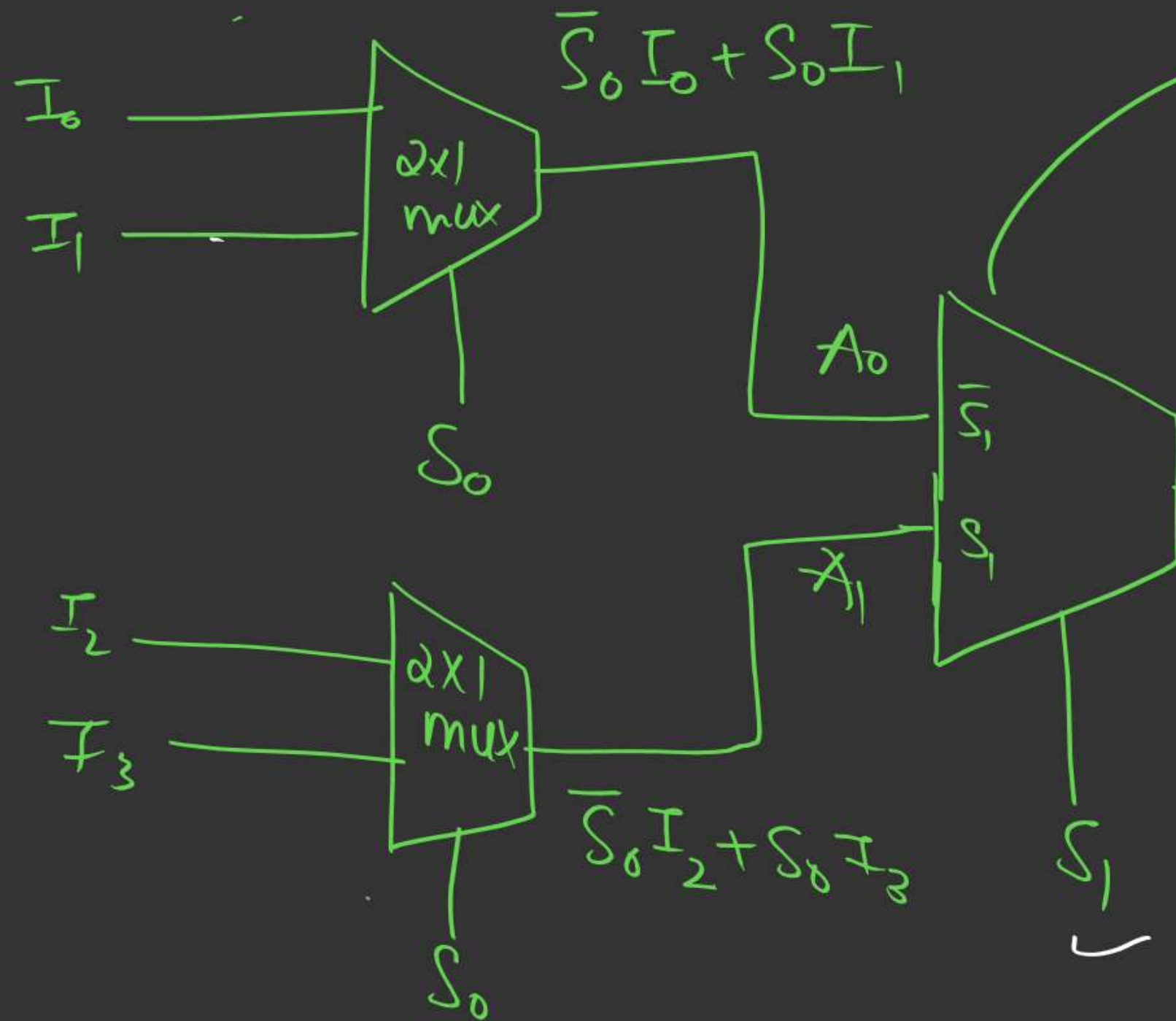

$$(\bar{S}_1 A_0 + S_1 A_1)$$

$$\bar{S}_1 (\bar{S}_0 I_0 + S_0 I_1) + S_1 (\bar{S}_0 I_2 + S_0 I_3)$$

$$= [\bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + \bar{S}_1 \bar{S}_0 I_2 + S_1 S_0 I_3]$$

3 2x1 mux used

Ans:- Shortcut (to solve this)

✓ 4x1
2x1

$$\frac{4}{2} = 2$$


$$\frac{2}{2} = 1$$

keep dividing by
smaller max size
until reach ≤ 1 .

$$\text{Total} = \frac{4}{2} + \frac{2}{2} = 2 + 1 = 3 \quad (\underline{2 \times 1 \text{ max}})$$

(Q.2) How many 2×1 mux $\longrightarrow$ 8×1 mux?

$\hookrightarrow$ Outline of Design

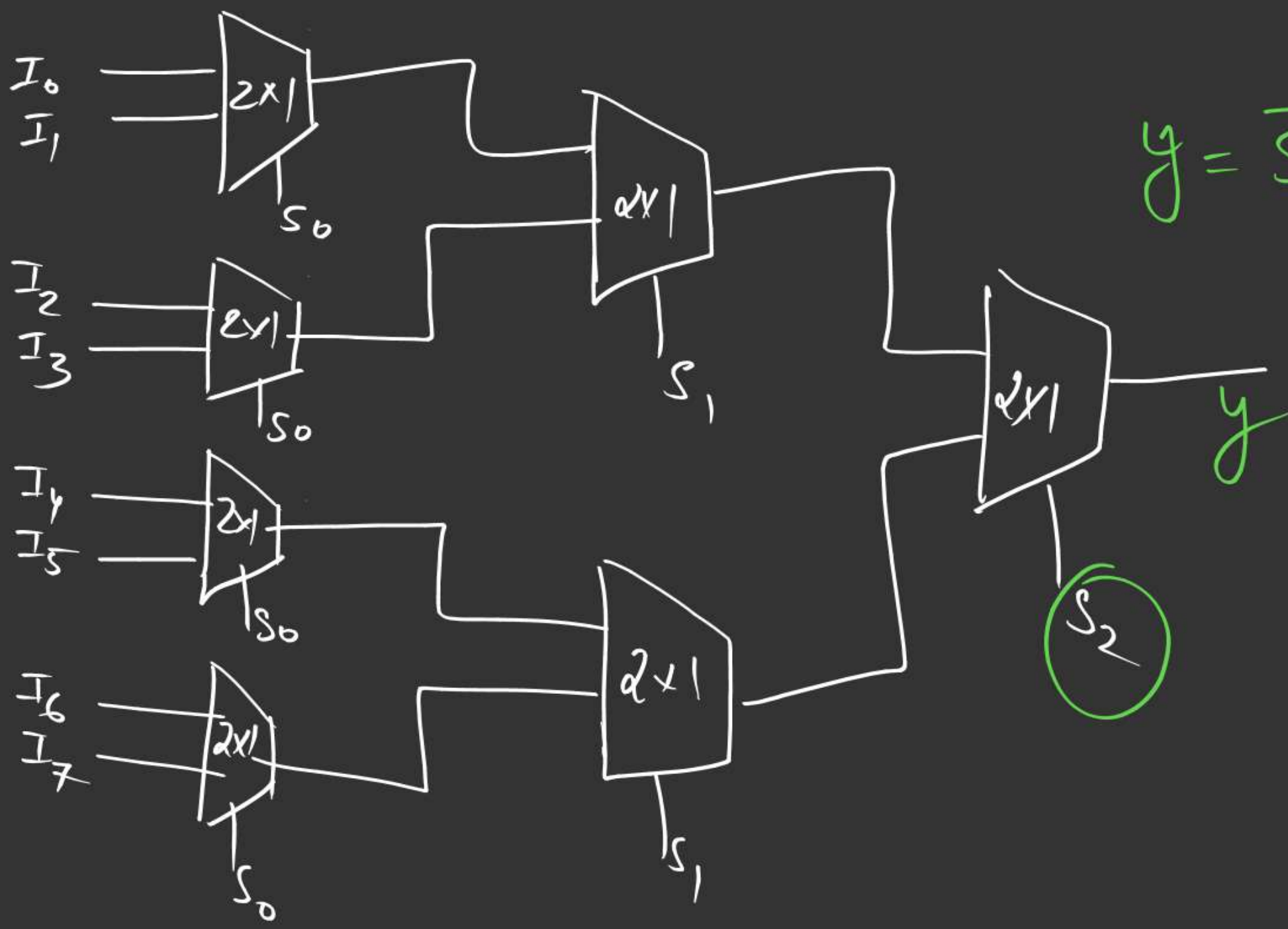


$$y = \overline{S_2} (\quad) + S_2 (\quad)$$

Ans (7)

ShortCut

841

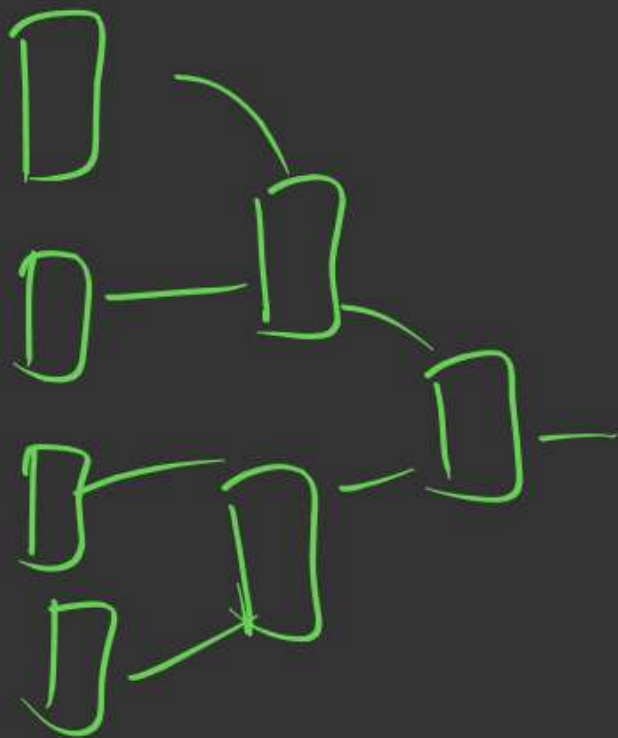

$$\frac{8}{2} = 4$$

$$\frac{4}{2} = 2$$

$$\frac{2}{2} = 1$$

$$\frac{4}{2} = 2$$

$$\frac{Q}{2} = 1$$

2x1

$$\text{Total } 2 \times 1 \text{ mmx} = 4 + 2 + 1 = 7$$

Apply Shortcut

- 1) How many $2 \times 1 \longrightarrow 16 \times 1$?
- 2) " $2 \times 1 \longrightarrow 64 \times 1$?

Property :

How many 2×1 mux needed to
design a $2^n \times 1$ mux ?



Ans: $(2^n - 1)$

4×1	$\rightarrow$	3
8×1	$\rightarrow$	7
16×1	$\rightarrow$	15
64×1	$\rightarrow$	63

(8) How many 4×1 mux
needed to design a 16×1 mux?

Shortcut : $(16) \times 1$ using $(4) \times 1$

$$\frac{16}{4} = 4$$

$$\frac{4}{4} = 1$$

$$\begin{aligned} \text{Total} &= 4 + 1 \\ &= 5 \quad (4 \times 1 \text{ max}) \end{aligned}$$

Q2:-

Design $64 \times 1 \longrightarrow$ using 4×1 _{max}.

$16 \rightarrow 4 \rightarrow 1$

$$\frac{64}{4} = 16$$

$$\frac{16}{4} = 4$$

$$\frac{4}{4} = 1$$

$$\text{Total} \Rightarrow 16 + 4 + 1$$

$$= \underline{\underline{21}}$$

Special Cases


(Shortcut still works)

eg3)

Design 32×1 using 4×1 mux?

How many?

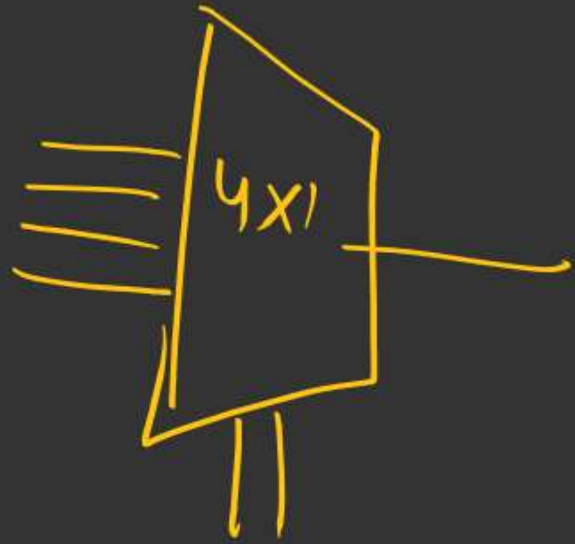$(32)_{10} \longrightarrow$ using $(4)_{10}$



$$\frac{32}{4} = 8$$

$$\frac{8}{4} = 2$$

$$\frac{2}{4} \leq 1 \quad \checkmark \text{ Stop}$$

$$\text{Total} = 8 + 2 + 1 = (11)$$



How:

How many 8×1 mux
needed for
 64×1 ?

→ Think of internal working as well



2 mins Summary



→ MUX

→ Intro
→ Examples



THANK - YOU

