

CS & IT ENGINEERING



Digital Logic

Combinational Circuits

Lecture No. 9



By- Aditya sir



Recap of Previous Lecture



Topic



Decoder
Questions

Topics to be Covered



Topic

Combinational Circuits

└ Adder, Subtractor
 ↓
 Half,
 full
 ↓
 Half
 Full



HA	HS	→ 2 bits i/p
FA	FS	→ 3 bits i/p




Topic : Half Adder

Half Adder

0	0	1	1
+0	+1	0	1
<u>00</u>	<u>01</u>	<u>01</u>	<u>10</u>


- Two bit adder are known as half adder.

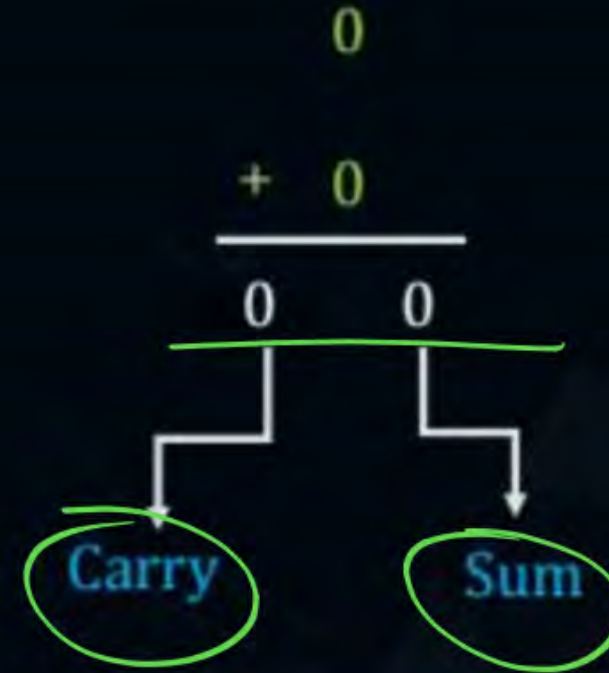



Topic : Half Adder

Step-1

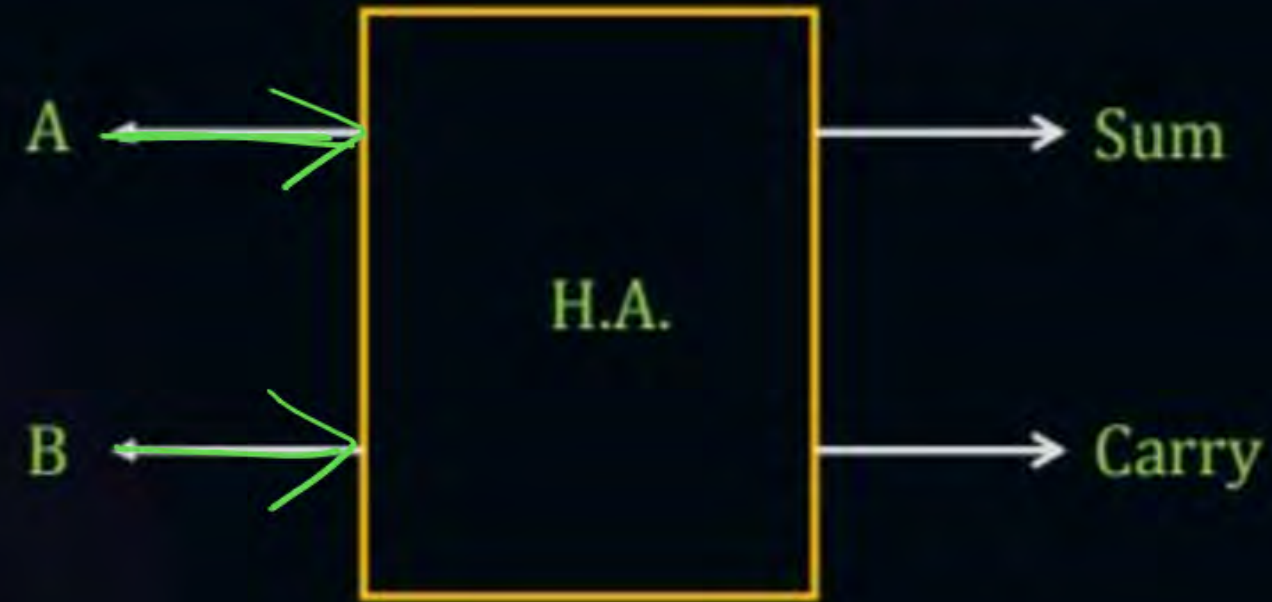

2⁰/p

2⁰/p → 1) Sum
 → 2) Carry



Topic : Half Adder

Step-2

Truth Table

A	B	Sum	Carry
0	0	0	0
0 →	1	1	0
← 1	0	1	0
1	1	0	1



Topic : Half Adder

Step-3

$$\text{Sum} = \bar{A}B + A\bar{B} = \underline{\underline{A \oplus B}}$$

$$\text{Carry} = \underline{\underline{AB}}$$

Step-4

Minimization

No, already done



Topic : Half Adder






Topic : Half Adder



Step-5

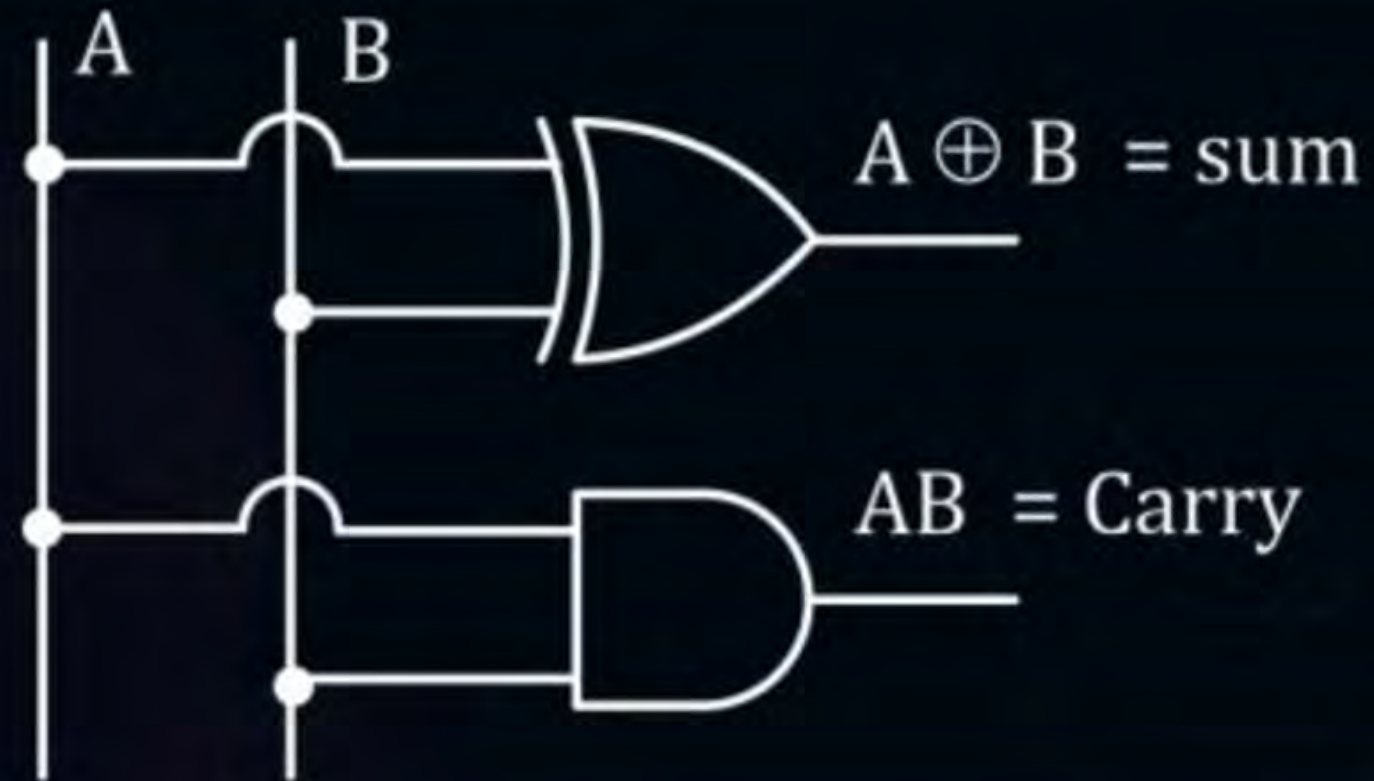

min NAND

for H.A ?

Misconception

Min no. of NAND
for H.A

$\Rightarrow$ H.A $\Rightarrow$

XOR $\rightarrow$ 4 NAND

+

AND

$\rightarrow$ 2 NAND


$\rightarrow 4+2 = 6$

$\downarrow$
(wrong)



Topic : Half Adder

HA
BY NAND GATE

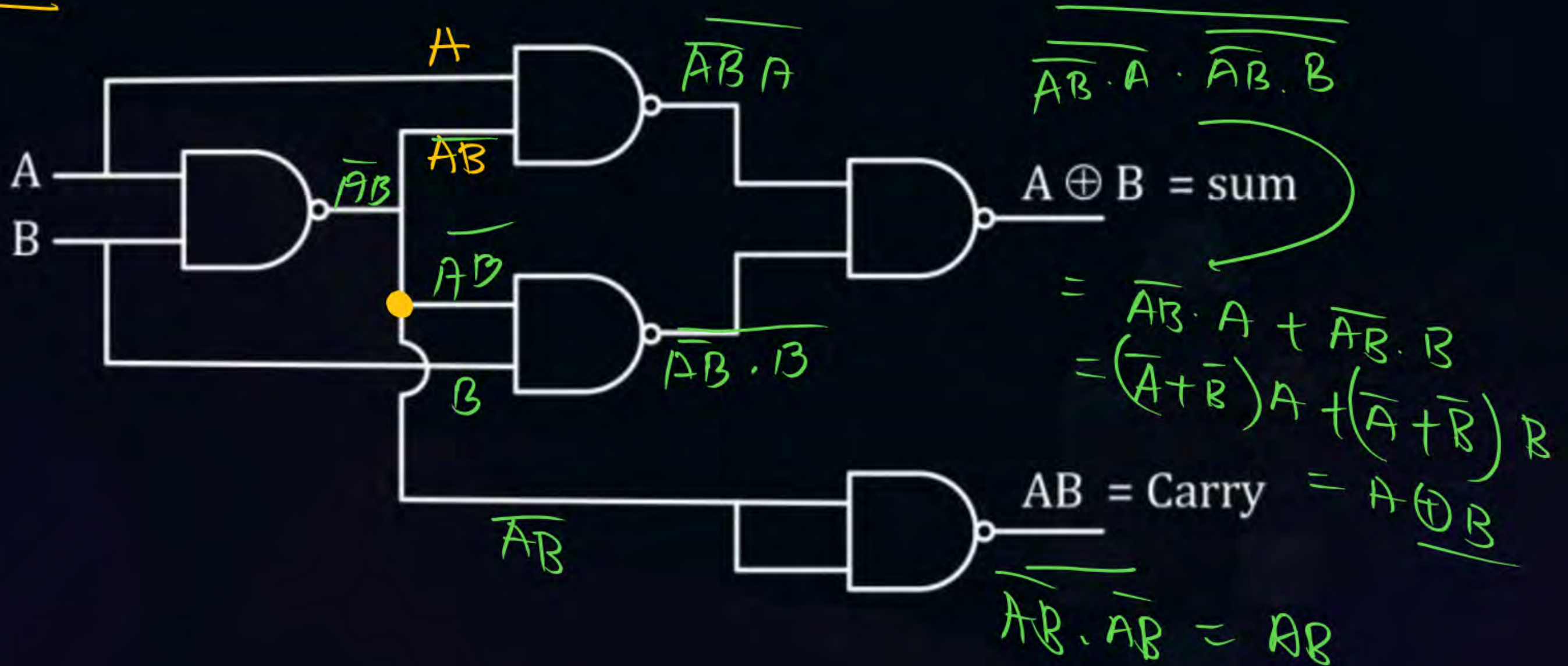




Topic : Half Adder

By NOR GATE


5 NOR
HA

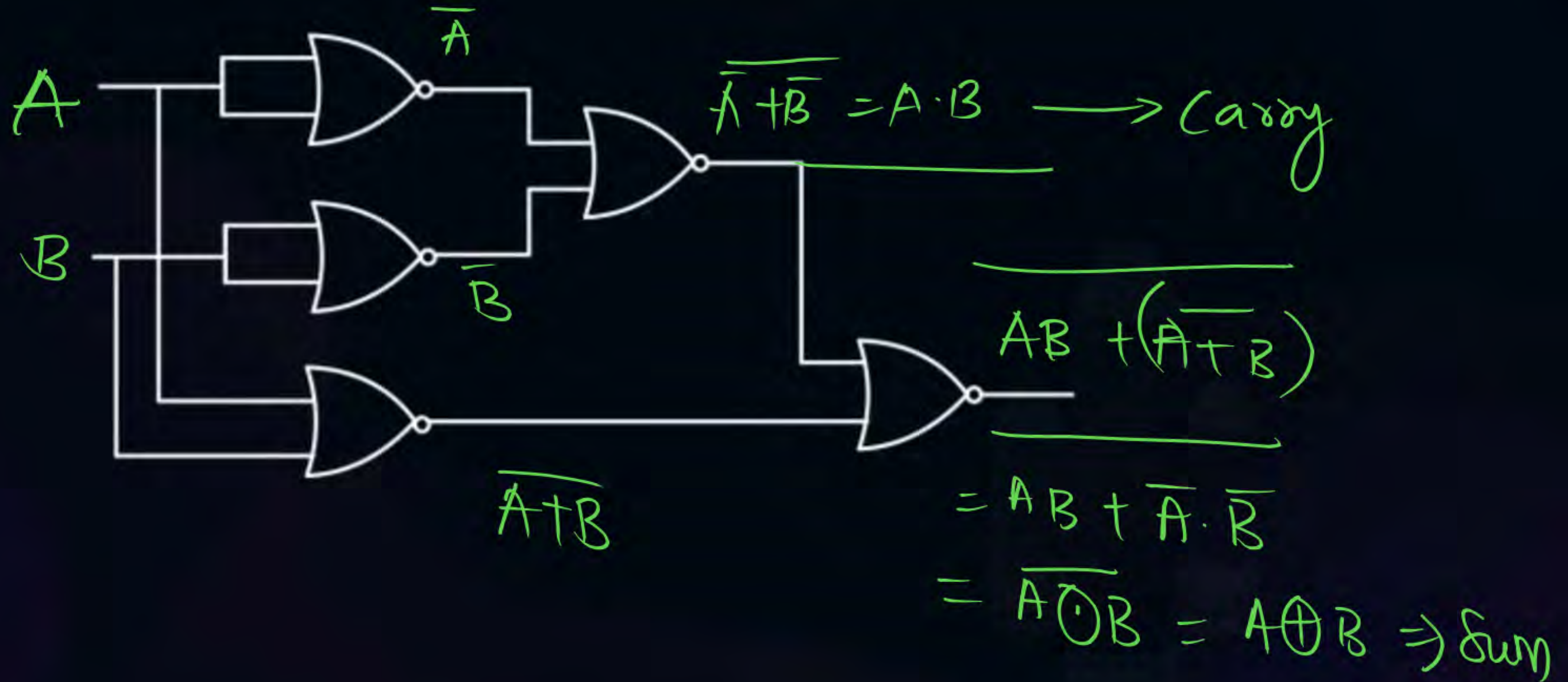


Shortcut



Anything HALF → 5

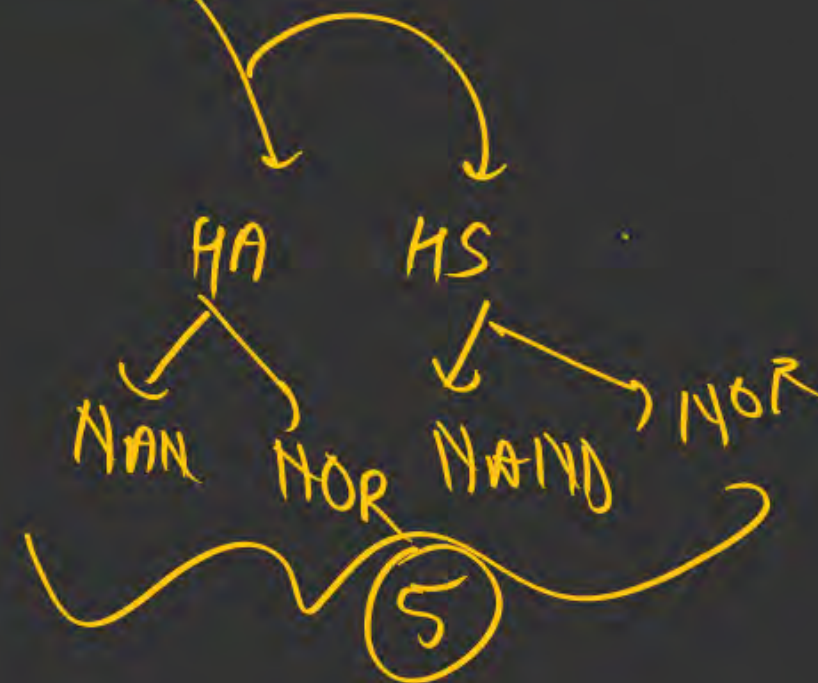

Anything FULL → 9

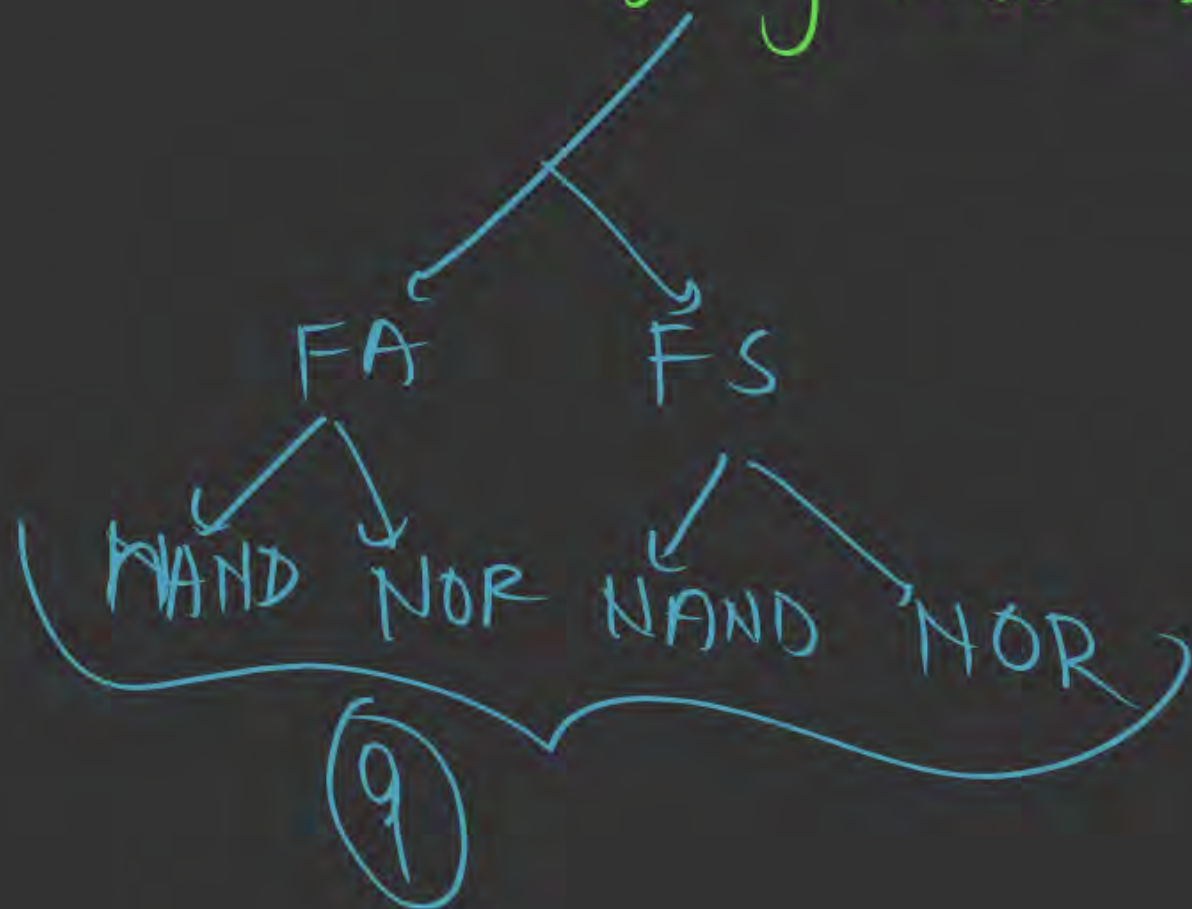




Topic : Half Adder


2x4

Half adder by using Decoder

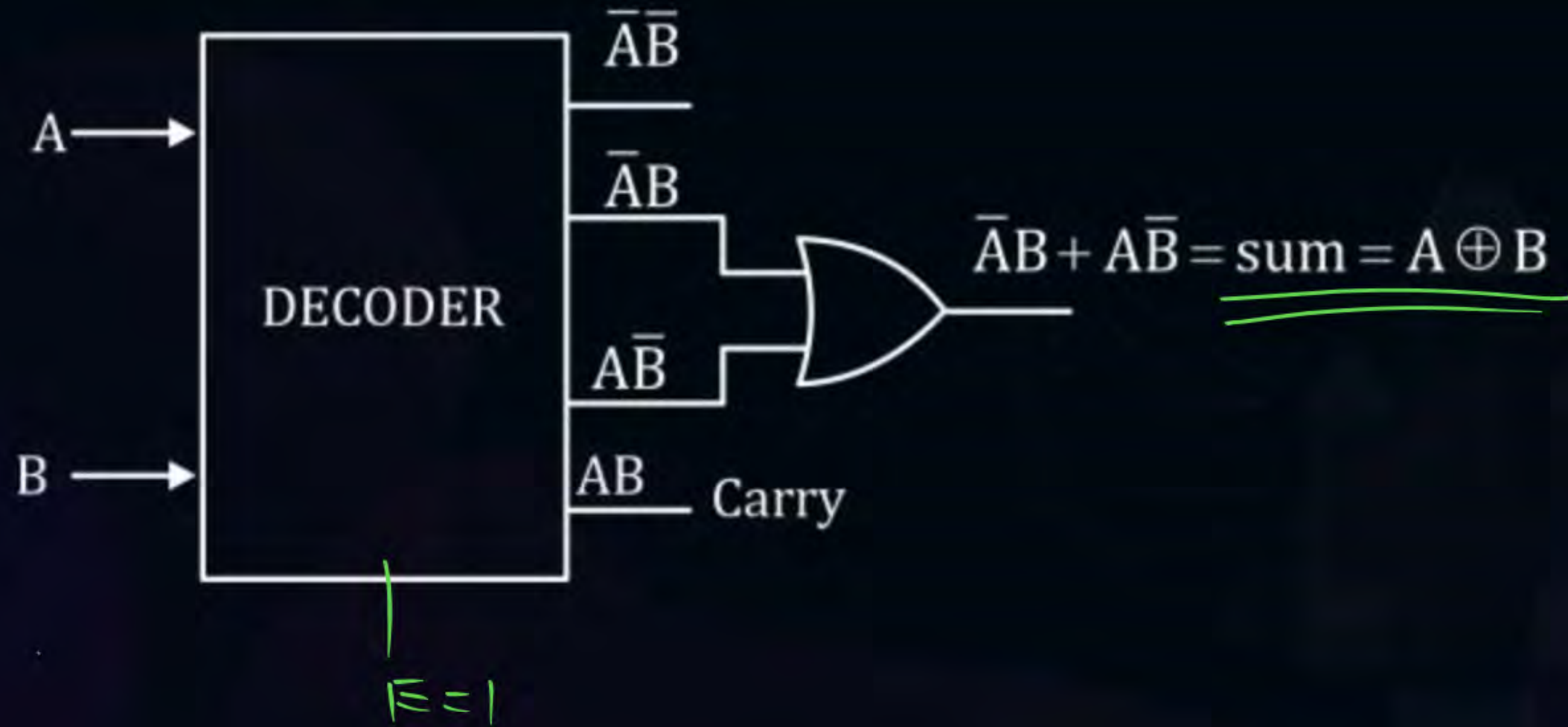

[NAT]

#Q. What is the value of f_1 and f_2 ?

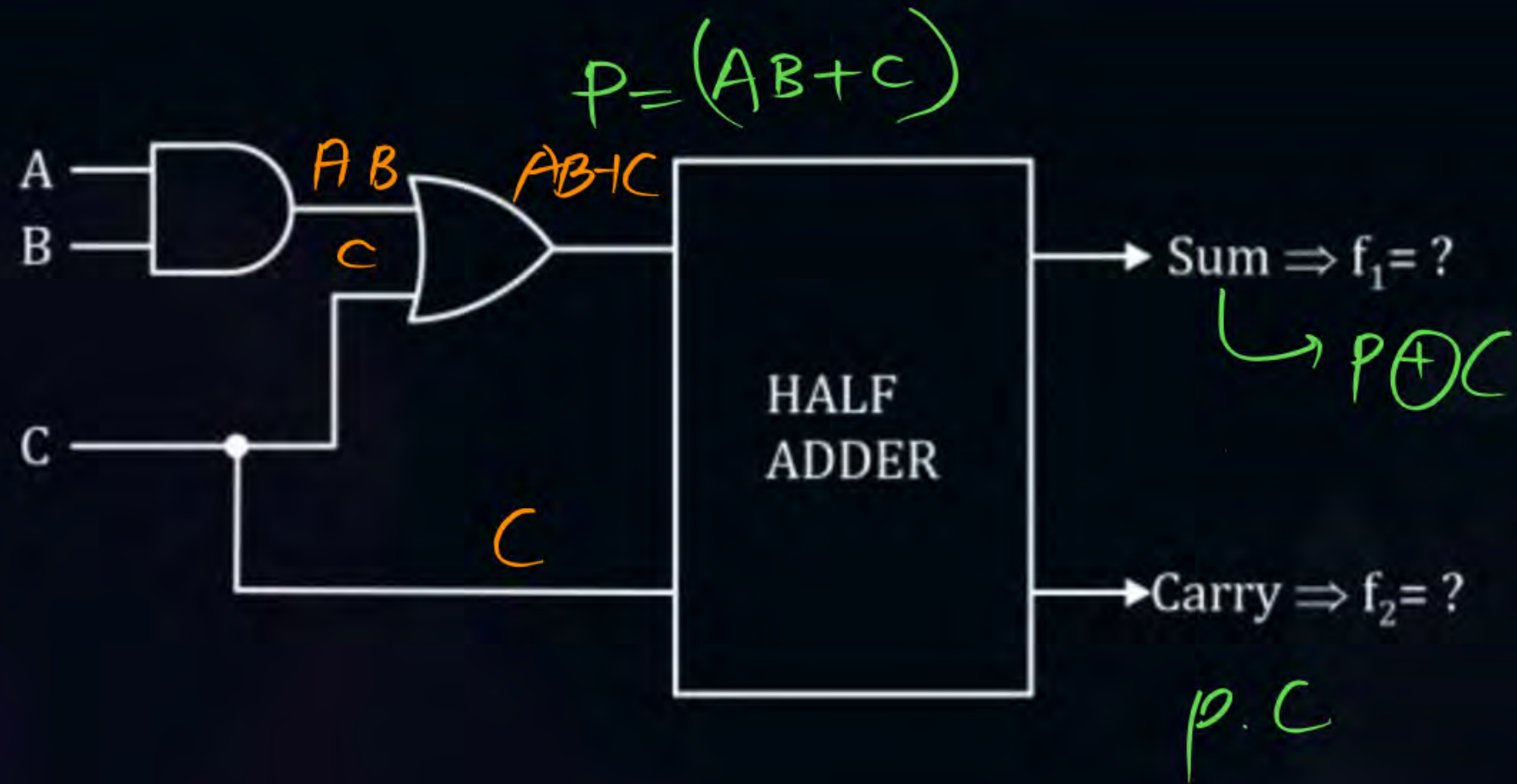

Ans
on Telegram



Topic : Full Adder

Three ~~bit~~ adder are known as full adder.

bits

0	0	0	1
0	0	1	1
+0	+1	+1	+1
<u>00</u>	<u>01</u>	<u>10</u>	<u>11</u>

Carry Sum

$$\begin{array}{r} 0 \\ 1 \\ + 0 \\ \hline 01 \\ \hline \end{array}$$



Topic : Full Adder



Step-1

$V_p \rightarrow 3$

$Q_p \rightarrow 2$





Topic : Full Adder



Step-2

0
1
2
3
4
5
6
7

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

V. Imp Obs : Carry = 1, when 2 or more i/p's are 1
out of 3 i/p's.

$\left. \begin{matrix} 2/3 \text{ or } 3/3 \end{matrix} \right\}$

→ Majority High input logic

A B C

0 1 0 → 0

1 0 1 → 1

0 1 0
0 1 0



Topic : Full Adder

Step-3 $\text{Sum (A,B,C)} = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$
 $= \Sigma m(1,2,4,7)$
 $= A \oplus B \oplus C$

Step-4 $\text{Carry (A,B,C)} = \Sigma m(3,5,6,7) = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$
 $= AB + BC + AC \rightarrow \text{Minimize expression}$
 $= (\bar{A}B + A\bar{B})C + AB(\bar{C} + C)$
 $= (A \oplus B)C + AB \rightarrow \text{Semi minimized}$

	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
$\bar{A}$	0	1	3	2
A	4	5	7	6

Imp





Topic : Full Adder

Step-5

$$\text{Sum} = A \oplus B \oplus C$$

$$\text{Carry} = AB + BC + AC$$

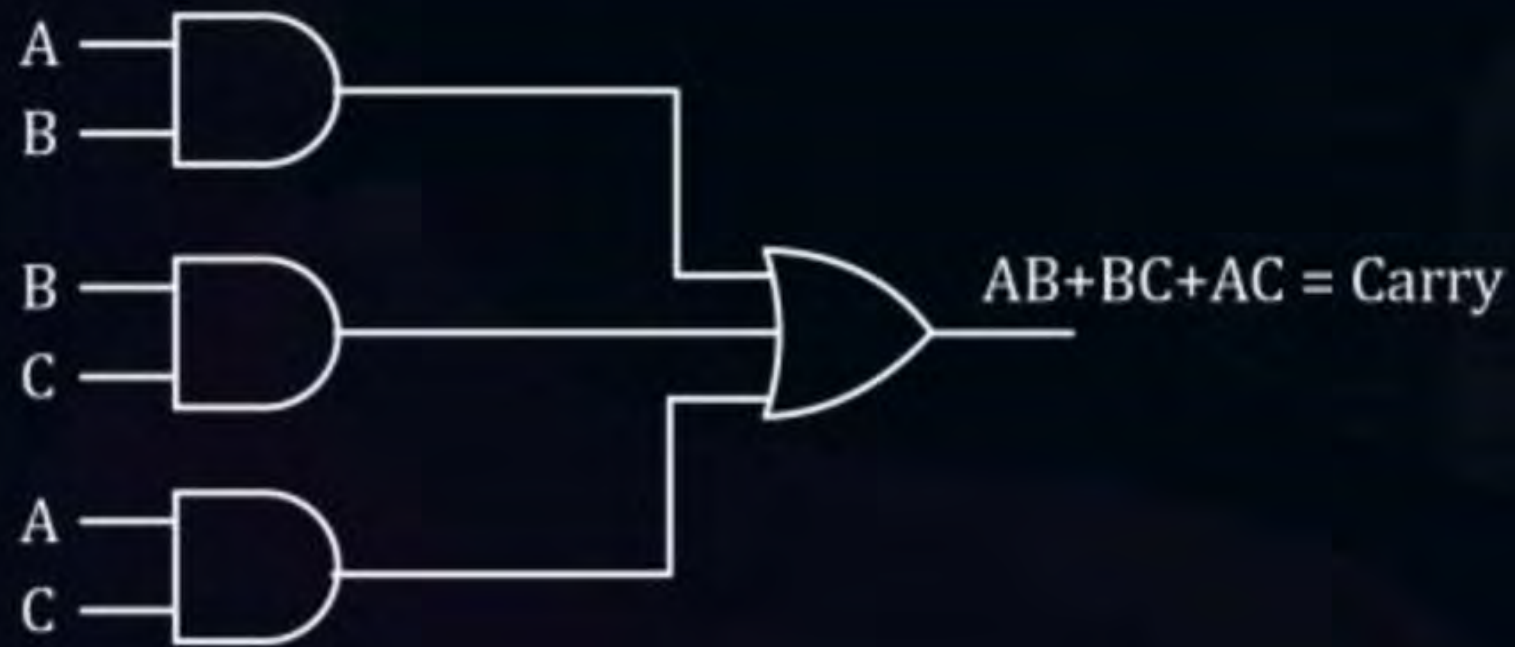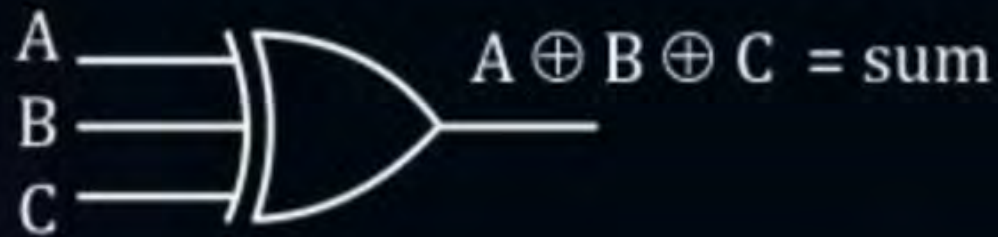

Imp eks:

$$\text{Sum} = A \oplus B \oplus C$$



$$\text{Carry} = (A \oplus B) \cdot C + AB \rightarrow \text{Semi-minimized}$$



Topic : Full Adder

$$\text{Sum} = (A \oplus B) \oplus C$$


$$\text{Carry} = (A \oplus B)C + AB$$

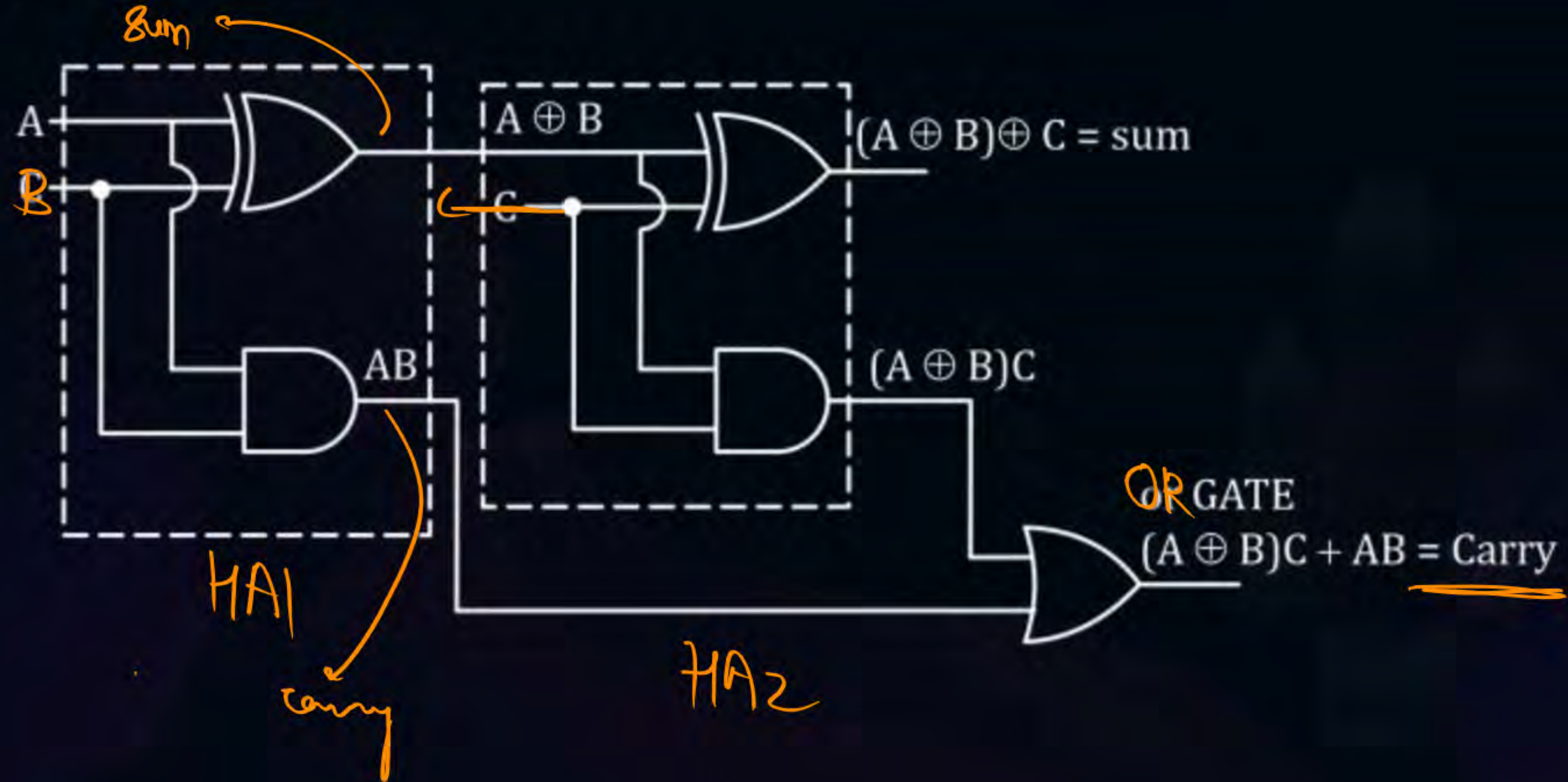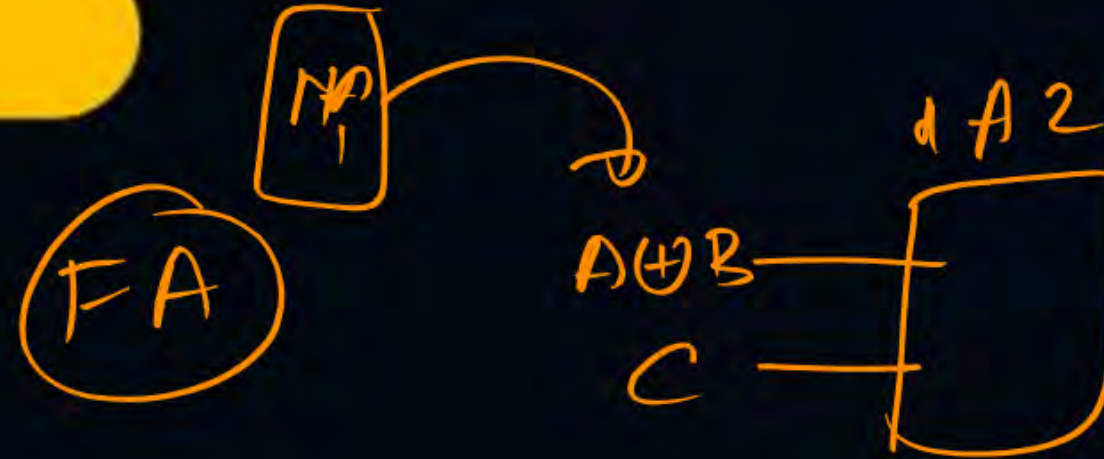



Topic : Full Adder

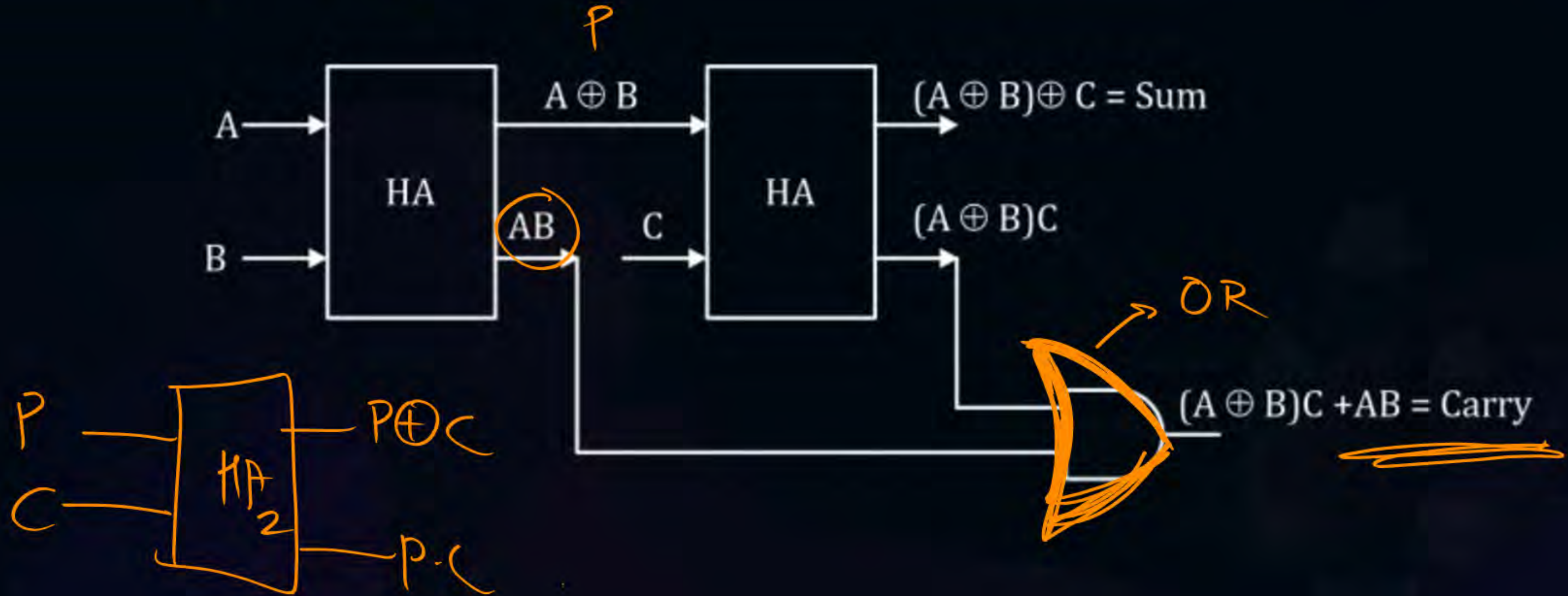Simplified Rep^r $\Rightarrow$ FA using HA




$$\left\{ \begin{array}{l} \text{Full Adder} = 2 \text{ Half Adder} \\ + \\ 1 \text{ OR Gate} \end{array} \right\}$$



Topic : Full Adder

Full adder by using NAND GATE

9 NAND

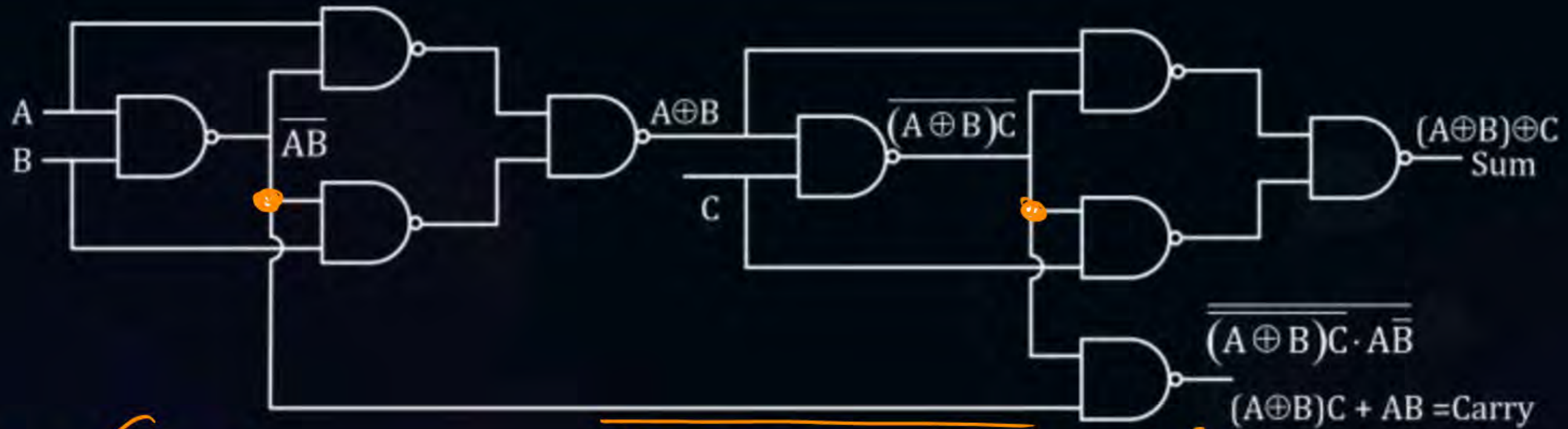

$$\text{Carry} = (A \oplus B) \cdot C + AB$$

$$(A \oplus B) \cdot C \cdot \overline{AB}$$

[NAT]


#Q. Full order by using NOR GATE

H.W 😊 → ⑨



Topic : Full Adder

Full adder by using decoder

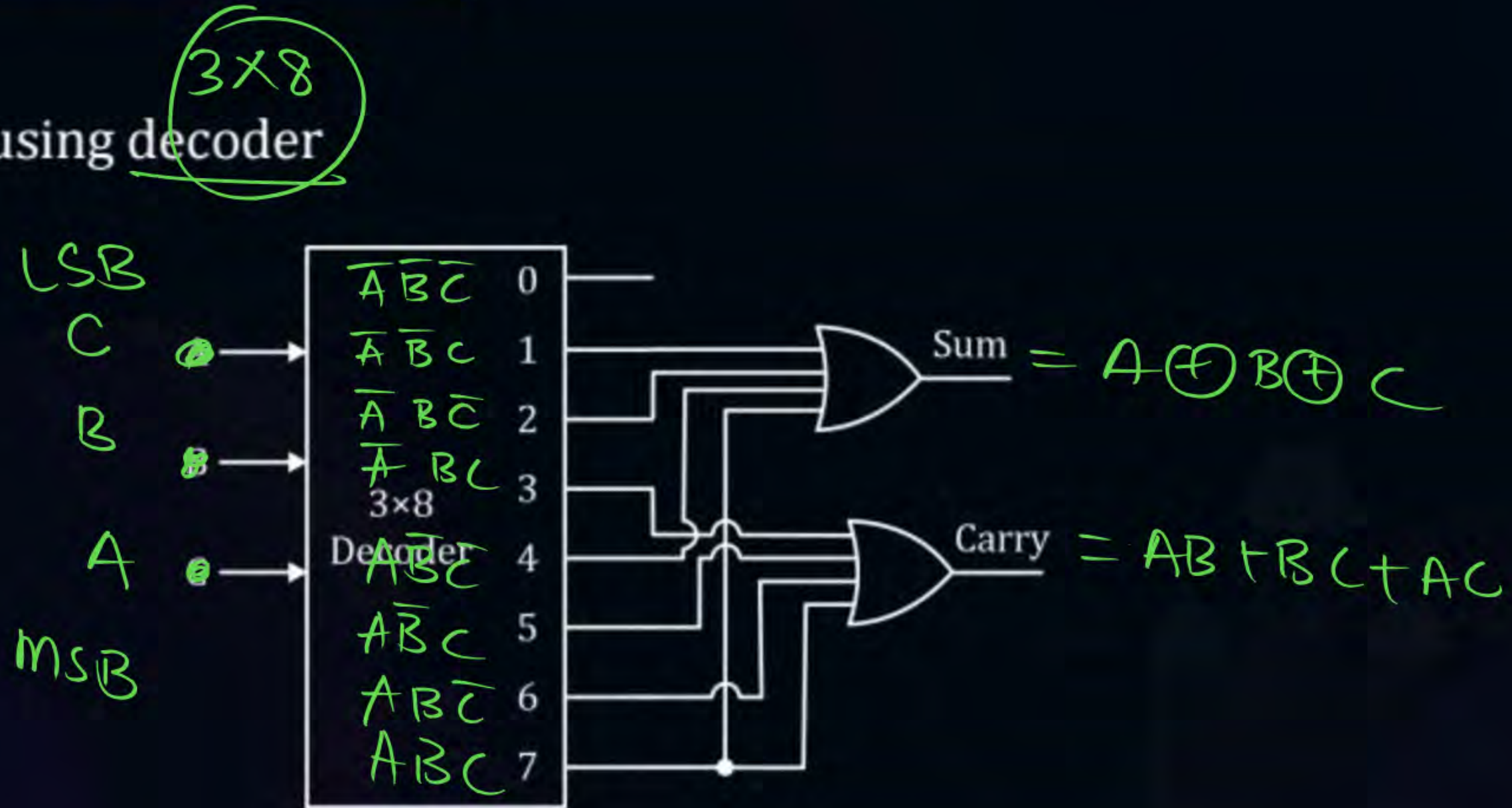




Topic : Full Adder

H.W Ans

Full Adder using NOR

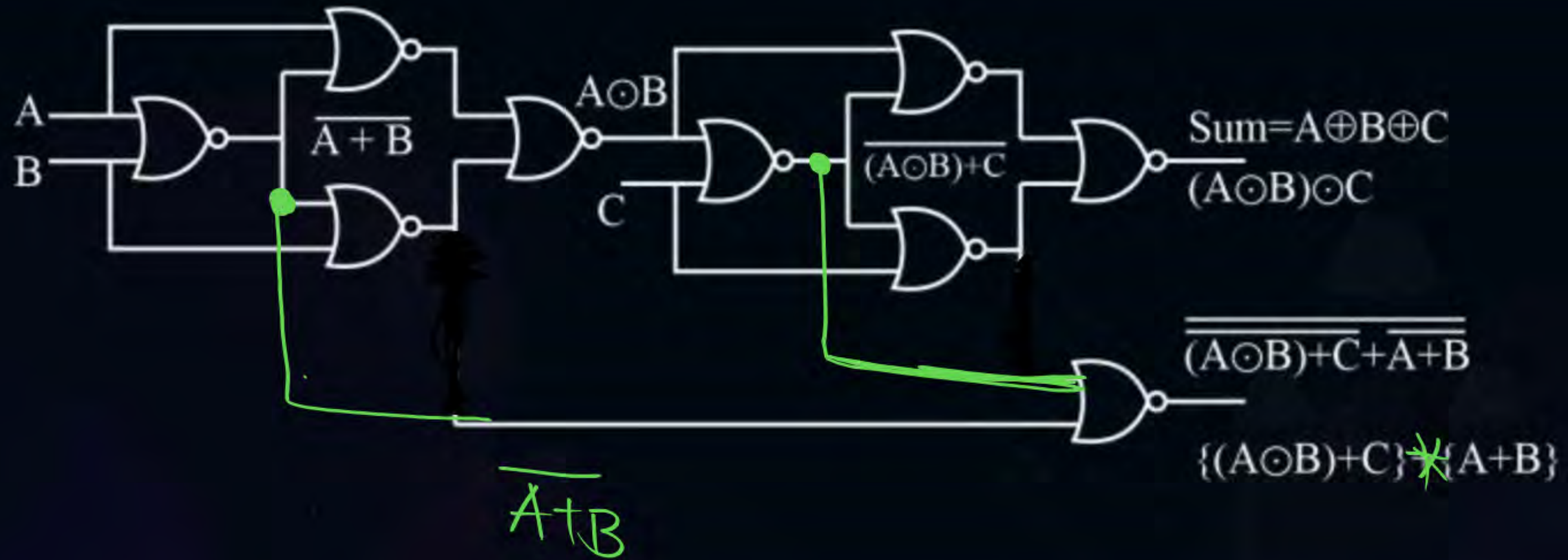

FA using NOR

as per prev image,

$$\text{Sum} = A \odot B \odot C = A \oplus B \oplus C \checkmark$$

$$\text{Carry} = ((A \odot B) + C) (A + B)$$

$$= ((AB + \bar{A}\bar{B}) + C) (A + B)$$


$$= \cancel{ABA + ABB + \bar{A}\bar{B}A + \bar{A}\bar{B}B} + AC + BC$$

$$= AB + AB + AC + BC$$

$$= AB + BC + AC \quad \text{😊}$$

Full Subtractor (FS)


↳ minor changes in the
NOR impl of FA

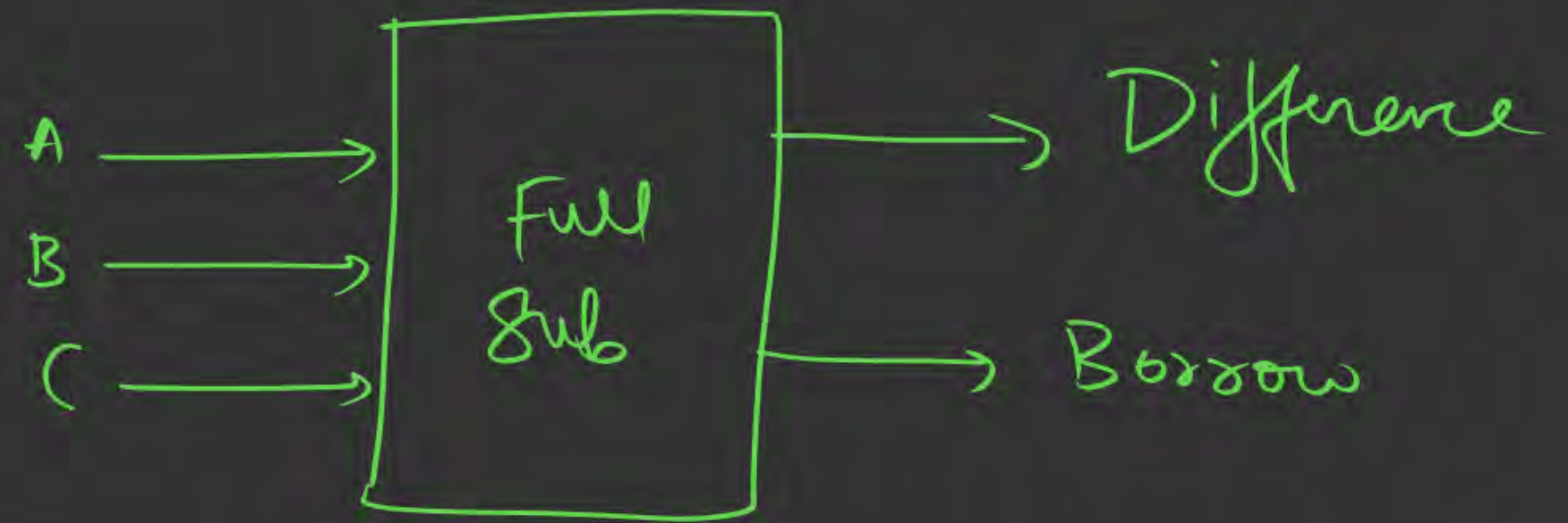



Topic : Full Addder

(FA & FS using NOR)

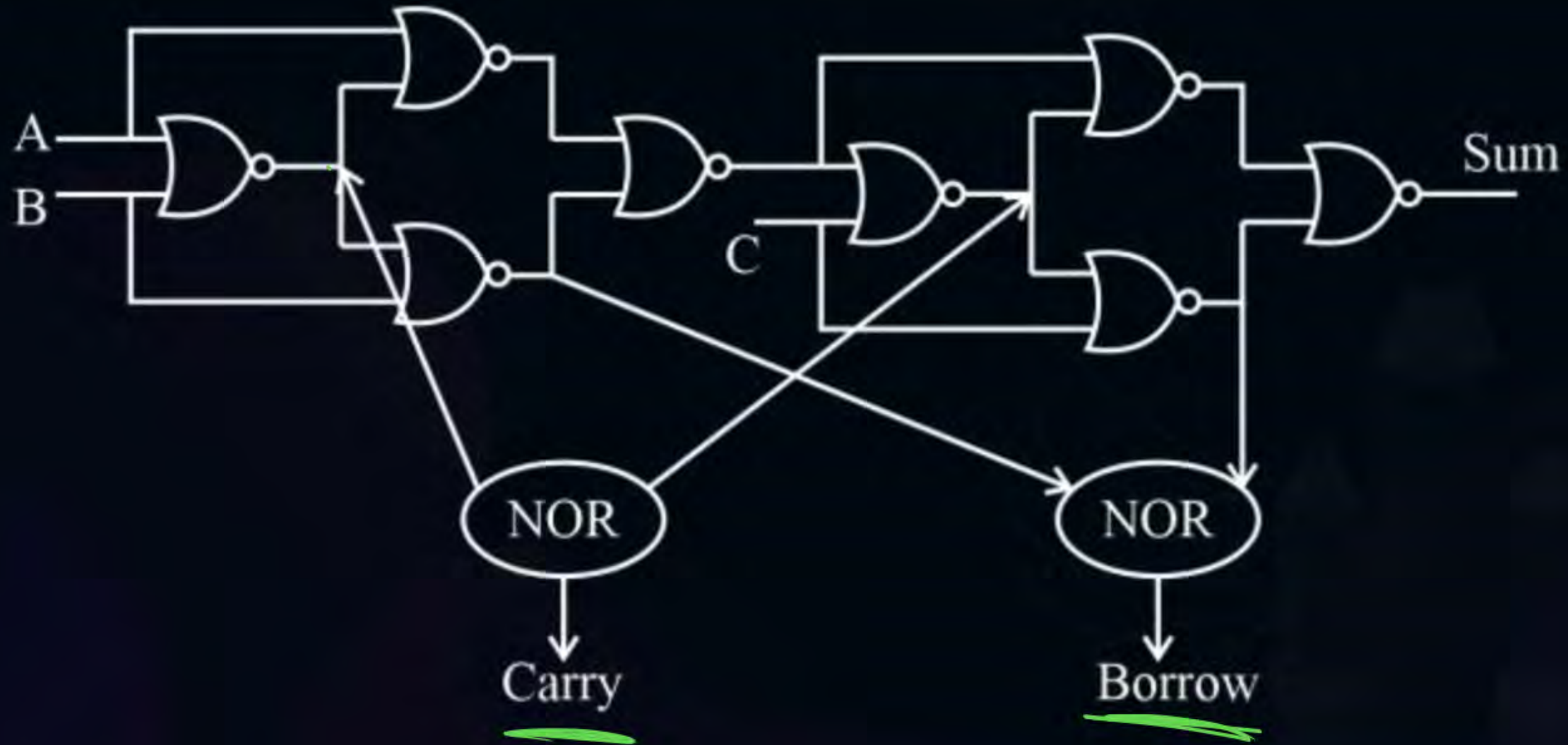




Topic : Full Adder

H.W Ans

Full Subtractor using NOR

(Bonus)

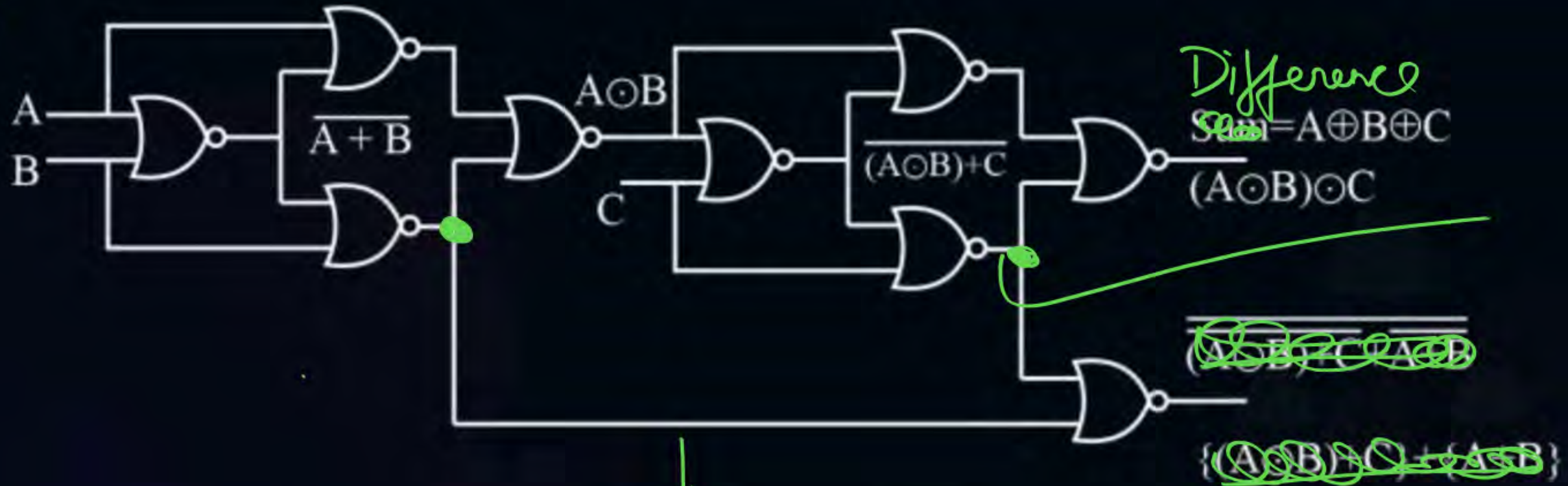

$$\overline{A+B+B} = \overline{A \cdot B + B} = \overline{A \cdot B} \cdot \overline{B} = (A+B) \cdot \overline{B} = A \cdot \overline{B}$$



Topic : Full Addder



$$\overline{A\bar{B}} + (A \odot B)\bar{C}$$

$$\overline{A\bar{B}} \diamond \overline{(A \odot B)\bar{C}}$$

$$(\bar{A} + B) \left[\overline{(A \odot B)} + C \right]$$

$$(\bar{A} + B)[\bar{A}B + A\bar{B} + C]$$

$$\bar{A}B + \bar{A}C + \bar{A}B + BC$$

$$\bar{A}B + \bar{A}C + BC \Rightarrow \boxed{\text{Borrow}}$$

Shortcut 😊

$$F.A \quad \underline{\underline{\text{carry}}} \Rightarrow AB + BC + AC$$

$$F.S \quad \underline{\underline{\text{borrow}}} \Rightarrow \bar{A}B + BC + \bar{A}C$$



Topic : Full Adder

Half adder

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = AB$$

$$\text{NAND / NOR} = 5$$

Summary
for
GATE

Full adder


$$\text{Sum} = \sum m\{1,2,4,7\} = A \oplus B \oplus C$$

$$\text{Carry} = \sum m(3,5,6,7)$$

$$= (A \oplus B)C + AB \rightarrow \text{semi-minimized}$$

$$= \underline{AB + BC + AC}$$

$$\text{NAND / NOR} = 9$$

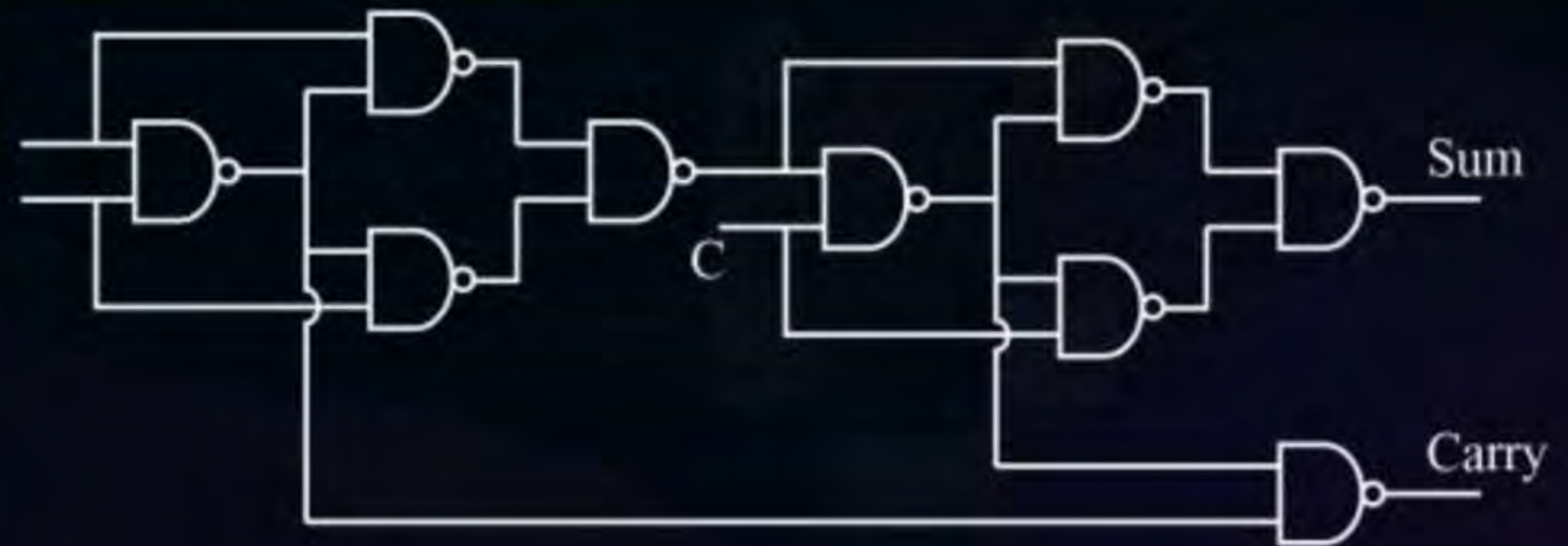



Topic : Half Subtractor

Two bit subtractor are known as half subtractor.

Step-1

2 i/p
2 o/p





Topic : Half Subtractor



Step-1

A	B	Diff.	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Step-2

$$\begin{array}{r} 00 \\ - 00 \\ \hline 00 \end{array}$$

$$\begin{array}{r} 11 \\ - 00 \\ \hline 11 \end{array}$$

$$\begin{array}{r} 10 \\ - 01 \\ \hline \end{array}$$

★

Borrow

Diff



Topic : Half Subtractor

Step-3

Diff. $A \oplus B$

$$\begin{array}{r} 0 \\ - 1 \\ \hline 11 \\ \hline \end{array}$$

Borrow: $\bar{A}B$

Shortcut :-

F. A
H. A

} Replace $A \Rightarrow \bar{A}$, you get Borrow

H. A $\rightarrow$ Carry $A \cdot B$

H. S $\rightarrow$ Borrow $\bar{A}B$




Topic : Half Subtractor

Step-4

No minimization

Step-5

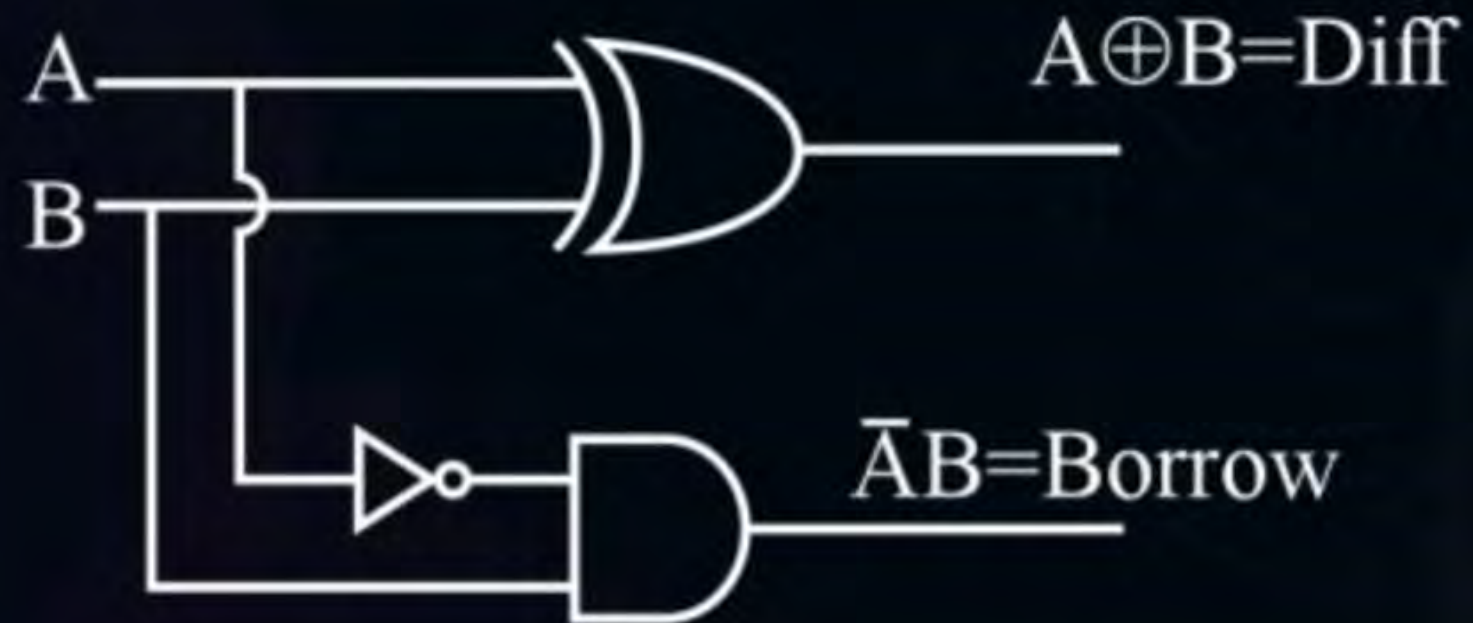



Topic : Half Subtractor


$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

5 NAND



$$\overline{A \cdot A} = \overline{A}$$

(Not gate)

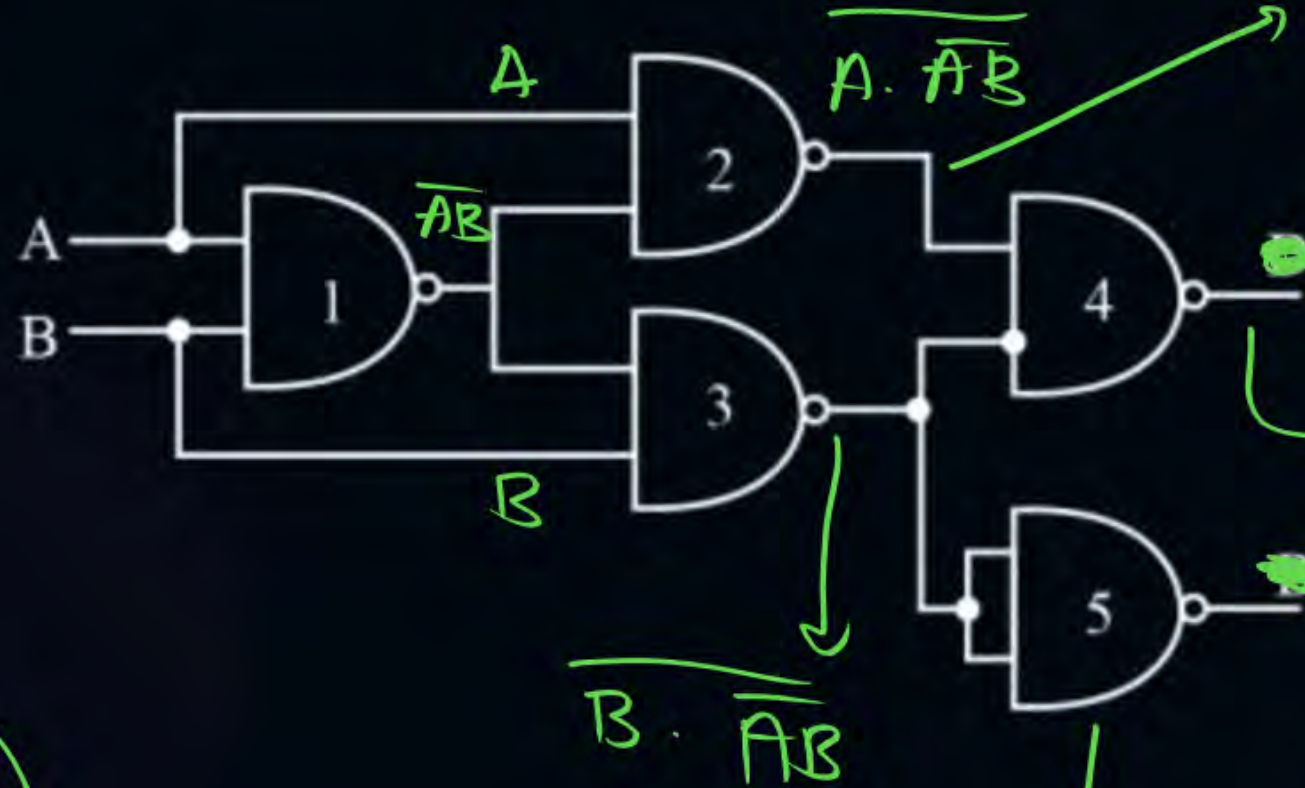

$$\begin{aligned} \overline{A} + \overline{\overline{A} \cdot \overline{B}} &= \overline{A} + AB \\ &= (\overline{A} + A)(\overline{A} + B) \\ &= \overline{A} + B \end{aligned}$$

$$\begin{aligned} &(\overline{A+B}) \cdot (A+\overline{B}) \\ &= \overline{A+B} + \overline{A+B} \\ &= A \cdot \overline{B} + \overline{A} \cdot B \end{aligned}$$

$$= A \oplus B \rightarrow \text{Diff}$$

$$A+B = \overline{\overline{A} \cdot \overline{B}}$$

→ Borrow

$$\begin{aligned} &B \cdot \overline{\overline{A} \cdot \overline{B}} \\ &= \overline{B} + \overline{\overline{A} \cdot \overline{B}} \\ &= \overline{B} + AB \\ &= (B+A)(\overline{B}+B) = A+B \end{aligned}$$


Half Subtractor using NAND gate



Topic : Half Subtractor

H.S using NOR

H.W

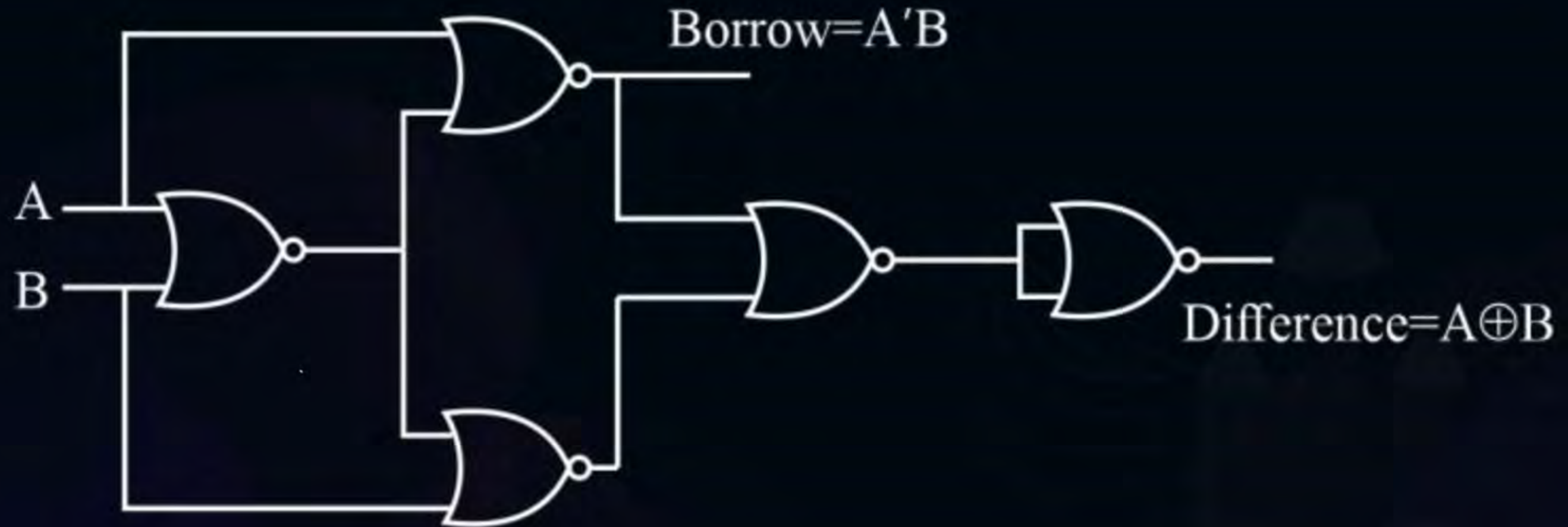



Topic : Full Subtractor





Topic : Full Subtractor



hp.w

INPUT			OUTPUT	
A	B	C	D	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1



Topic : Full Subtractor



H.W

HA

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = AB$$

HS

$$\text{Diff. } A \oplus B$$

$$\text{Borrow: } \bar{A}B$$

} $F \rightarrow \bar{A}$

FA

$$\text{Sum} = A \oplus B \oplus C$$

$$\text{Carry} = AB + AC + BC$$

HS

$$\text{Diff. } A \oplus B \oplus C$$

$$\text{Borrow: } \bar{A}B + \bar{A}C + BC$$

} $A \rightarrow \bar{A}$



2 mins Summary



HA

FA

HS

FS

→ Revisp
Tomorrow



THANK - YOU