


DPP 01

CS & IT

Digital Logic


Miscellaneous Topics

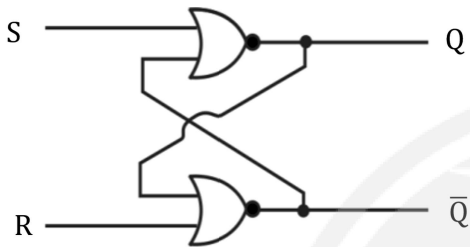- Q1** In an SR latch made by cross-coupling two NAND gates, if both S and R inputs are set to 0, then it will result in




- (A) $Q = 0, Q' = 1$
 (B) $Q = 1, Q' = 0$
 (C) $Q = 1, Q' = 1$
 (D) Indeterminate states

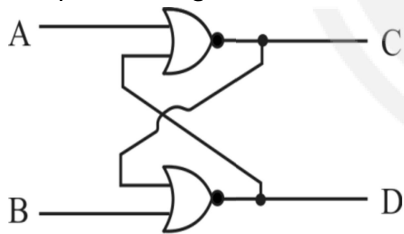- Q2** In the circuit shown below, when inputs $A = B = 0$, the possible logic states of C and D are




- (A) $C = 0, D = 1$ or $C = 1, D = 0$
 (B) $C = 1, D = 0$
 (C) $C = 1, D = 1$ or $C = 0, D = 0$
 (D) $C = 0, D = 1$

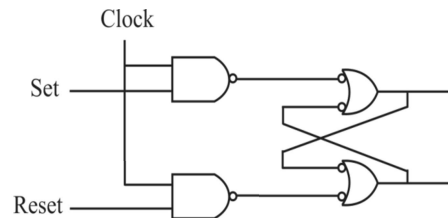- Q3** The two NAND gates before the latch circuit shown below, are used to



- (A) act as buffers
 (B) operate the latch faster
 (C) avoid racing
 (D) invert the latching action

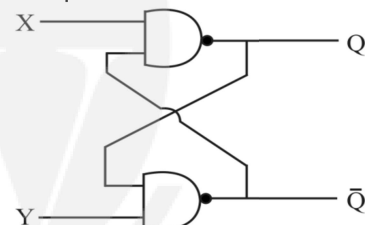- Q4** In the circuit shown below, outputs $Q\bar{Q} = 01$, the possible values of X and Y are



- (A) $X = 1, Y = 0$
 (B) $X = 1, Y = 1$
 (C) $X = 0, Y = 1$
 (D) $X = 0, Y = 0$

- Q5** Latch is a device with
 (A) One stable state
 (B) Two stable state
 (C) Three stable state
 (D) Infinite stable state

- Q6** The two addition operations $24 + 14 = 41$ and $23 + 12 = 101$ are performed on number bases b_1 and



b_2 respectively. The values of b_1 and b_2 are respectively

- (A) 7 and 4 (B) 4 and 7
(C) 8 and 4 (D) 4 and 8

Q7 If x and y are successive numbers in a number system of base b such that $(xy)_b = (25)_{10}$ and $(yx)_b = (31)_{10}$, then

- (A) $x = 4, y = 5$ and $b = 7$
(B) $x = 3, y = 4$ and $b = 6$
(C) $x = 4, y = 5$ and $b = 6$
(D) $x = 3, y = 4$ and $b = 7$

Q8 If $a = (4.4)_5$ and $b = (3.3)_5$, then $a + b = (x)_5$. The subscript 5 denotes the base on which the

corresponding number is expressed. The value of x is

- (A) 31.2 (B) 7.2
(C) 8.7 (D) 13.2

Q9 If $(X1CY)_{16} = (120702)_8$, then X and Y are

- (A) A and 2 (B) B and 1
(C) 1 and B (D) 2 and A

Q10 Given $(135)_b + (144)_b = (323)_b$, where subscript b denotes the base on which numbers are expressed. What is value of b ?

- (A) 4 (B) 5
(C) 6 (D) 7



Answer Key

Q1	(C)	Q6	(A)
Q2	(A)	Q7	(D)
Q3	(D)	Q8	(D)
Q4	(A, B)	Q9	(A)
Q5	(B)	Q10	(C)



Hints & Solutions

Q1 Text Solution:

$Q = 1, Q' = 1$

Q2 Text Solution:

$C = 0, D = 1$ or $C = 1, D = 0$

Q3 Text Solution:

invert the latching action

Q4 Text Solution:

$X = 1, Y = 0$

$X = 1, Y = 1$

Q5 Text Solution:

Two stable state

Q6 Text Solution:

7 and 4

Q7 Text Solution:

$x = 3, y = 4$ and $b = 7$

Q8 Text Solution:

13.2

Q9 Text Solution:

A and 2

Q10 Text Solution:

6



[Android App](#)

| [iOS App](#)

| [PW Website](#)