

CS & IT ENGINEERING



Digital Logic

Optimisation

Lecture No. 02



By- Aditya sir

Recap of Previous Lecture



Topic

Universal Gates
NAND, NOR



Topics to be Covered



Topic

Continue with
Universal Gates

Practice Questions



Case 1 :- $y = A \cdot B \cdot \overline{C} \cdot D$

NAND :- $(2n - 2) + k$

NOR :- $(3n - 3) - k$

n = total no. of
i/p variables

k = no. of compl var.

(8) $y = \overline{P} + \overline{Q} + \overline{R}$

min. NAND $\rightarrow a = 3$

$a + b = ?$

min. NOR $\rightarrow b$



$7 + 3 = \underline{10}$

$$y = \bar{P} + \bar{Q} + \bar{R}$$

$$\underline{\underline{b=7}}$$

NOR



$$(2n-2)+K$$


$$n=3$$

$$K=3$$

$$3 \times 2 - 2 + 3$$

$$6 - 2 + 3$$

$$= \textcircled{7}$$

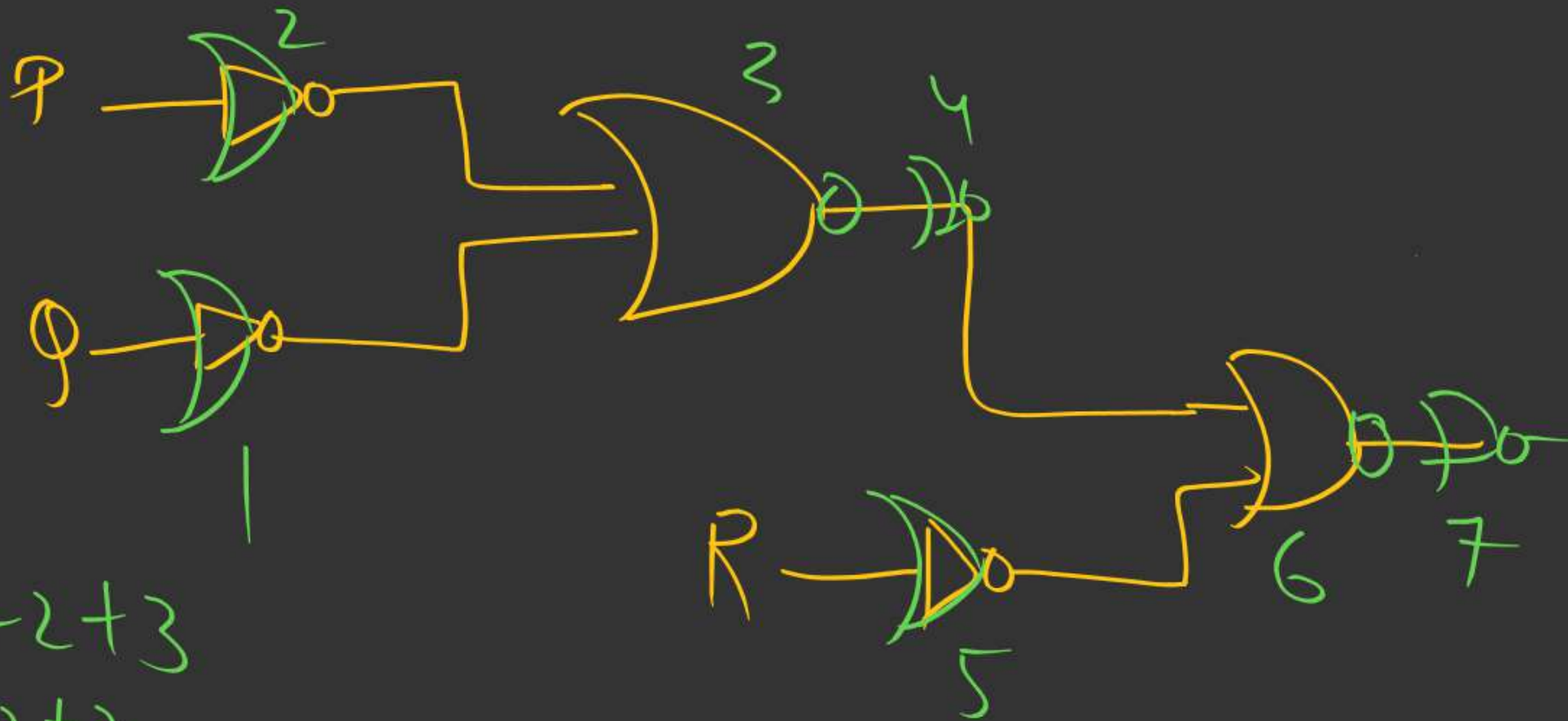

$$\underline{\underline{a=3}}$$

$$n=3, k=3$$

$$3n-3-k$$

$$3 \times 3 - 3 - 3$$


$$= \textcircled{3}$$



$$Y = \overline{P} \overline{Q} R \overline{S}$$

NAND

$$\underline{\underline{a=9}}$$

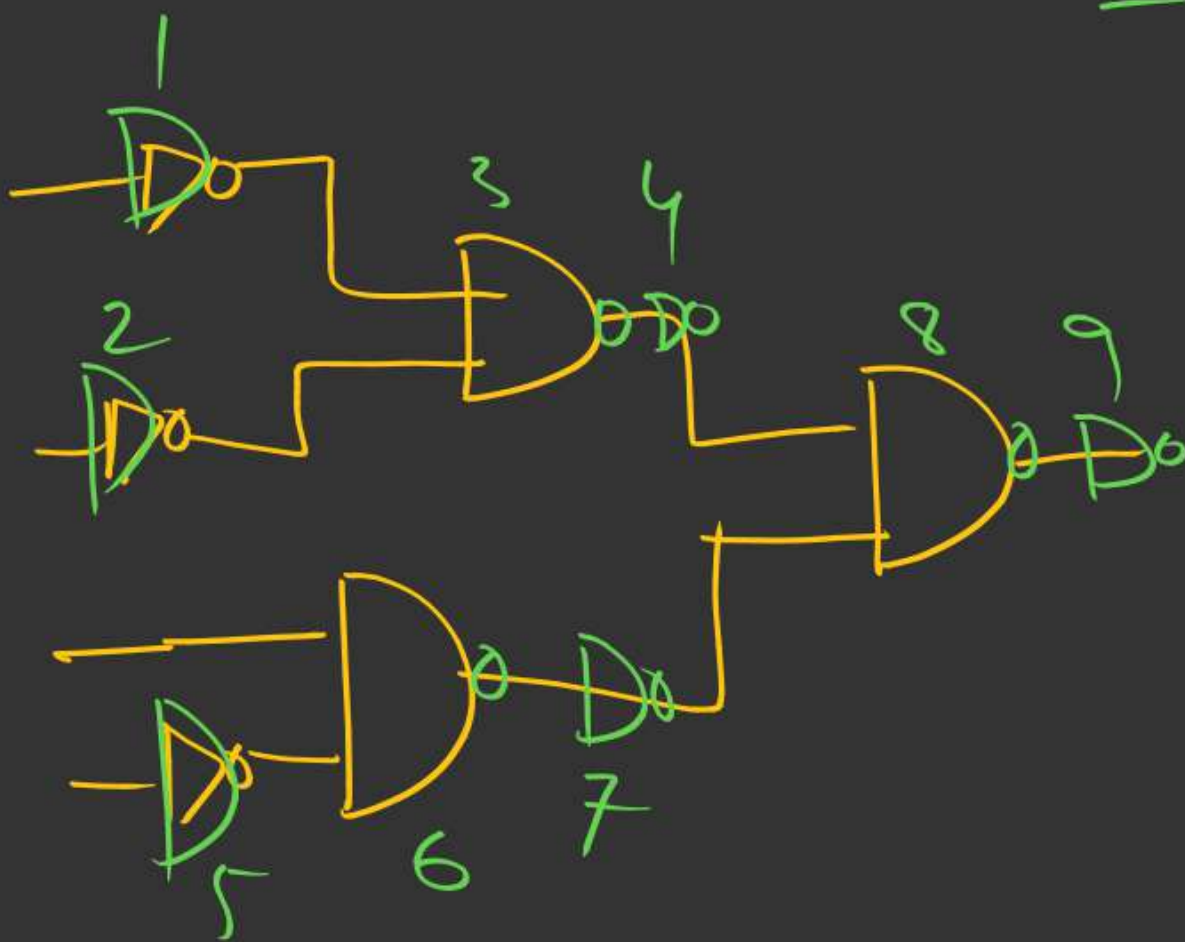

Calc:- $(2^n - 2) + k$

$$n=4$$

$$k=3$$

$$2 \times 4 - 2 + 3$$

$$= 8 + 1 = \textcircled{9}$$

NOR

$$\underline{\underline{b=6}}$$


$$n=4, k=3$$

$$3n-3-k$$

$$3 \times 4 - 3 - 3$$

$$= 12 - 6 = 6$$


$$y = \overline{P} \overline{Q} R \overline{S}$$

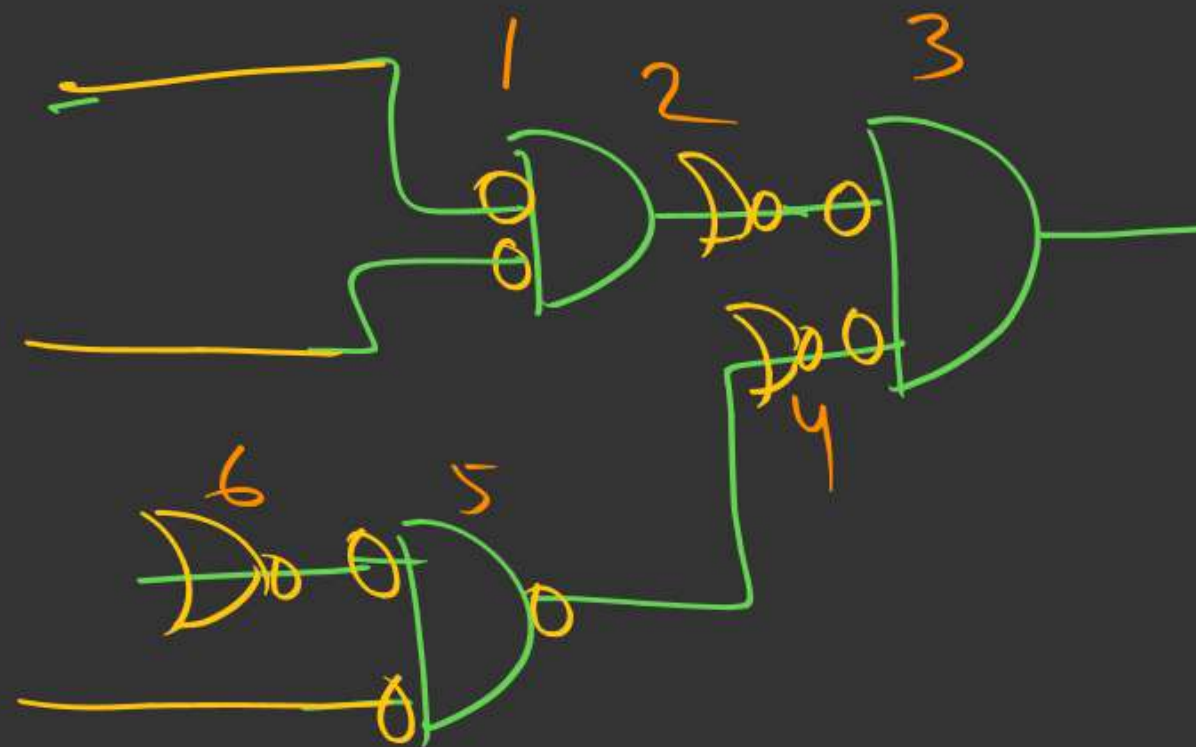


Case 3:- SOP format

NAND




$$y = AB + CD$$

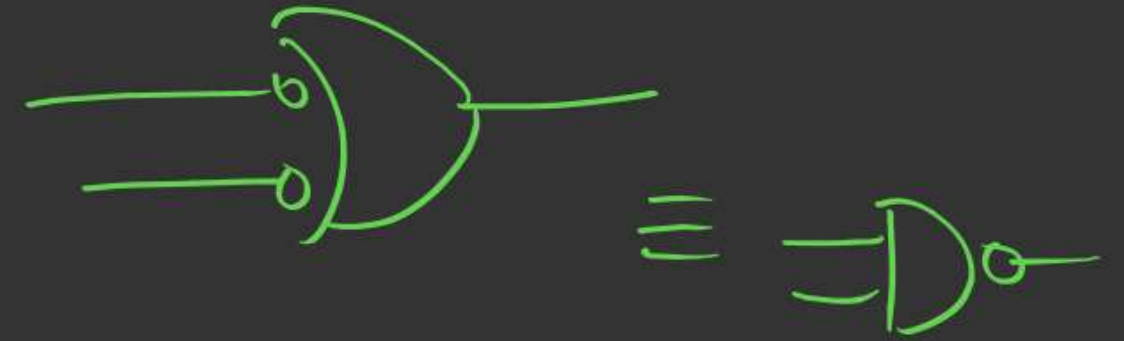

AOI

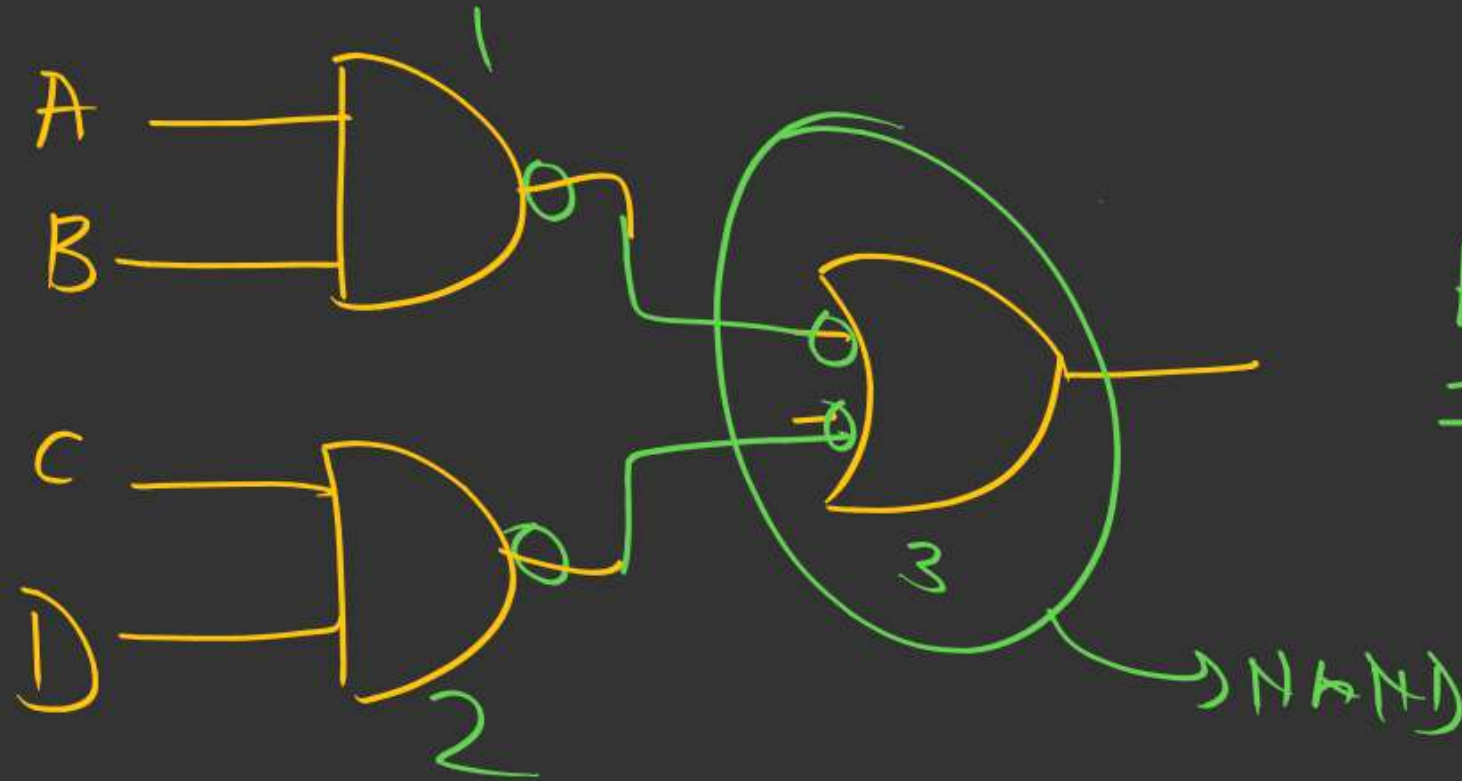

Ans: 3

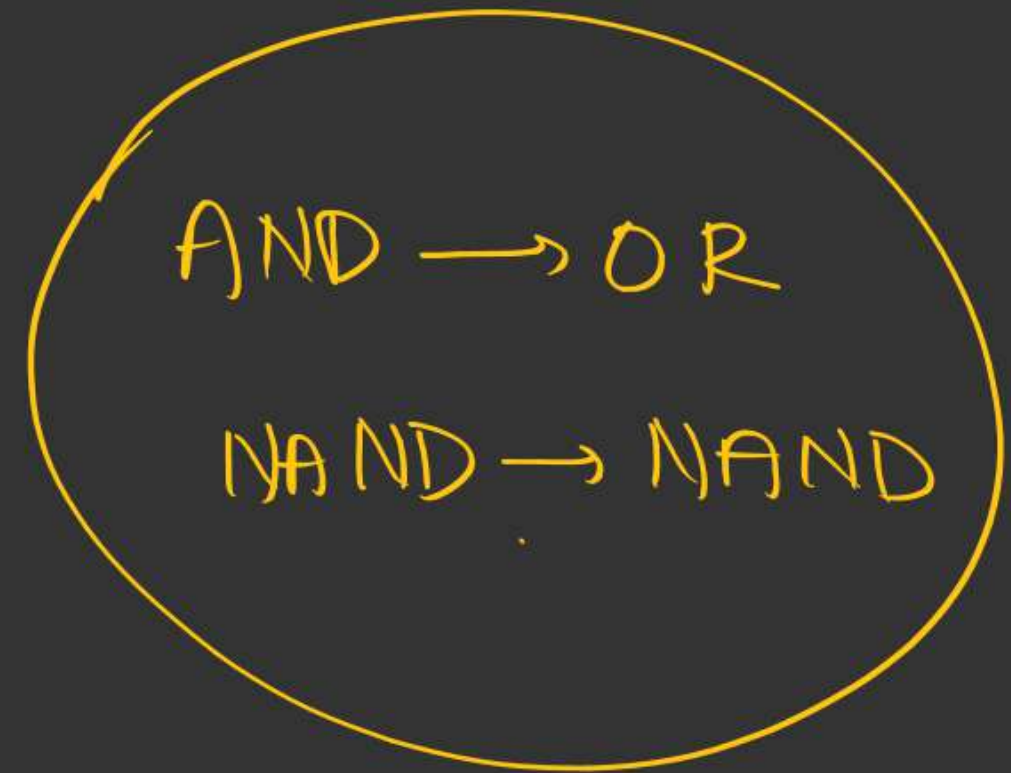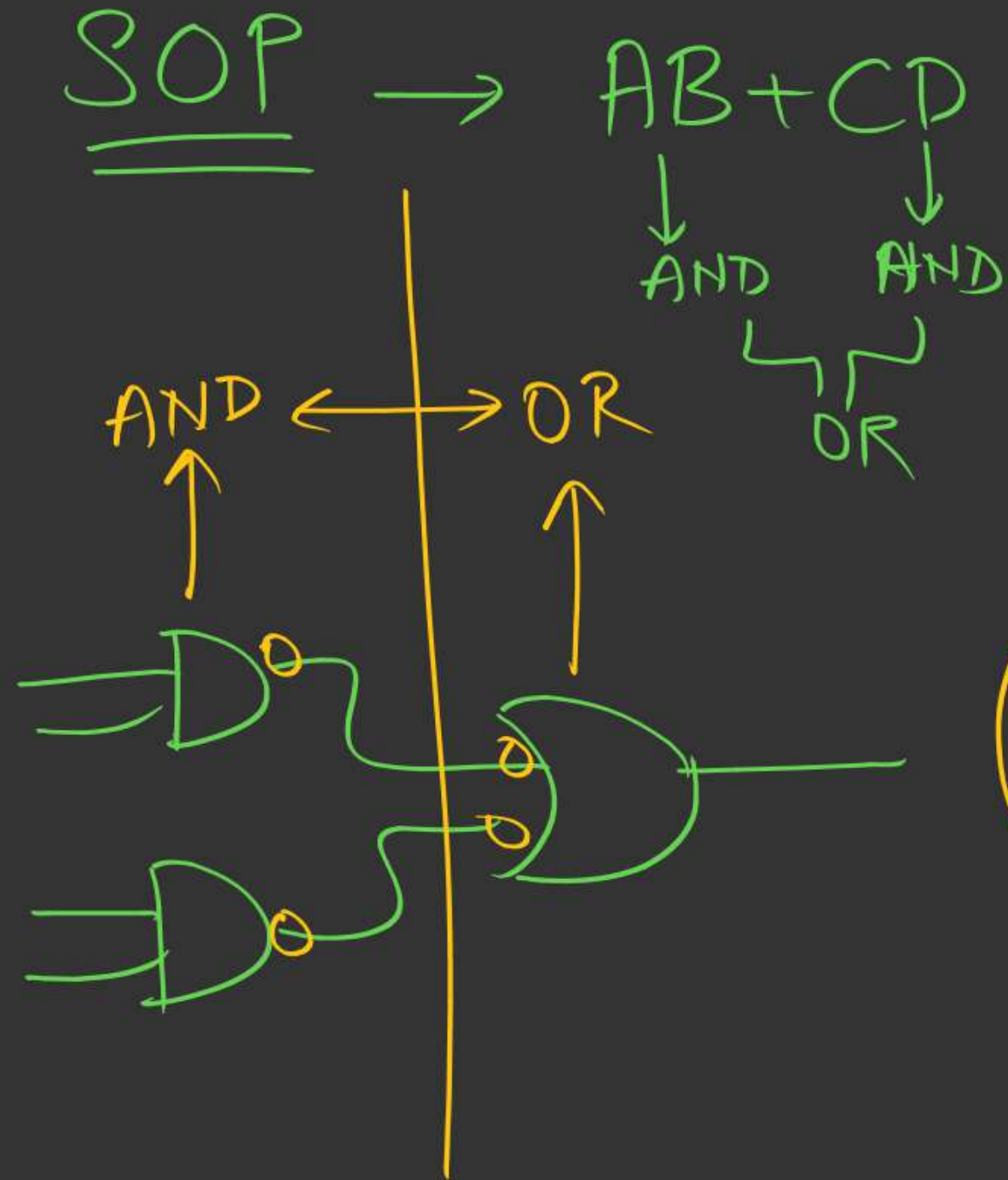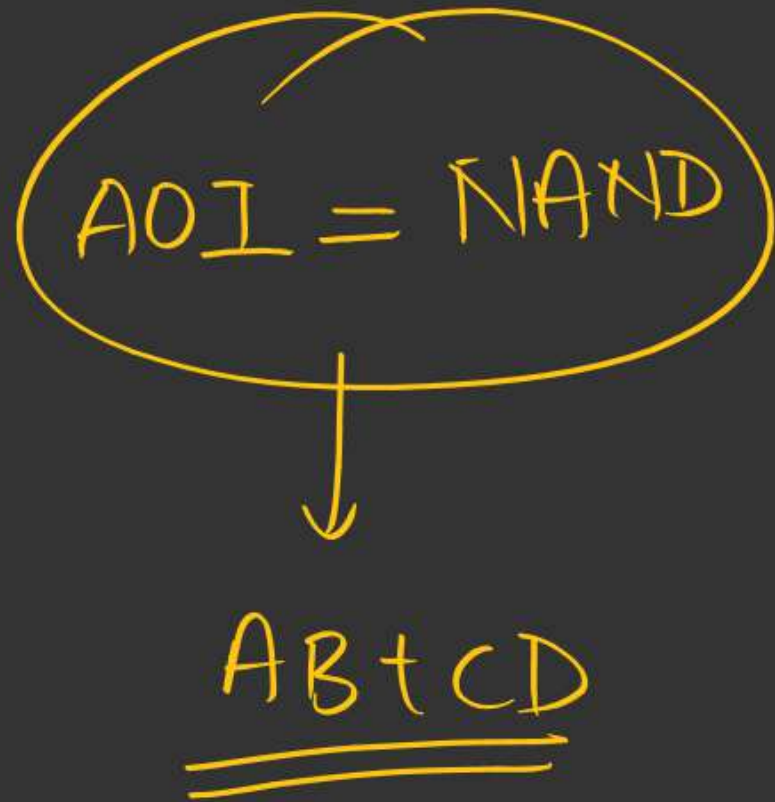

Imp:- $\rightarrow$ Min. no. of NAND

Steps:-


1) Write $\rightarrow$ SOP format

2) Use AOI $\Rightarrow$ [AND $\rightarrow$ OR]

3) Ans is exactly equal to AOI


bcoz AND $\rightarrow$ OR = (NAND $\rightarrow$ NAND)

Check
diagram

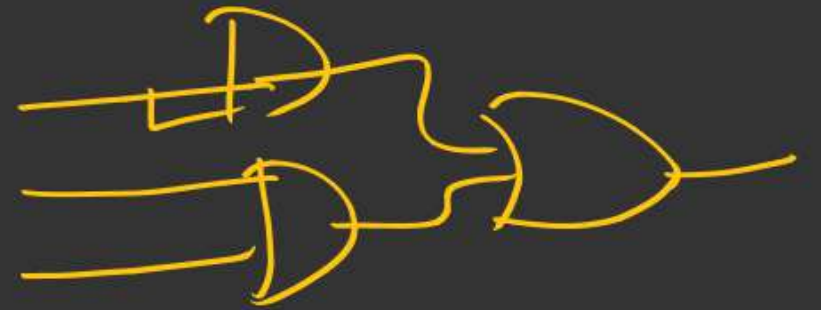

ex 2) :- $y = \bar{P}Q + RS \rightarrow \underline{\text{SOP}}$

NAND

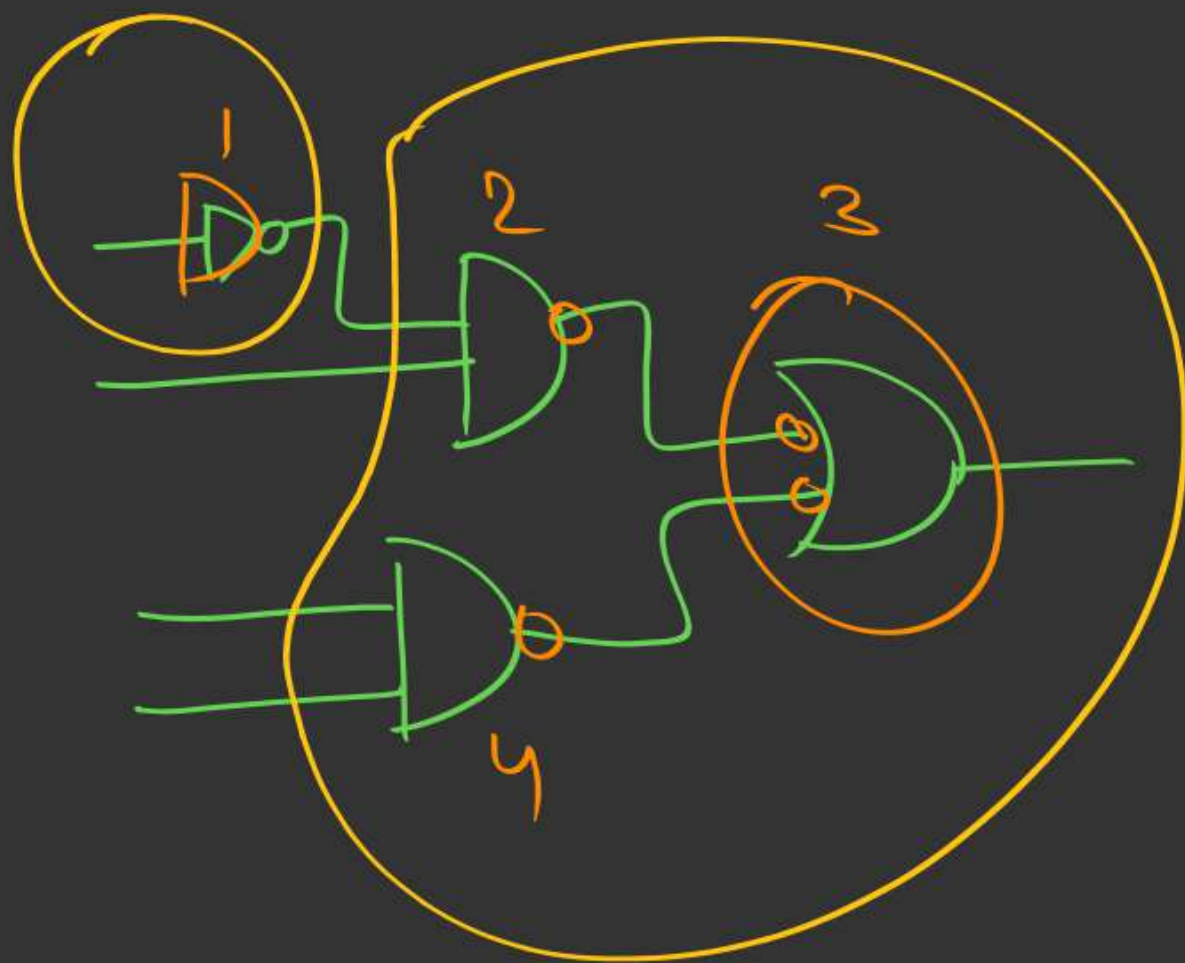

62%

AJ
Shortcut

$$y = \bar{P}Q + RS$$

Let $\bar{P} = A$ 1
NAND

$$y = \bar{A}Q + RS$$

$$3+1 = 4$$

3 NAND

71%


eg 3)

$$Y = PQ + R$$

$$\underline{\underline{PQ + RS}}$$

NAND?

$$Y = PQ + R \cdot R$$

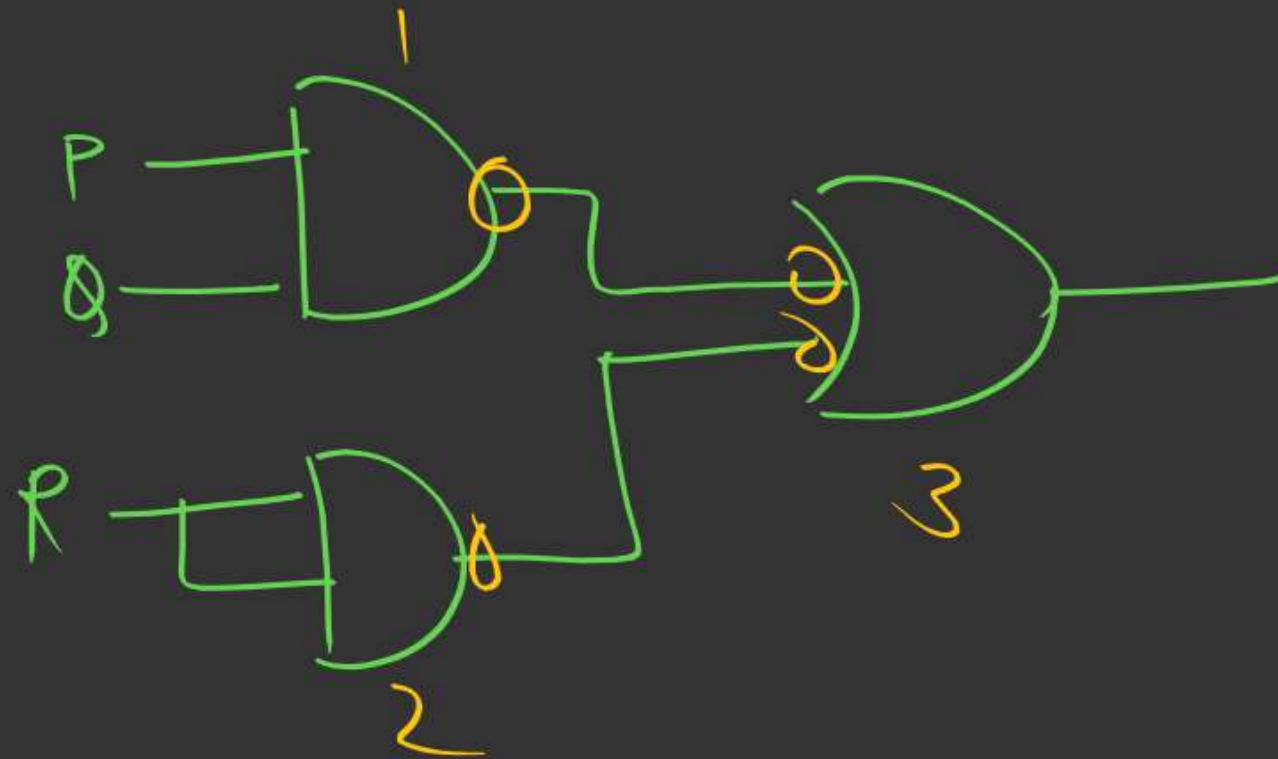


Ans: 3

$$PQ + RS$$

eg 4)

$$y = A + B$$

$$y = A + B \\ = A \cdot A + B \cdot B$$

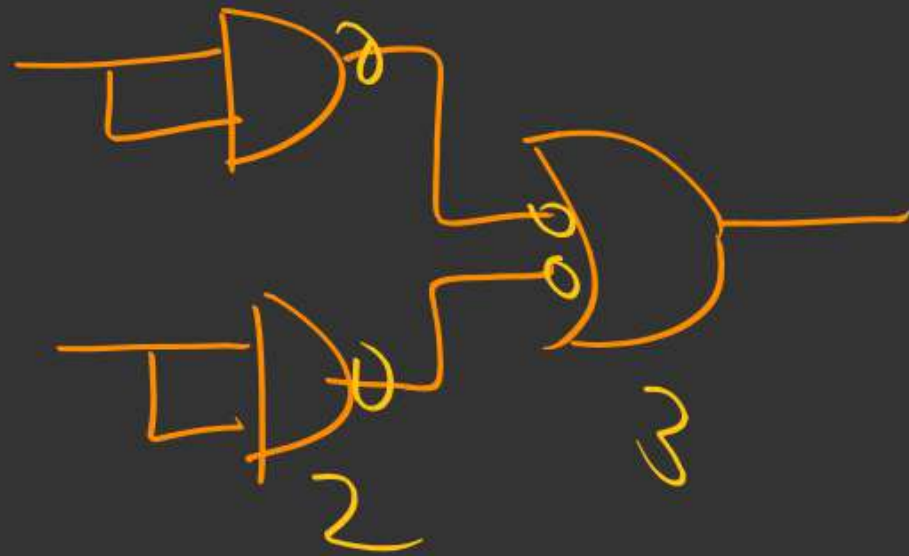

Solve using
Case 3


3 NAND

log 5)
min NAND?

AND $\rightarrow$ OR

$$y = PQ + RS + AB$$


3 NAND

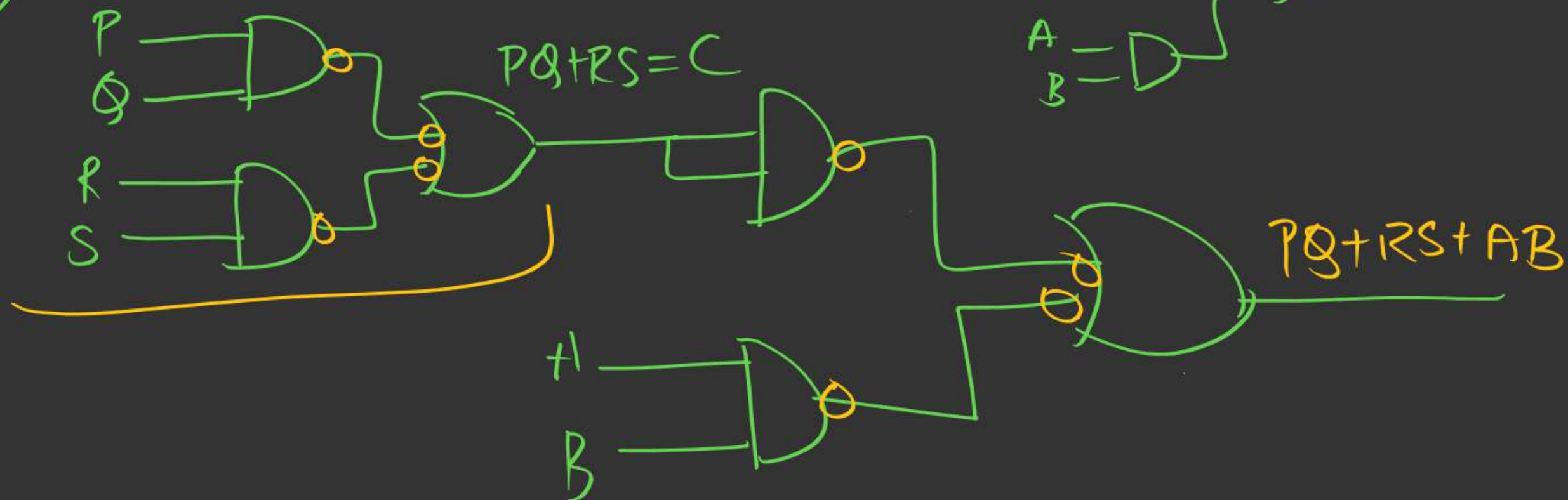

70%

45%

2 I/p

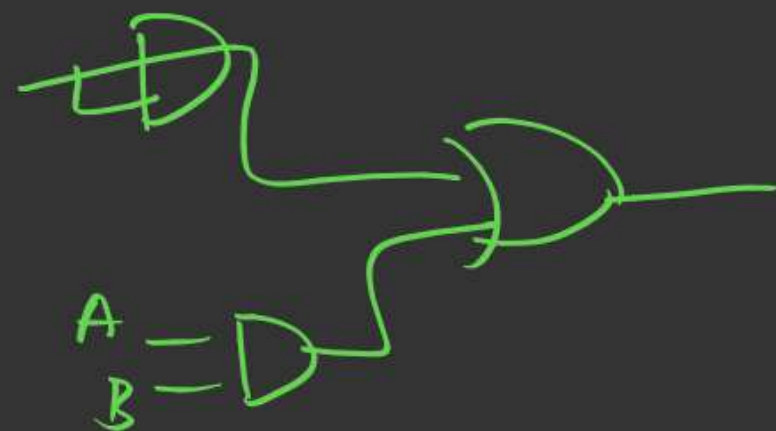

Explanation

$$y = \underbrace{PQ + RS} + AB$$

$$\underline{PQ + RS}$$

$$\text{let } C = \underbrace{PQ + RS}$$

$$y = C + AB$$

$$\underbrace{y = C \cdot C + AB}$$


3 NAND

$$3 + 3 = \underline{\underline{6 \text{ NAND}}}$$

3 NAND

min NAND

~~A~~

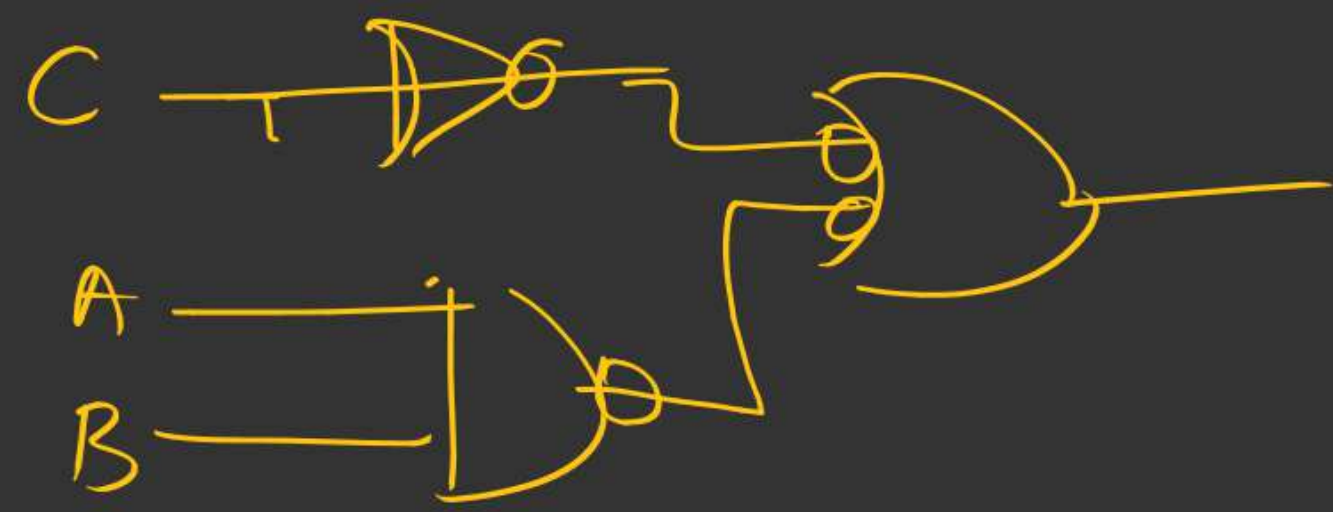

76%

$$y = PQ + R + AB$$
$$= \underbrace{PQ + AB + R}_C$$

min NAND = ?

$$C = PQ + RS$$

$C \rightarrow 3 \text{ NAND}$


$\rightarrow 3 \text{ NAND}$

$$y = \underbrace{C + R}$$

$C \cdot C + R \cdot R \} 3 \text{ NAND}$

6 NAND


6 NAND

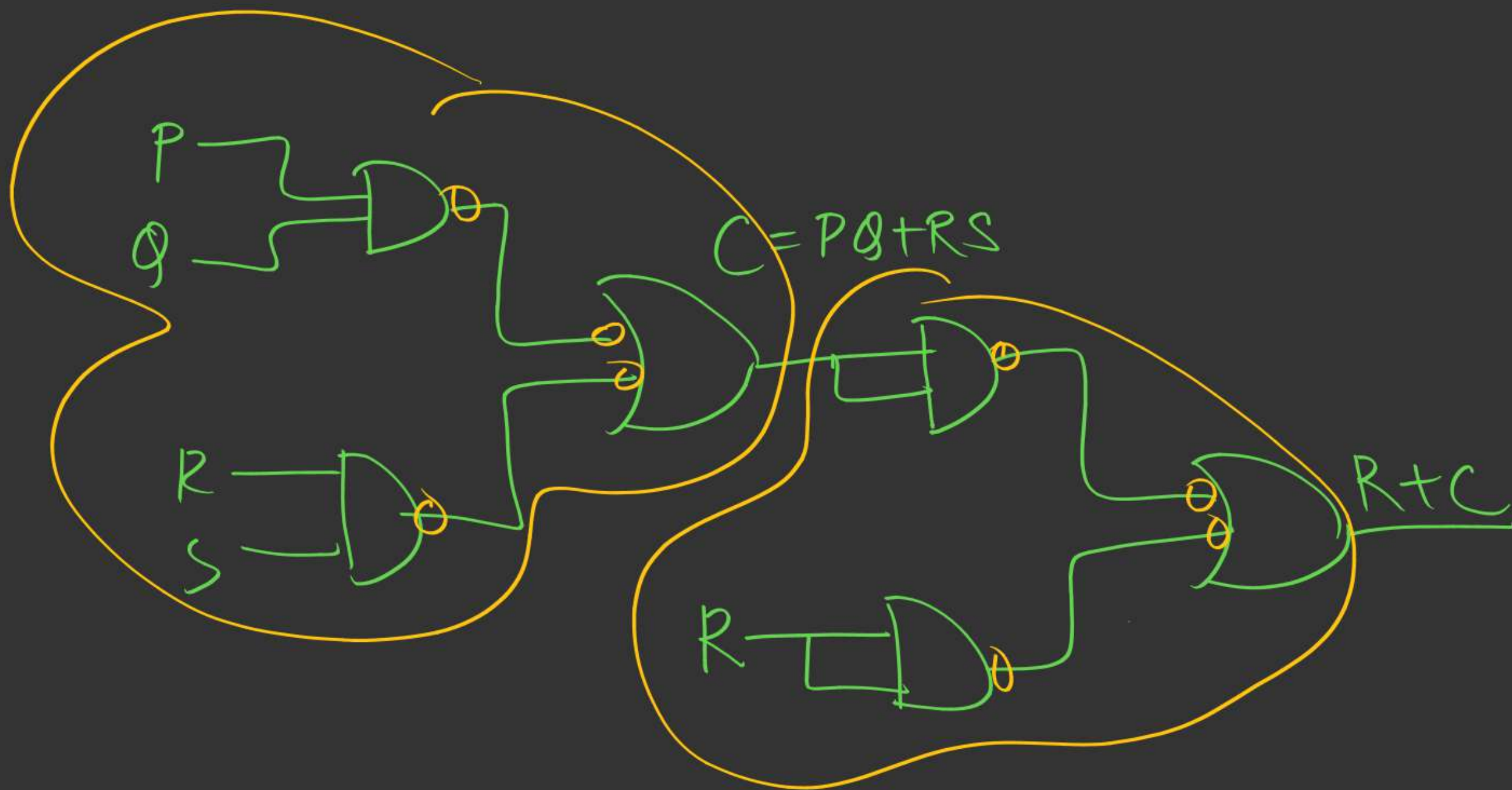

70%

$$y = PQ + \bar{R}\bar{S}$$

min NAND = ?

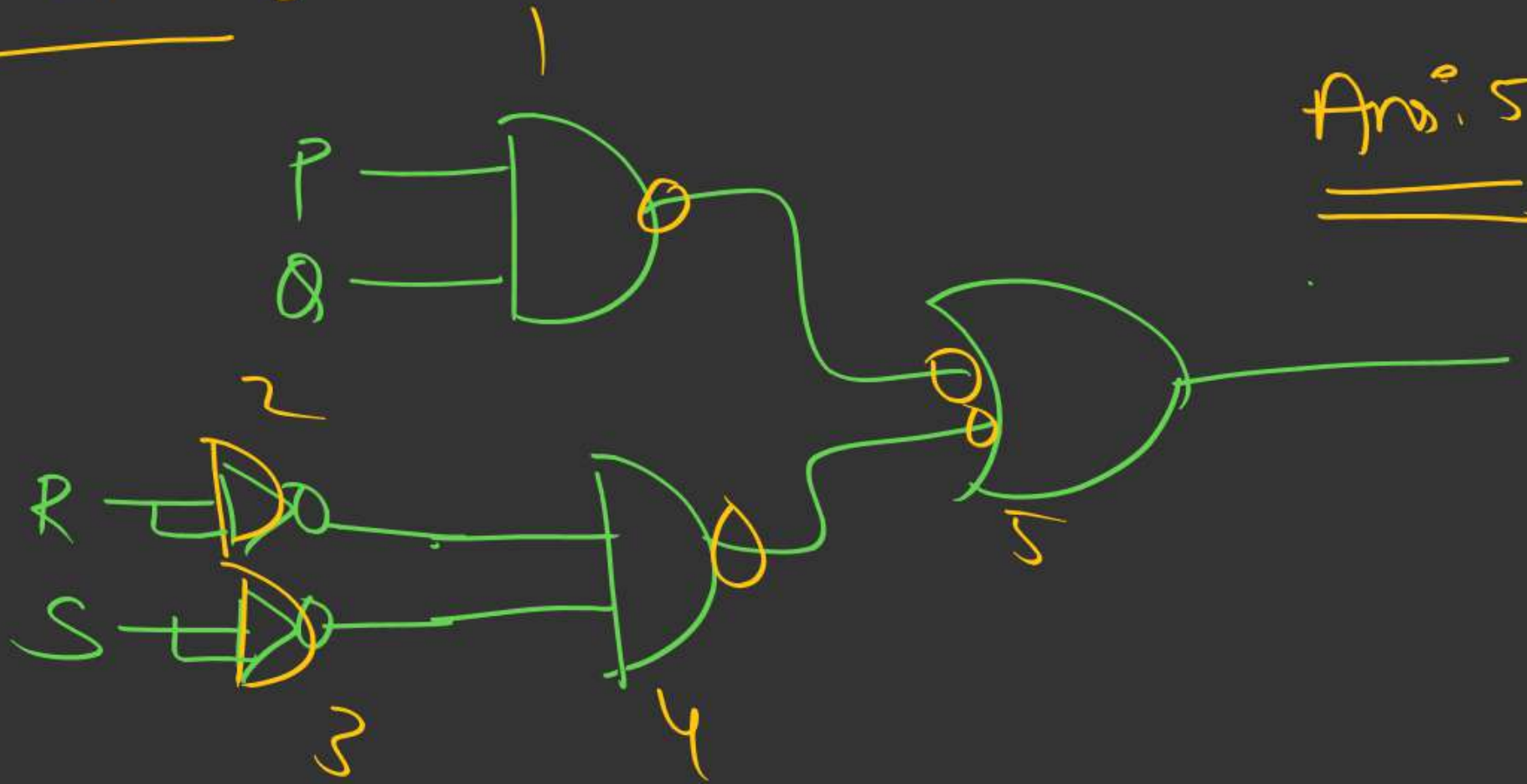

Ans: 5

$$y = PQ + \bar{R}\bar{S}$$

Let $A = \bar{R}$ →

$B = \bar{S}$ →

1 NAND

1 NAND


→ $1 + 1 + 3$
 $= 5$

→ $y = PQ + AB$

3 NAND

$$y = AB + BC + CD + DA$$

3

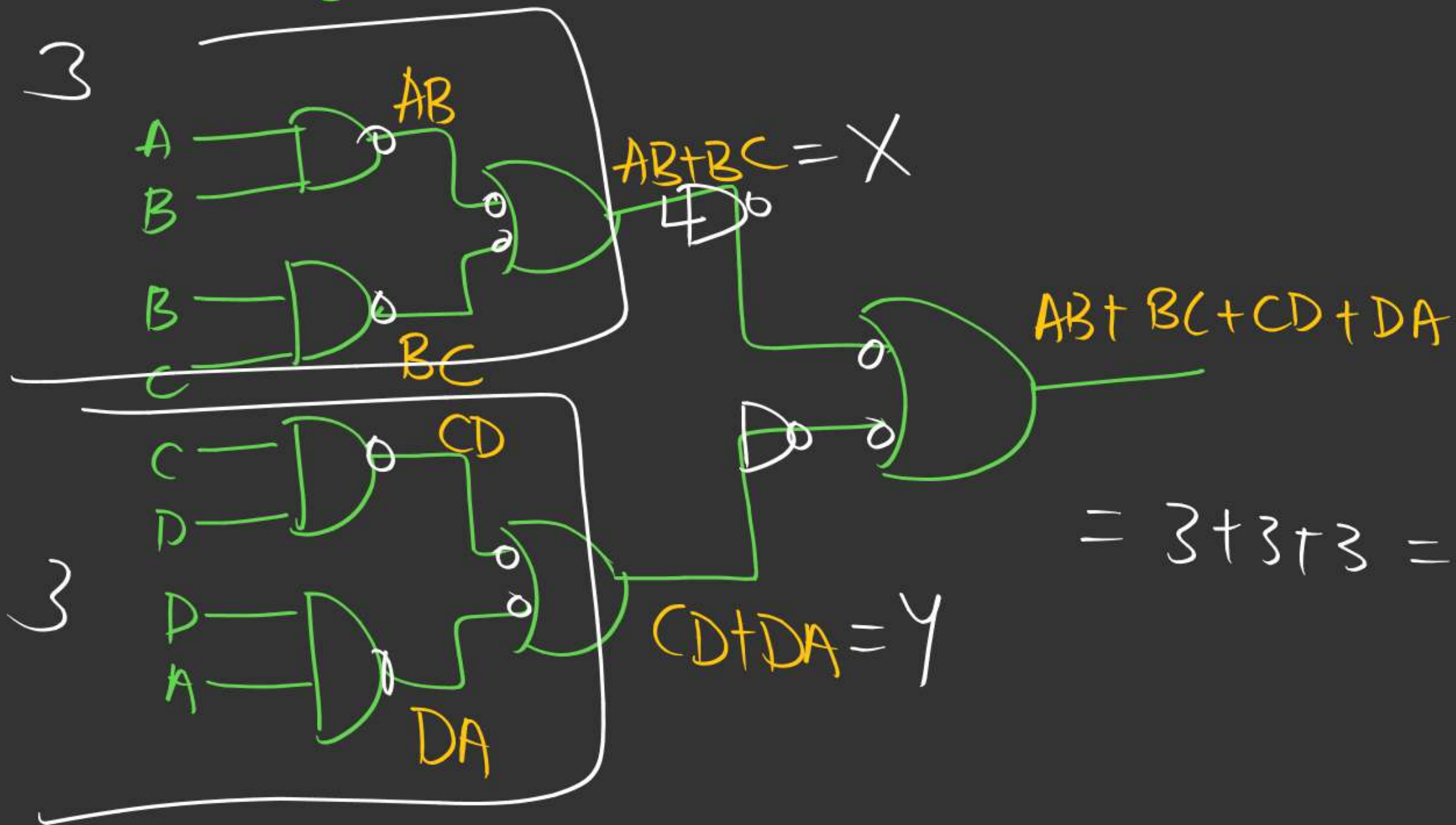

$$= 3 + 3 + 3 = 9$$

$$y = \underbrace{AB + BC}_P + \underbrace{CD + DA}_Q$$


$$P = AB + BC \rightarrow 3$$

$$Q = CD + DA \rightarrow 3$$

$$y = P + Q$$

$$= P \cdot P + Q \cdot Q \rightarrow 3$$

$$3 + 3 + 3 = 9$$

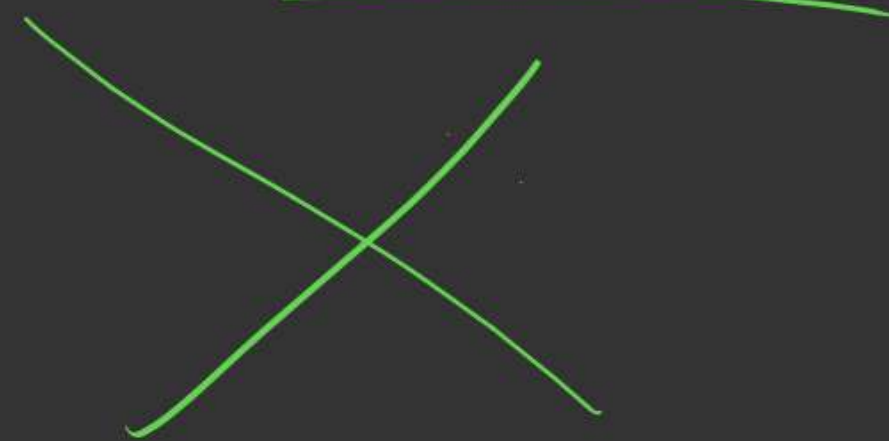

Appr 2:-

$$y = \underbrace{AB + BC} + \underbrace{CD + DA}$$

$$= B(A+C) + D(C+A)$$


$$= (B+D)(A+C)$$

Let $P = B+D \rightarrow 3$

$Q = A+C \rightarrow 3$

$y = \underline{\underline{P \cdot Q}} \rightarrow 2$

$$3+3+2 = \textcircled{8}$$

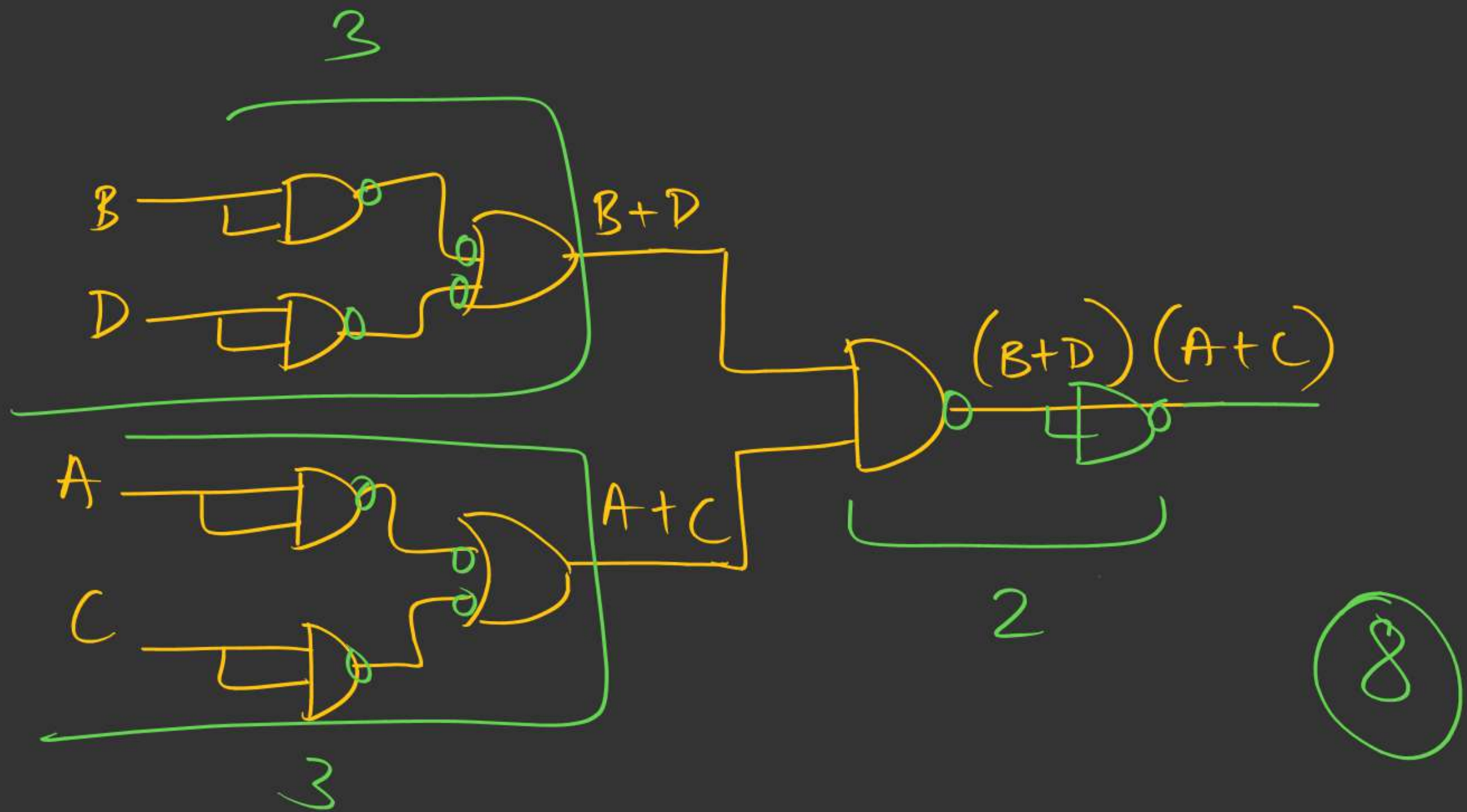

H.W1 → Draw diagram



2 mins Summary



NAND, NOR



THANK - YOU

