

CS & IT ENGINEERING



Digital Logic

Optimisation

Lecture No. 03



By- Aditya sir

Recap of Previous Lecture



Topic

V. Imp

Min no. of universal gates.



Topics to be Covered



Topic

Few more Cases


→ Application





Case 4:- POS $\rightarrow$ product of Sums (NOR)

eg:- $y = (P+Q)(R+S)$

$$y = (P+Q)(R+S)$$

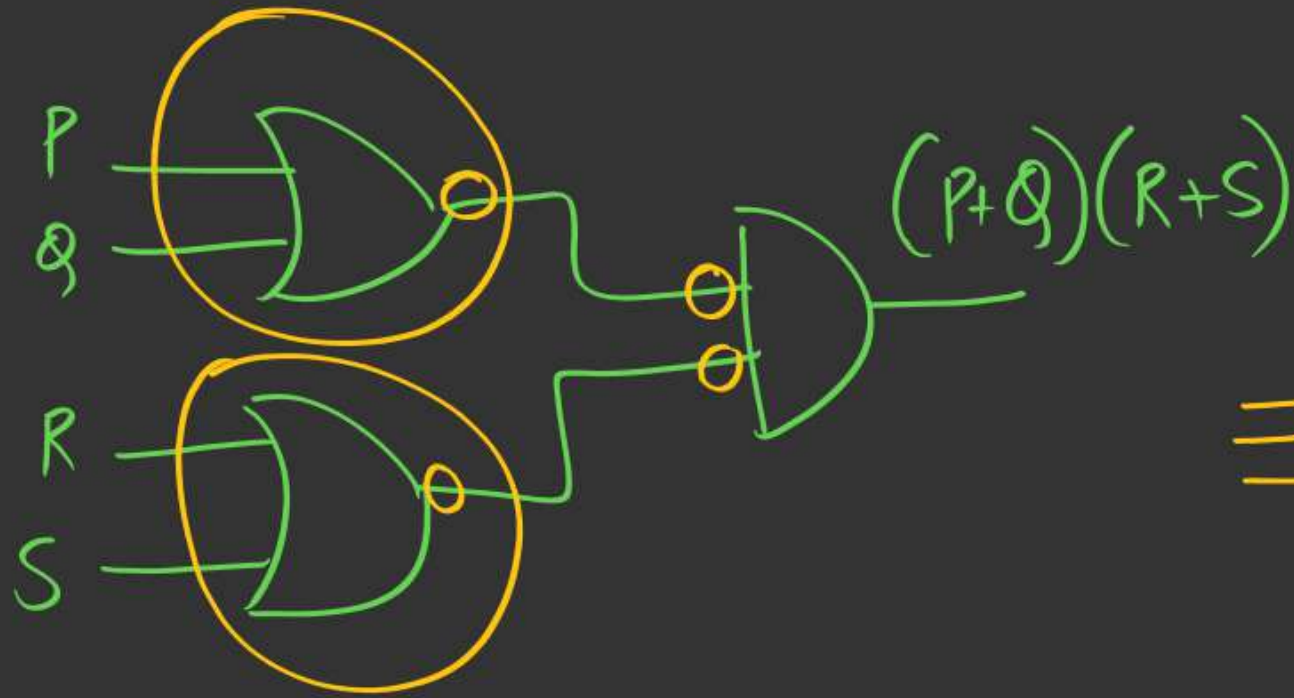

$\equiv$

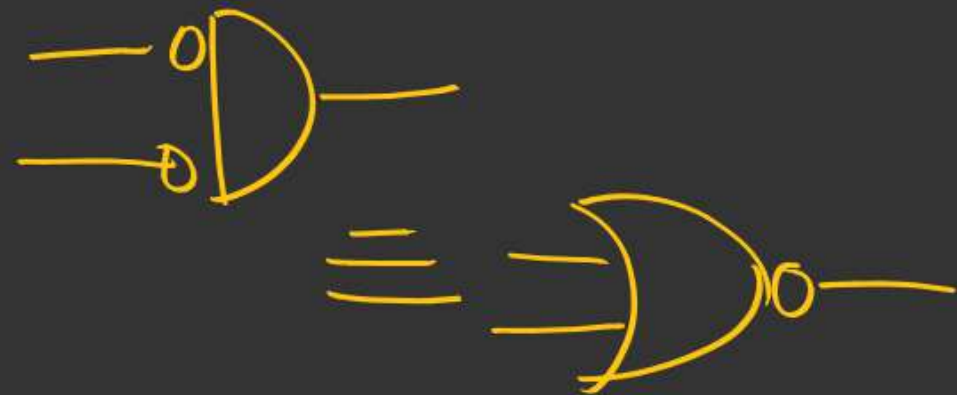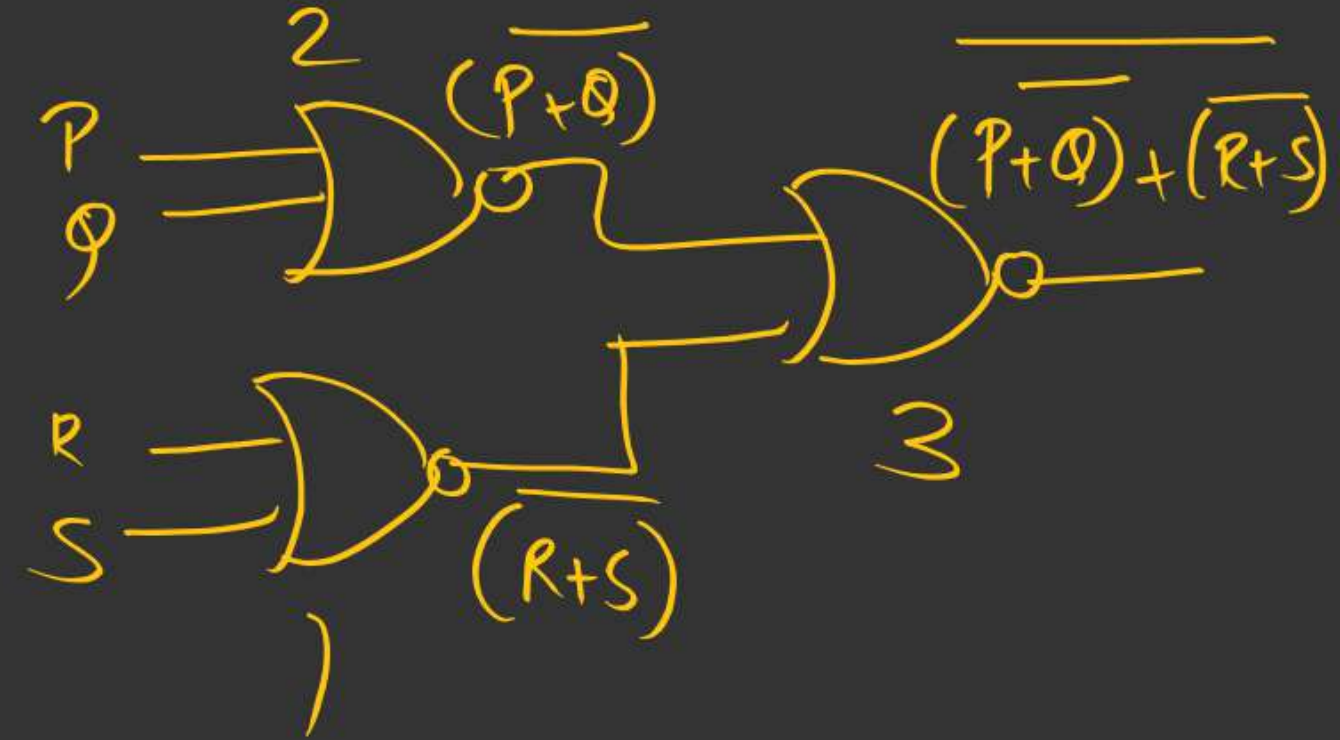

Ans 3

AOI
=

$$\begin{aligned} y &= \overline{(P+Q) + (R+S)} \\ &= \overline{(P+Q)} \cdot \overline{(R+S)} \end{aligned}$$

$$y = \underline{\underline{(P+Q) \cdot (R+S)}}$$


SOP



AND — OR

NAND — NAND


POS

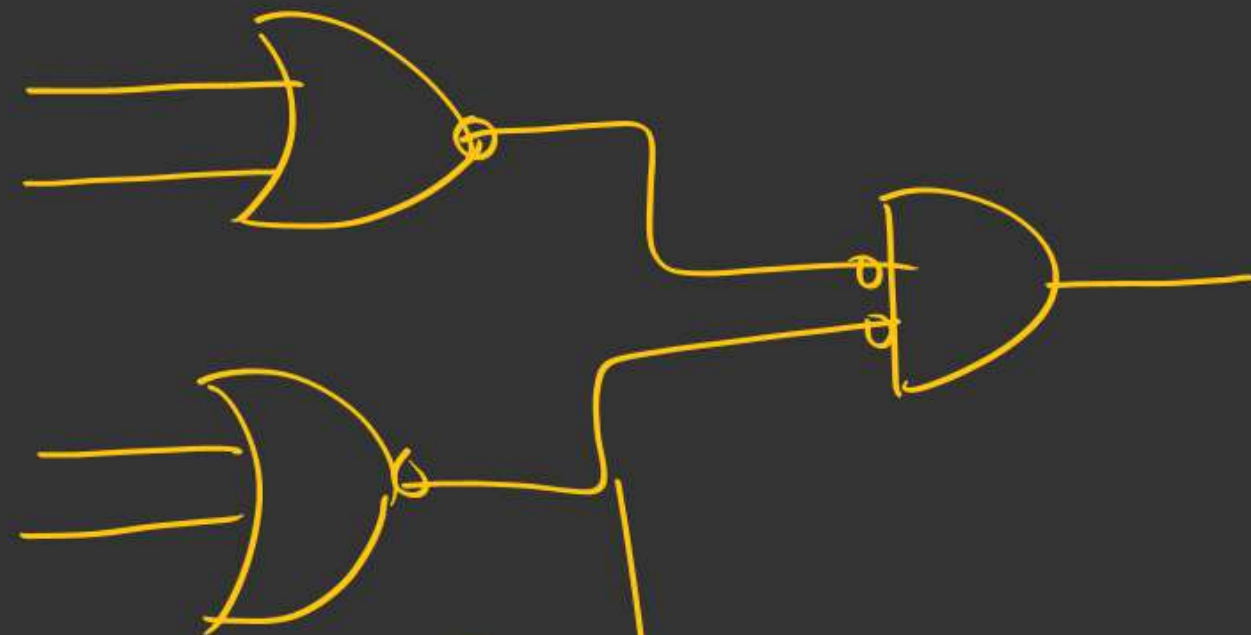

OR — AND

XOR — NOR

Imp:

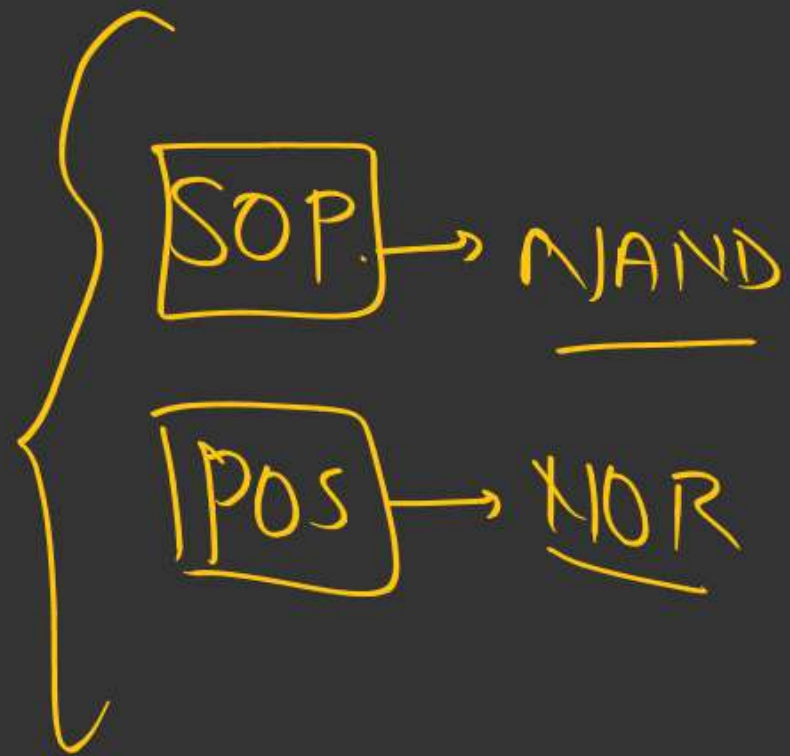

Min no. of NOR?

1) Convert to POS.

2) Implement using AOI

OR $\rightarrow$ AND

3) Convert NOR $\rightarrow$ NOR $\rightarrow$ Count NORs

eg - $y = PQ + R$

min NAND →


min NOR ?

$$y = PQ + R$$

NAND $\rightarrow$ SOP

3
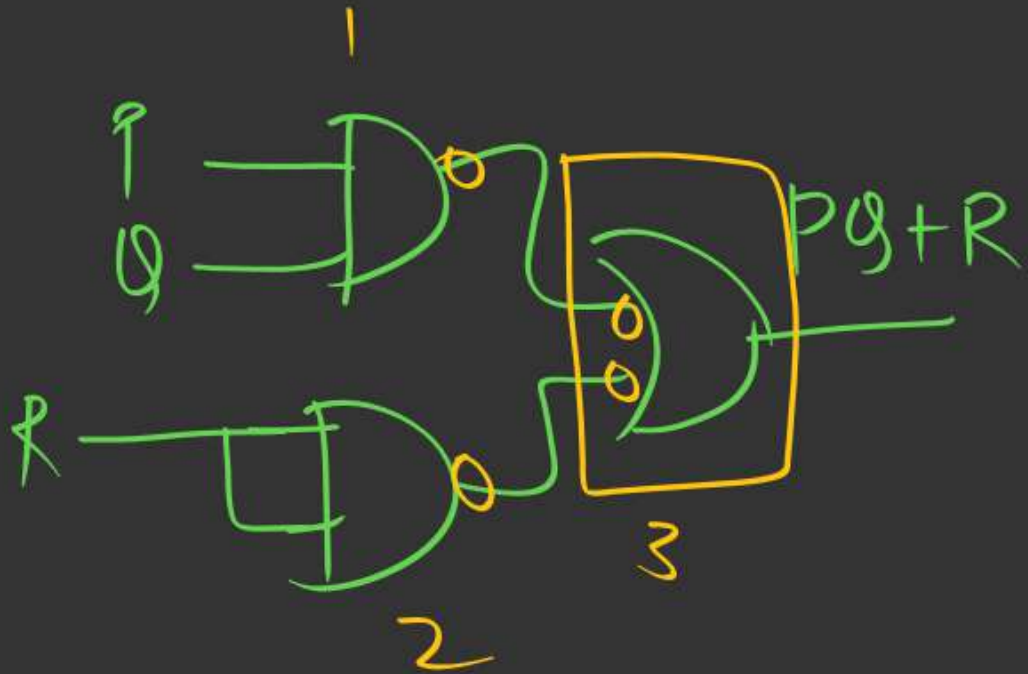
$$\begin{aligned} y &= PQ + R \\ &= PQ + R \cdot R \end{aligned}$$



$$y = PQ + R$$


NOR → POS

↓
(3)

$$y = \overline{R + PQ}$$

$$= (R + P)(R + Q)$$

AOT

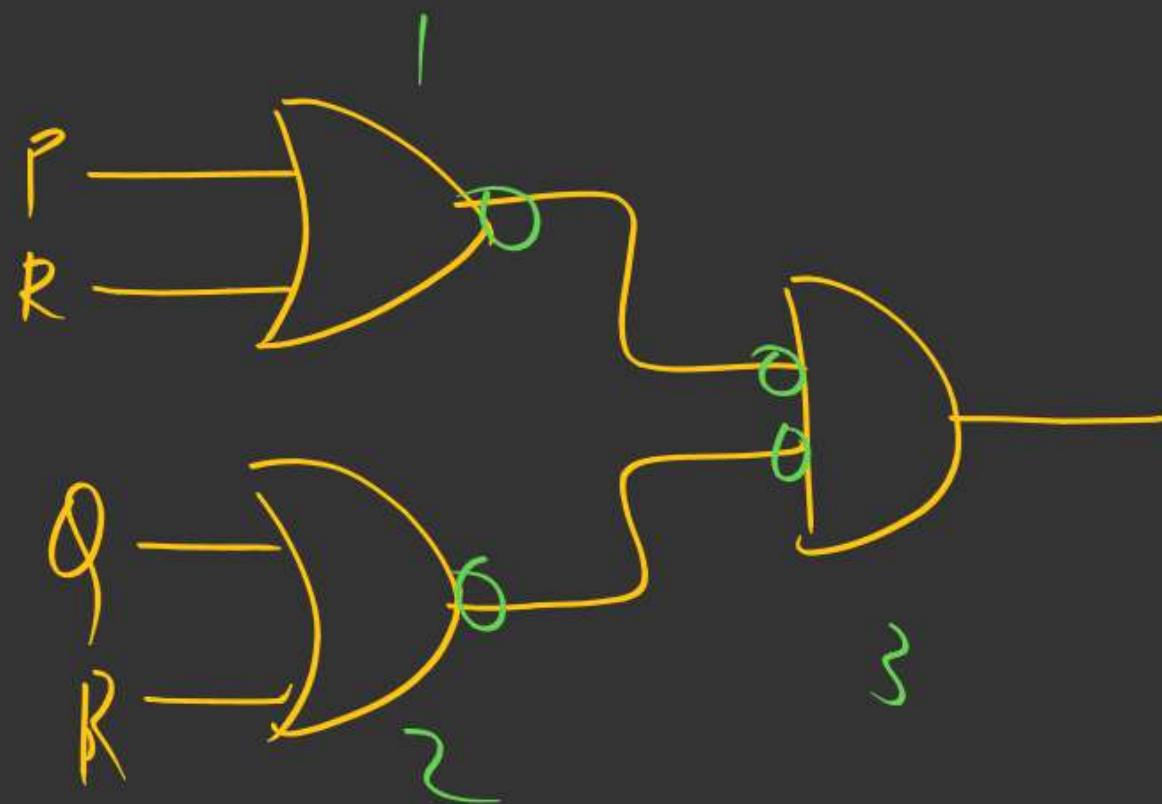

H.W

$$y = AB + BC + CD + DA$$

$$= \underline{B(A+C) + D(A+C)}$$


NAND

Let $\underline{A+C=P}$ $= \underline{B \cdot P + D \cdot P} \rightarrow 3$

3 ←

$$P = A + C$$
$$= A \cdot A + C \cdot C$$

Ans: (6)

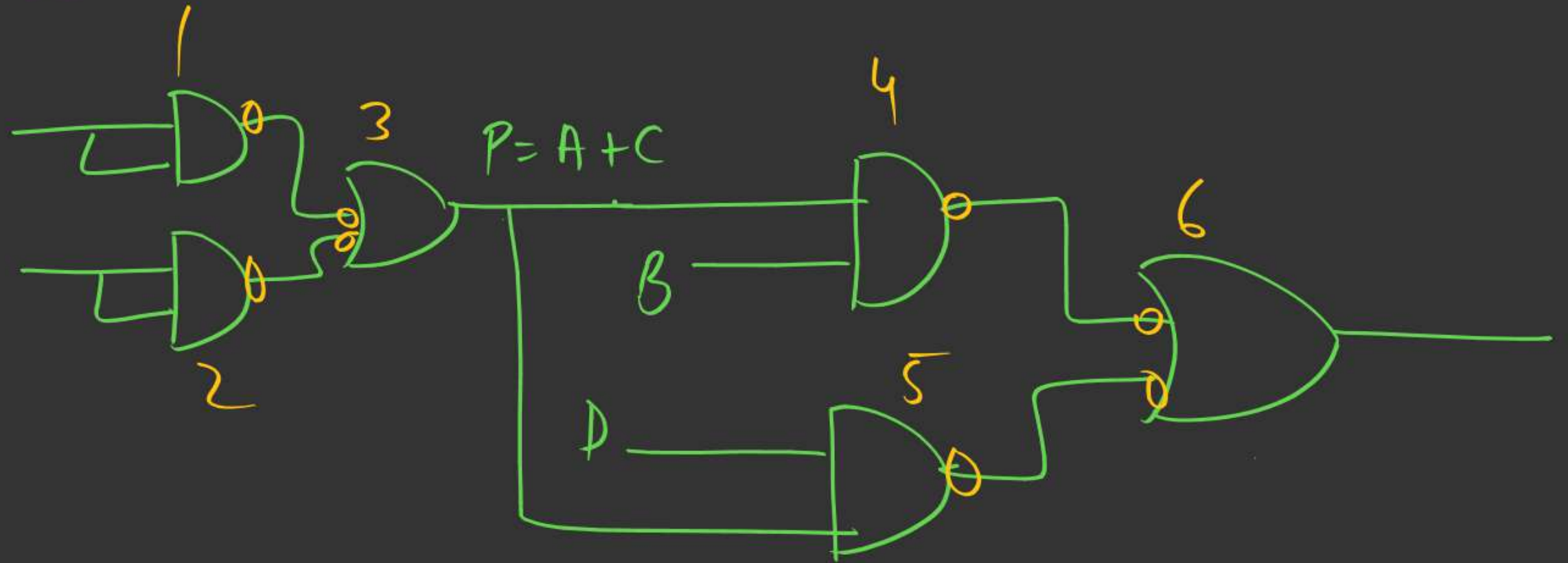

9
8
6


exception $\rightarrow$ XOR

XOR

$$y = A\bar{B} + \bar{A}B$$

$$= A \oplus B$$

(4) NAND
(5) NOR

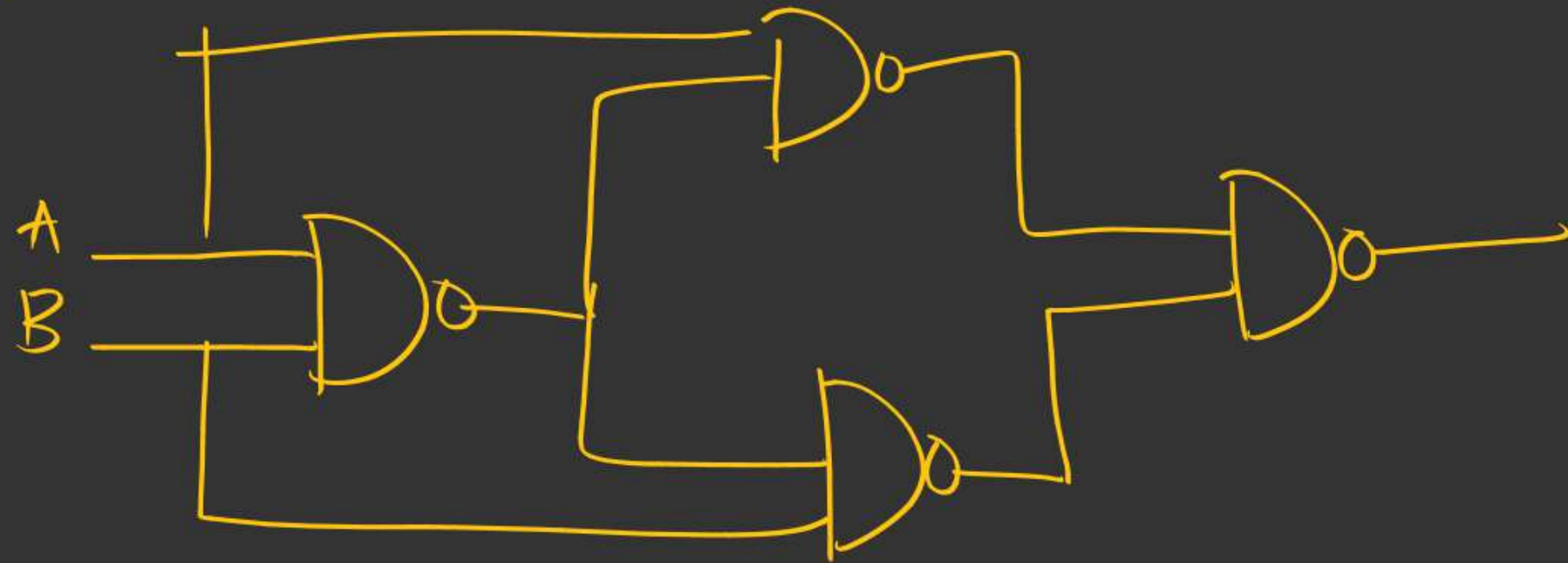

msq

(Q) $f(P, Q) = P \oplus QP \oplus Q$

$\bar{f}$ is equivalent to ?

A) NAND

☒ B) OR

C) min 2 NAND gates reqd

☒ D) min 3 NAND " "

Appr 2:-

(Backup)

P	Q	P.Q	$f = P \oplus P.Q \oplus Q$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

} OR

(Q.2) $F(P, Q) = \underbrace{(P+Q)}_X \oplus P$

$$f = x \oplus p$$

$$= \overline{X} P + \overline{P} X$$


$$= (\overline{P+Q}) \cdot P + \overline{P} \cdot (P+Q)$$

$$= \cancel{\bar{P} \cdot \bar{Q} \cdot P} + \cancel{\bar{P} \cdot P} + \bar{P} Q$$

$$= \overline{PQ}$$

- A) $P \cdot Q$
~~B) $\overline{P} Q$~~
 C) $\overline{Q} P$
 D) $P + Q$

(Q.3)

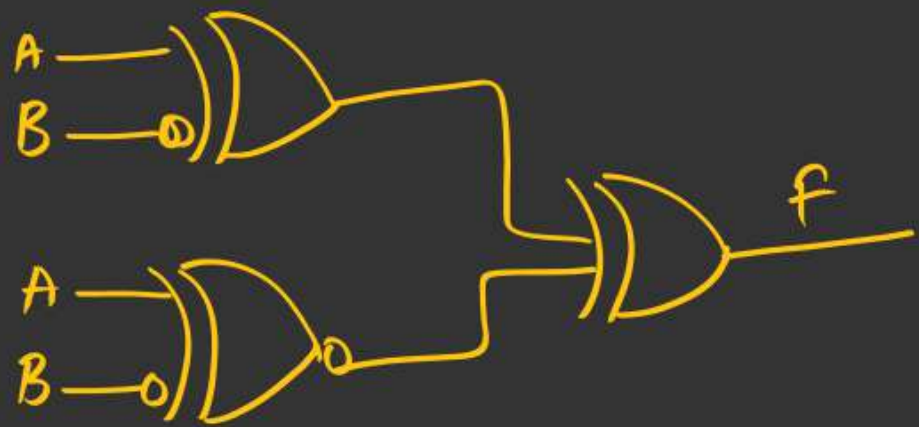

50%

A) 0

B) $A \oplus B$

C) $A \odot B$

✓ D) 1

$$f = (A \oplus \overline{B}) \oplus (A \odot \overline{B})$$

$$= \underbrace{(A \odot B)}_P \oplus \underbrace{(A \oplus B)}_{\overline{P}} = P \oplus \overline{P} = \textcircled{1}$$

$$(Q.1) \quad F(P, Q, R) = Q \cdot P \cdot \bar{R} + P + R \cdot P \cdot Q$$

min NAND gates?


26%

$$F(P, Q, R) = Q \cdot P \cdot \bar{R} + P + R \cdot P \cdot Q$$

$$= P(Q\bar{R} + 1 + QR)$$

$$= P$$

Ans. 0

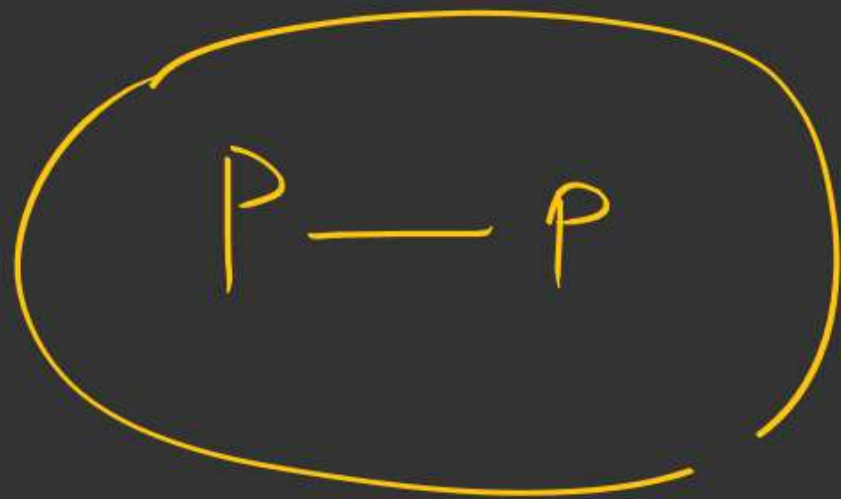

(8)

$$F = P + P\overline{Q}$$

$$= P(1 + \overline{Q})$$

$$= \textcircled{P}$$

$$(Q) \quad F(P, Q) = \overline{P} \cdot \overline{Q} + P \cdot Q + \overline{P} \cdot Q$$

$$= \overline{P}(\overline{Q} + Q) + P \cdot Q$$

$$= \overline{P} \cdot 1 + P \cdot Q$$

$$= \overline{P} + P \cdot Q$$

$$= (\overline{P} + P) (\overline{P} + Q)$$

$$F(P, Q)$$

$$= \underline{\underline{(\overline{P} + Q)}}$$

$$(9) \quad F(P, Q) = \bar{P} \cdot Q + \bar{P} \cdot \bar{Q} + P \cdot Q + P \cdot \bar{Q}$$

$$= \bar{P}(Q + \bar{Q}) + P(Q + \bar{Q})$$

$$= \bar{P} + P$$

$$= 1$$

min-terms


$$F = (\bar{P} \cdot Q + P \cdot \bar{Q}) + P \cdot Q + \bar{P} \cdot \bar{Q}$$

$$= \underbrace{(P \oplus Q)}_A + \underbrace{(P \odot Q)}_{\bar{A}}$$

$$= A + \bar{A}$$

$$= 1$$

$n=1$ variable :-

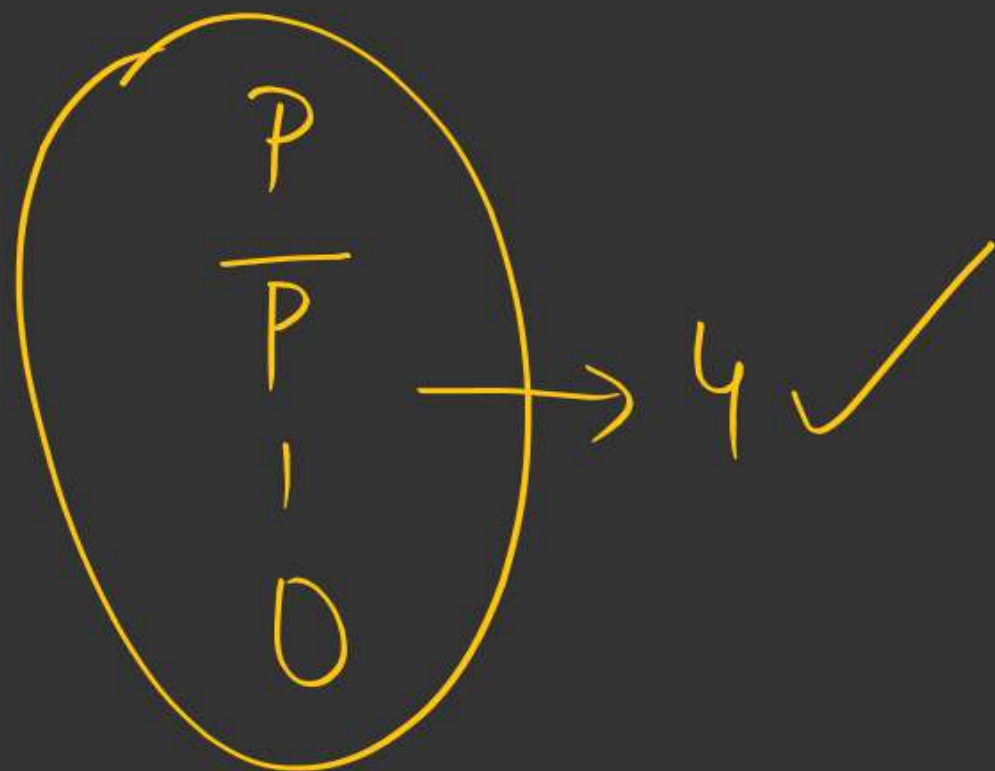

$n=2$ i/p var

How many simplified

O/p's ?

16

<u>P, Q</u>		(SOP) <u>minterms</u>	(POS terms) <u>max terms</u>
1	P	$P \cdot Q$	$P + Q$
0	$\overline{P}$	$P \cdot \overline{Q}$	$P + \overline{Q}$
	Q	$\overline{P} \cdot Q$	$\overline{P} + Q$
	$\overline{Q}$	$\overline{P} \cdot \overline{Q}$	$\overline{P} + \overline{Q}$
		(4)	(4)

$$\overline{P} \cdot \overline{Q} + P \cdot Q = P \odot Q$$

$$\overline{P} \cdot Q + P \cdot \overline{Q} = P \oplus Q$$

(2)

(16)

In general,

'n' i/p variables

2^n

distinct expressions can be formed



$(2^n \rightarrow \text{minterms})$

$(2^n \rightarrow \text{maxterms})$

$$(Q) \quad y = A + BC + \bar{A}C = ?$$

Options $\rightarrow$ PDF

open PDF Lec-4 H.W (24th April)

(Q.1) $PQ + QR + \bar{P}R$ simplifies to?

$\begin{matrix} P & X \\ Q & X \\ R & X \end{matrix}$

- ✓ A) $(\bar{P}+Q)(Q+R)$
B) $PQ + Q\bar{R}$
C) $PQ + \bar{P}R$
D) $\bar{P}R + Q\bar{R}$

$$PQ + Q\bar{R} + \bar{P}R$$

$$\begin{aligned} \underline{Q(P + \bar{R})} + \underline{\bar{P} \cdot R} &= Q \cdot X + \bar{X} \\ &= (Q + \bar{X})(X + \bar{X}) \\ &= \underline{\underline{(Q + \bar{X})}} \end{aligned}$$

$$\text{Let } P + \bar{R} = X$$

$$\begin{aligned} \bar{X} &= \overline{P + \bar{R}} \\ &= \bar{P} \cdot R \end{aligned}$$

$$J = Q + \bar{X}$$

$$\begin{aligned} \bar{X} = \bar{P} \cdot R &= \underline{\underline{Q + \bar{P} R}} \\ &= (Q + \bar{P})(Q + R) \end{aligned}$$

SOP $\rightarrow$ POS

POS $\xrightarrow{f}$ SOP

SOP

msq

(Q.2) $f(p, q, r) = \sum (1, 2, 4, 6, 7)$

then $f(p, q, r)$ is ?

A) $\pi(0, 3, 5)$

☒ B) $\sum(0, 3, 5)$

C) $\sum(1, 2, 4, 6, 7)$

☒ D) $\pi(1, 2, 4, 6, 7)$

Ans B, D

H.W

$$y = (P + Q + RS) (\bar{P} + Q + \bar{R} \cdot S) (\bar{P} + Q + R)$$

Simplify

==



2 mins Summary



- Min universal gates
- Imp Practice Questions



THANK - YOU

